



# Digital System Design

---

Hajar Falahati

[hfalahati@ipm.ir](mailto:hfalahati@ipm.ir)  
[hfalahati@ce.sharif.edu](mailto:hfalahati@ce.sharif.edu)

# Combinational Logic & Verilog

---

- Combinational Logic
  - Use **always block** + “**blocking**” assignments
    - Normally for high-complexity Comb. Logic
    - When output depends on several conditions, which requires if-else
- Sequential Logic
  - Can **only** be realized using an **always block**
  - When using the **always block** for the sequential Logic, “**Non-blocking**” assignments are used

# Outline

---


- How to implement FSMs




# FSM

---

# Moore and Mealy Machines

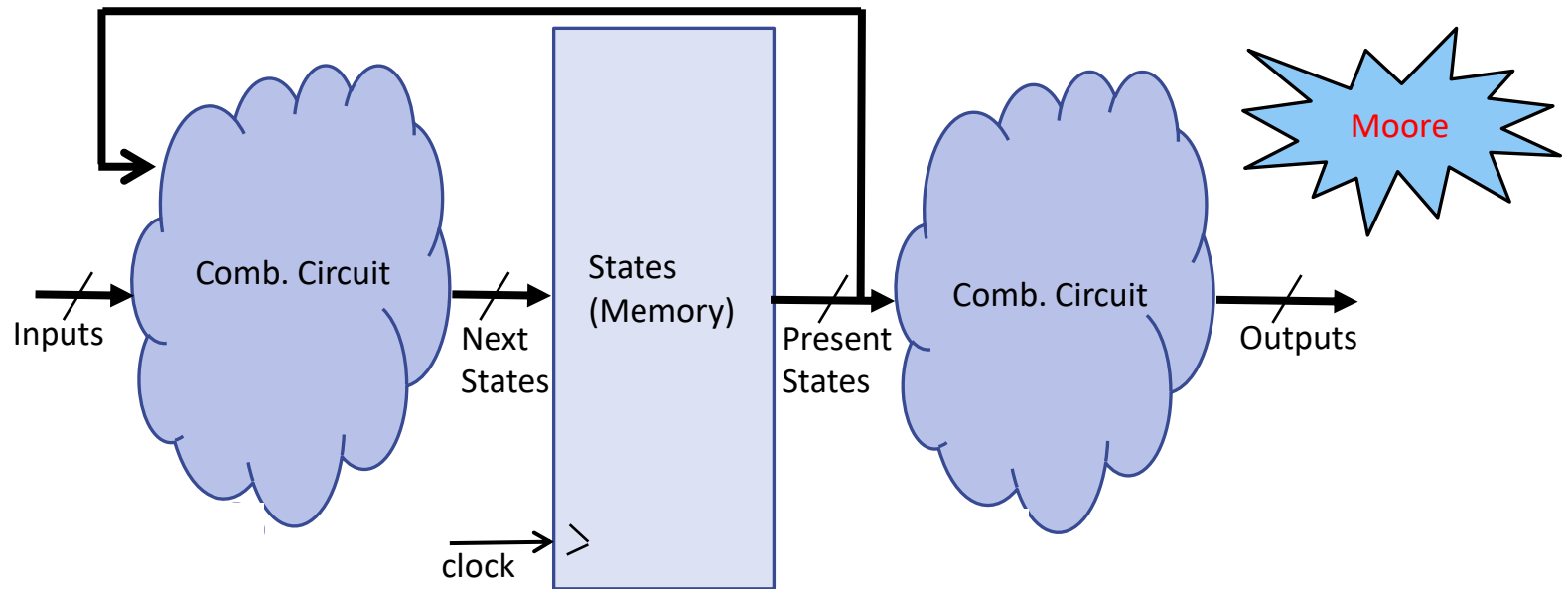

# Moore and Mealy Machines


 


# How to Describe FSMs in Verilog?

---


- Determine how to derive
  - Next State (NS)
  - Current State (CS)
  - Output

# Verilog Statements and Verilog

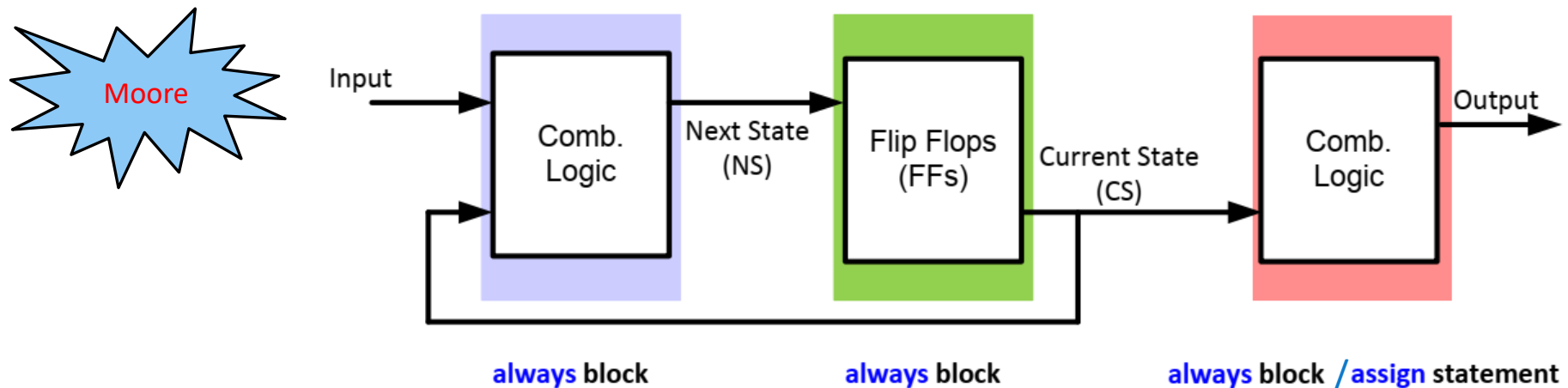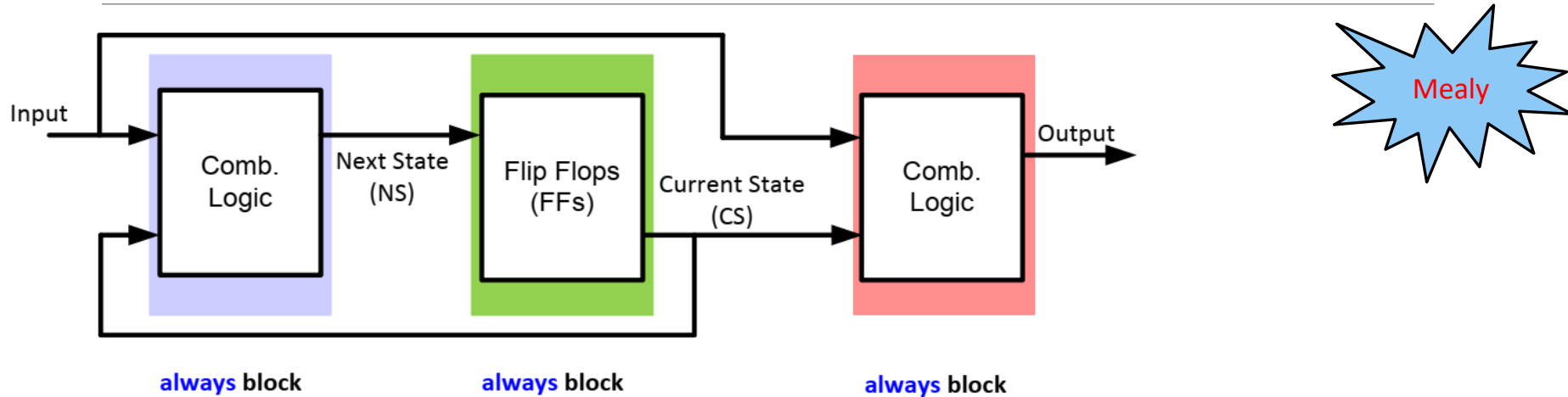




# Mealy FSM Code Structure

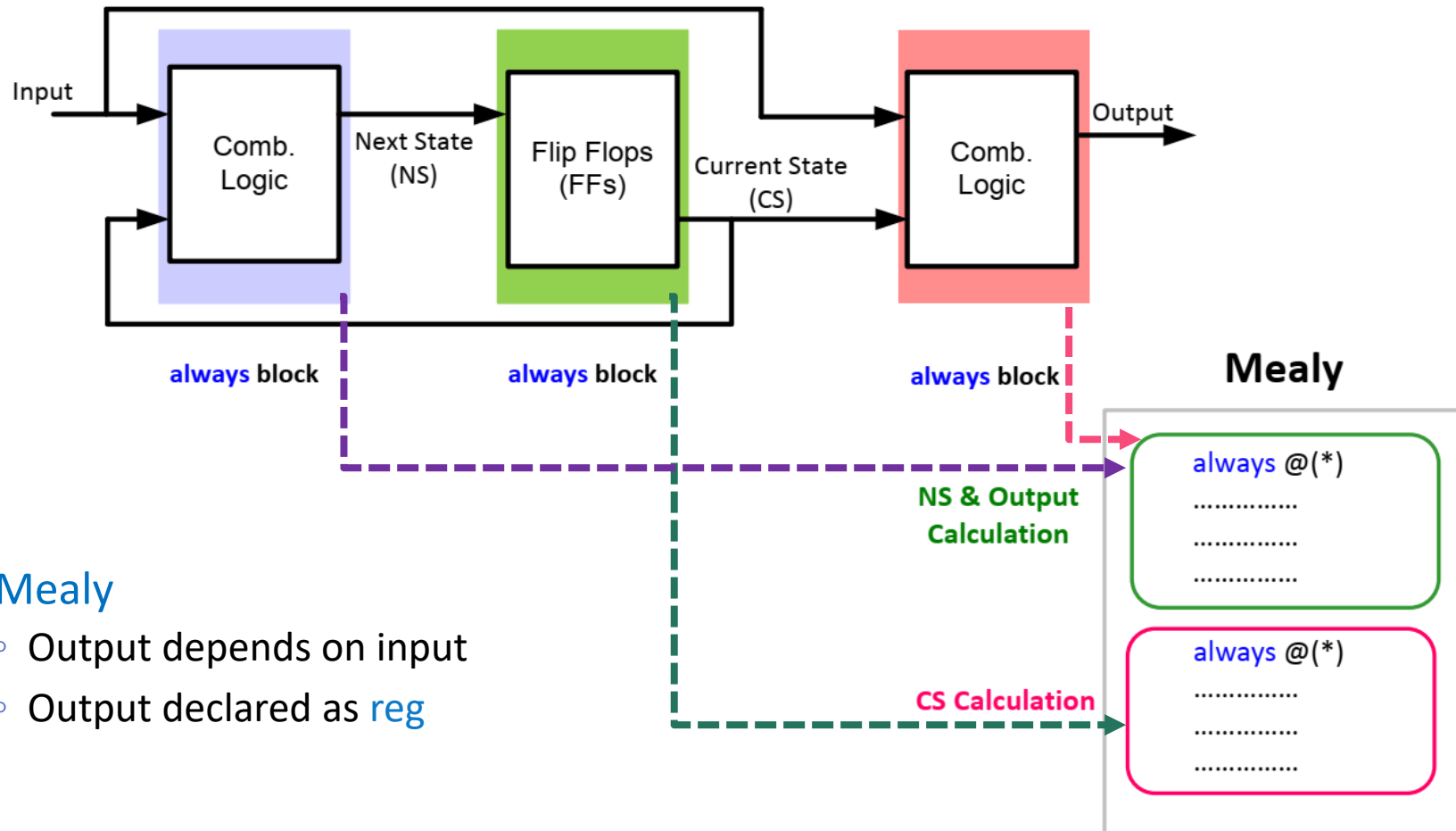


# Moore FSM Code Structure

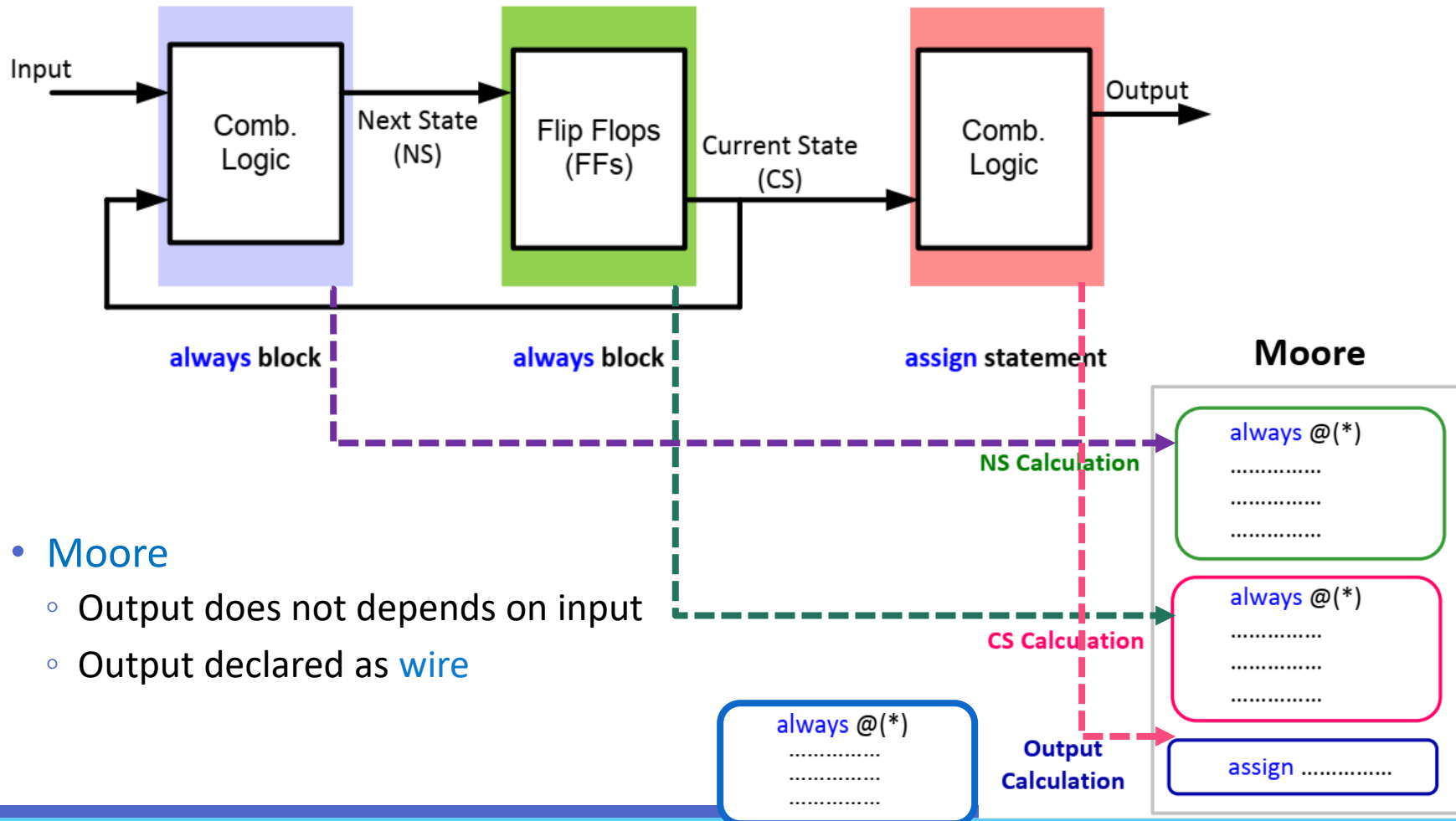
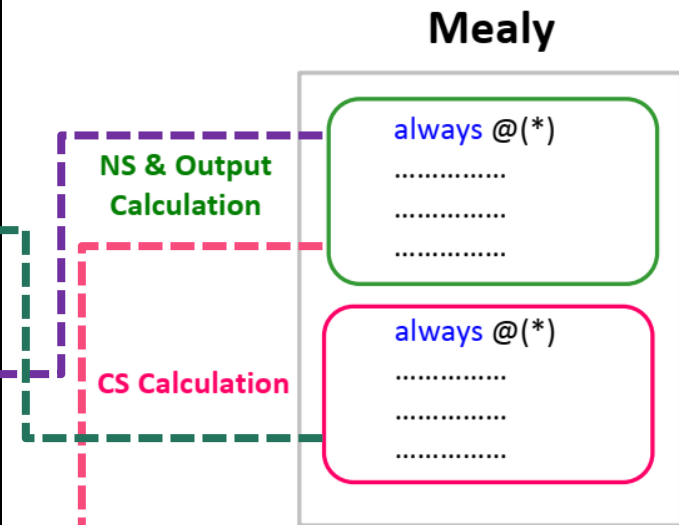
# General Mealy FSM

```
module mealy(outs, inputs, clk);  
    input      inputs, clk;  
    output reg  outs;  
  
    reg [log-num-states-1:0] state, next_state;  
  
    always @(posedge/negedge clk)  
        // Change the state  
  
    always @(state or inputs)  
        // Evaluate next state  
  
    always @(state or inputs)  
        // Evaluate output  
endmodule
```



# General Moore FSM

## Moore

```
module moore(outs, inputs, clk);  
    input      inputs, clk;  
    output reg  outs;  
  
    reg [log-num-states-1:0] state, next_state;  
  
    always @(posedge/negedge clk)  
        // Change the state  
  
    always @(state or inputs)  
        // Evaluate next state  
  
    always @(state)  
        // Evaluate output  
endmodule
```

NS Calculation

CS Calculation

Output  
Calculation

always @(\*)

.....  
.....  
.....

always @(\*)

.....  
.....  
.....



assign .....

always @(\*)

.....  
.....  
.....


# Finite State Machine (FSM)

Moore FSM

  

What are the tradeoffs?


Mealy FSM

 
 
# FSM Sample 1


---

- Recognize a specific bit pattern (*110*) in a bitstream


 
# 110 Detector


- State **S0**
  - We have **not** recognized **any** useful pattern
- State **S1**
  - We have recognized the **pattern '1'**
- State **S2**:
  - We have recognized the **pattern '11'**
  - **Output**: recognizing an input bit '0' in state S2



# 110 Detector : Module

```
module mealy (out, i, clk, reset);
```


```
endmodule
```

 


 
# 110 Detector : Ports


```
module mealy (out, i, clk, reset);  
  input  i, clk, reset;  
  output out;  
  reg    out;  
  
  _____  
  
endmodule
```



# 110 Detector : Signals

```
module mealy (out, i, clk, reset);  
  input  i, clk, reset;  
  output out;  
  reg    out;  
  reg [1:0] state, next_state;
```

```
endmodule
```

 

# 110 Detector : Next State & Output

```
module mealy(out, i, clk, reset);  
  input  i, clk, reset;  
  output out;  
  reg    out;  
  reg [1:0] state, next_state;
```

```
  always @(state or i)  
  case (state)  
    2'b00 : next_state = i ? 1 : 0;  
    2'b01 : next_state = i ? 2 : 0;  
    2'b10 : next_state = i ? 2 : 0;  
    default: next_state = 0;  
  endcase
```

```
  always @(state or i)  
  if (state == 2'b10 && i==0) out = 1;  
  else out = 0;
```

```
endmodule
```


## Mealy

NS & Output  
Calculation

```
always @(*)  
.....  
.....  
.....
```

CS Calculation
 
```
always @(*)  
.....  
.....  
.....
```



# 110 Detector : Current State

```
module mealy(out, i, clk, reset);
  input  i, clk, reset;
  output out;
  reg    out;
  reg [1:0] state, next_state;
```

```
always @(posedge clk)
  if( reset) state <= 0;
  else state <= next_state;
```

```
always @(state or i)
  case (state)
    2'b00 : next_state = i ? 1 : 0;
    2'b01 : next_state = i ? 2 : 0;
    2'b10 : next_state = i ? 2 : 0;
    default: next_state = 0;
  endcase
```

```
always @(state or i)
  if (state == 2'b10 && i==0) out = 1;
  else out = 0;
```

```
endmodule
```

## Mealy

NS & Output  
Calculation


```
always @(*)
```

```
.....
```

CS Calculation

```
always @(*)
```


```
.....
```

 

# 110 Detector :
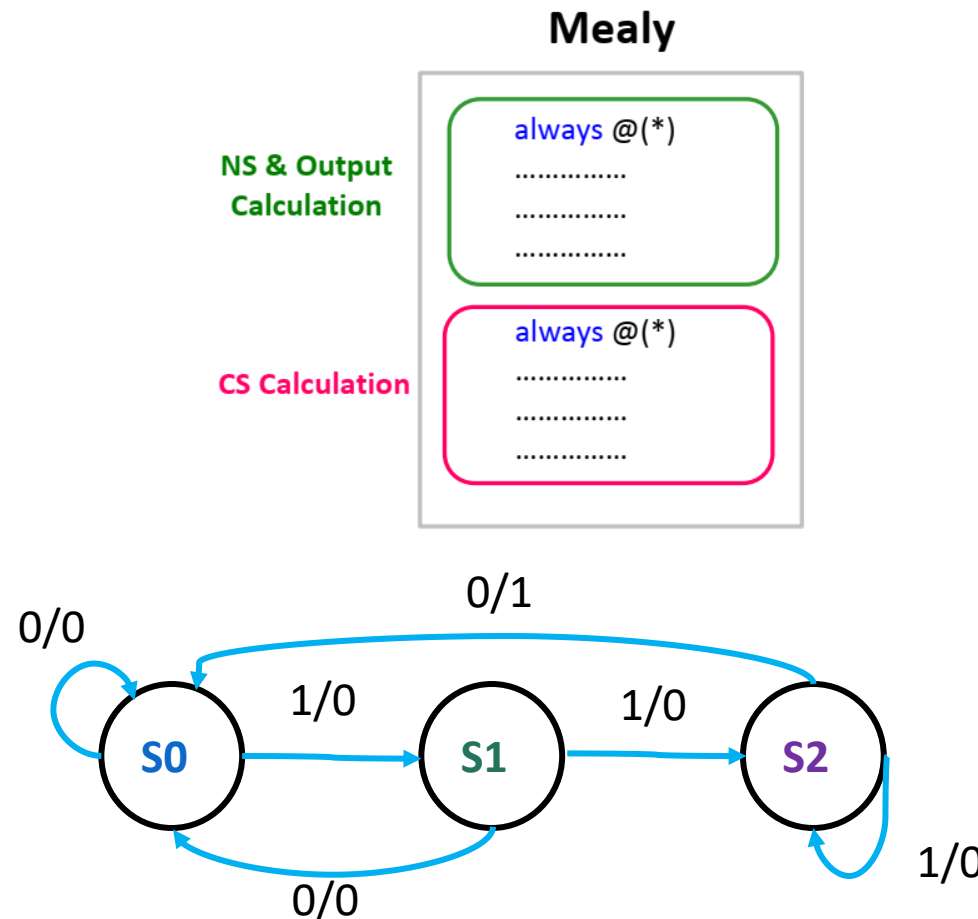
## Merged Next State + Output

```
module mealy(out, i, clk, reset);  
  input  i, clk, reset;  
  output out;  
  reg    out;  
  reg [1:0] state, next_state;  
  
  always @(posedge clk)  
    if( reset) state <= 0;  
    else state <= next_state;  
  
  always @(state or i)  
    case (state)  
      2'b00 : next_state <= i ? 1 : 0;  
      2'b01 : next_state <= i ? 2 : 0;  
      2'b10 :  
        begin  
          next_state <= i ? 2 : 0;  
          out <= i ? 0:1;  
        end  
      default: next_state = 0;  
    endcase  
  
endmodule
```



# 110 Detector: Modular

```

module mealy(out, i, clk, reset);
  input  i, clk, reset;
  output out;
  reg    out;
  reg [1:0] state, next_state;

  always @(posedge clk)
    if( reset) state <= 0;
    else state <= next_state;


  cmp_next_state(next_state, state, i);
  cmp_output(next_state, state, i);
endmodule

```

```

module cmp_next_state (output reg [1:0] next_state, input [1:0] state,
                      input i);
  always @(state or i)
  begin
    if (state == 0)    next_state = i ? 1 : 0;
    else if (state == 1) next_state = i ? 2 : 0;
    else if (state == 2) next_state = i ? 2 : 0;
    else next_state = 0;
  end
endmodule

```

 

```

module cmp_output (output reg out, input [1:0] state,
                  input i);
  always @(state or i)
  begin
    if (state == 2'b10 && i==0) out = 1;
    else out = 0;
  end
endmodule

```

# FSM Sample 2


---

- Recognize a specific bit pattern (*110*) in a bitstream using Moore FSM


 
# Moore FSM Sample : 110

- State **S0**
  - We have **not** recognized **any useful pattern**
- State **S1**
  - We have recognized the **pattern '1'**
- State **S2**:
  - We have recognized the **pattern '11'**
- State **S3**:
  - We have recognized the **pattern '110'**
  - **Output** becomes 1





# Moore 110 Detector : Module

```
module moore (out, i, clk, reset);
```

```
endmodule
```

## Moore

NS Calculation

```
always @(*)
```


CS Calculation

```
always @(*)
```

Output  
Calculation



```
assign .....
```

```
always @(*)
```

 

 
 
# Moore 110 Detector : Ports

```
module moore (out, i, clk, reset);  
  input  i, clk, reset;  
  output out;  
  reg   out;
```


 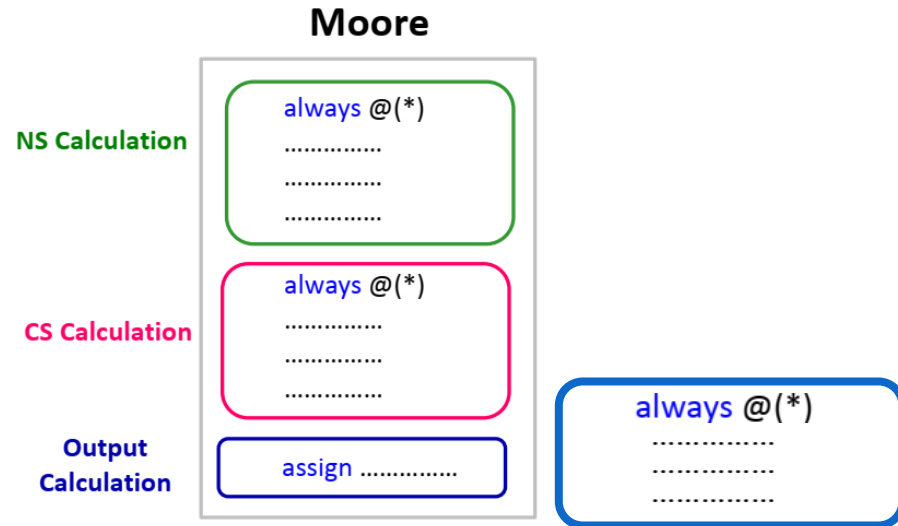
# Moore 110 Detector : Signals

```
module moore (out, i, clk, reset);  
  input  i, clk, reset;  
  output out;  
  reg    out;  
  reg [1:0] state, next_state;
```



# Moore 110 Detector : Next State & Output

```
module moore (out, i, clk, reset);
  input  i, clk, reset;
  output out;
  reg    out;
  reg [1:0] state, next_state;
```

```
always @(state or i)
  case (state)
    2'b00 : next_state = i ? 1 : 0;
    2'b01 : next_state = i ? 2 : 0;
    2'b10 : next_state = i ? 2 : 3;
    2'b11 : next_state = i ? 1 : 0;
    default: next_state = 0;
  endcase
```

```
always @(state)
  if (state == 2'b11) out = 1;
  else                out = 0;
```

endmodule

## Moore

NS Calculation

```
always @(*)
  .....
```


CS Calculation

```
always @(*)
  .....
```

Output  
Calculation

```
assign .....
```

```
always @(*)
  .....
```

 

# Moore 110 Detector : Current State

```
module moore(out, i, clk, reset);
  input  i, clk, reset;
  output out;
  reg    out;
  reg [1:0] state, next_state;
```

```
always @(posedge clk)
  if( reset) state <= 0;
  else state <= next_state;
```

```
always @(state or i)
  case (state)
    2'b00 : next_state = i ? 1 : 0;
    2'b01 : next_state = i ? 2 : 0;
    2'b10 : next_state = i ? 2 : 3;
    2'b11 : next_state = i ? 1 : 0;
    default: next_state = 0;
  endcase
```

```
always @(state )
  if (state == 2'b11 ) out = 1;
  else out = 0;
```

endmodule

## Moore

NS Calculation

```
always @(*)
  .....
  .....
  .....
```


CS Calculation

```
always @(*)
  .....
  .....
  .....
```

Output  
Calculation

```
assign .....
```
 
```
always @(*)
  .....
  .....
  .....
```



# Moore 110 Detector : Current State

```
module moore(out, i, clk, reset);
  input  i, clk, reset;
  output out;
  reg    out;
  reg [1:0] state, next_state;
```

```
  always @(posedge clk)
    if( reset) state <= 0;
    else state <= next_state;
```


```
  cmp_next_state(next_state, state, i)
```

```
  cmp_output(next_state, state);
```

```
endmodule
```


```
module cmp_next_state(output reg [1:0] next_state, input [1:0] state,
  input i);
  always @(state or i)
  begin
    if (state == 0)    next_state = i ? 1 : 0;
    else if (state == 1) next_state = i ? 2 : 0;
    else if (state == 2) next_state = i ? 2 : 3;
    else if (state == 3) next_state = i ? 1 : 0;
    else next_state = 0;
  end
endmodule
```
 
```
module cmp_output(output reg out,
  input [1:0] state);
  always @(state)
  begin
    if (state == 2'b11) out = 1;
    else                out = 0;
  end
endmodule
```



 
# Traffic Signal Controller

- Traffic Signal for main highway gets highest priority
  - Cars are continuously present on the main highway
  - Main highway signal remains green by default
- Traffic signal for the country road
  - Must turn **green** only long enough to let the cars on the country road go
  - As soon as there are **no cars** on the country road
    - Country road traffic signal turns **yellow** and then **red**
    - Traffic signal on the main highway turns **green** again
  - There is a sensor to detect cars waiting on the country road
    - Sends a signal X as input to the controller.
    - $X = 1$  if there are cars on the country road; otherwise,  $X = 0$ .



# Traffic Signal Controller (cont'd)

---

 

| State | Signals           |
|-------|-------------------|
| S0    | Hwy = G Cntry = R |
| S1    | Hwy = Y Cntry = R |
| S2    | Hwy = R Cntry = R |
| S3    | Hwy = R Cntry = G |
| S4    | Hwy = R Cntry = Y |



# Traffic Signal Controller (cont'd)

---

```
`define TRUE 1'b1
`define FALSE 1'b0

//Delays
`define Y2RDELAY 3 //Yellow to red delay
`define R2GDELAY 2 //Red to green delay

module sig_control
    (hwy, cntry, X, clock, clear);

    //I/O ports
    output [1:0] hwy, cntry;
        //2-bit output for 3 states of signal
        //GREEN, YELLOW, RED;
    reg [1:0] hwy, cntry;
        //declared output signals are registers

    input X;
        //if TRUE, indicates that there is car on
        //the country road, otherwise FALSE
    input clock, clear;

    parameter RED = 2'd0,
        YELLOW = 2'd1,
        GREEN = 2'd2;


    //State definition      HWY      CNTRY
    parameter S0 = 3'd0, //GREEN      RED
        S1 = 3'd1, //YELLOW      RED
        S2 = 3'd2, //RED          RED
        S3 = 3'd3, //RED          GREEN
        S4 = 3'd4; //RED          YELLOW
```

# Traffic Signal Controller (cont'd)

```
//Internal state variables
reg [2:0] state;
reg [2:0] next_state;

//state changes only at positive edge of clock
always @(posedge clock)
    if (clear)
        state <= S0; //Controller starts in S0 state
    else
        state <= next_state; //State change


//Compute values of main signal and country signal
always @(state)
begin
    hwy = GREEN; //Default Light Assignment for Highway light
    cntry = RED; //Default Light Assignment for Country light
    case(state)
        S0: ; // No change, use default
        S1: hwy = YELLOW;
        S2: hwy = RED;
        S3: begin
            hwy = RED;
            cntry = GREEN;
        end
        S4: begin
            hwy = RED;
            cntry = `YELLOW;
        end
    endcase
end
```

 

| State | Signals           |
|-------|-------------------|
| S0    | Hwy = G Cntry = R |
| S1    | Hwy = Y Cntry = R |
| S2    | Hwy = R Cntry = R |
| S3    | Hwy = R Cntry = G |
| S4    | Hwy = R Cntry = Y |
 
# Traffic Signal Controller (cont'd)

```
//State machine using case statements
always @(state or X)
begin
    case (state)
        S0: if(X)
            next_state = S1;
        else
            next_state = S0;
        S1: begin //delay some positive edges of clock
            repeat(`Y2RDELAY) @(posedge clock) ;
            next_state = S2;
        end
        S2: begin //delay some positive edges of clock
            repeat(`R2GDELAY) @(posedge clock);
            next_state = S3;
        end
        S3: if(X)
            next_state = S3;
        else
            next_state = S4;
        S4: begin //delay some positive edges of clock
            repeat(`Y2RDELAY) @(posedge clock) ;
            next_state = S0;
        end
        default: next_state = S0;
    endcase
end
endmodule
```



| State | Signals           |
|-------|-------------------|
| S0    | Hwy = G Cntry = R |
| S1    | Hwy = Y Cntry = R |
| S2    | Hwy = R Cntry = R |
| S3    | Hwy = R Cntry = G |
| S4    | Hwy = R Cntry = Y |

# Traffic Signal Controller: Test

---

```
//Stimulus Module
module stimulus;

wire [1:0] MAIN_SIG, CNTRY_SIG;
reg CAR_ON_CNTRY_RD;
    //if TRUE, indicates that there is car on
    //the country road
reg CLOCK, CLEAR;

//Instantiate signal controller
sig_control SC(MAIN_SIG, CNTRY_SIG, CAR_ON_CNTRY_RD, CLOCK, CLEAR);

//Set up monitor
initial
    $monitor($time, " Main Sig = %b Country Sig = %b Car_on_cntry = %b",
              MAIN_SIG, CNTRY_SIG, CAR_ON_CNTRY_RD);

//Set up clock
initial
begin
    CLOCK = `FALSE;
    forever #5 CLOCK = ~CLOCK;
end

//control clear signal
initial
```

# Traffic Signal Controller: Test (cont'd)

---

```
//control clear signal
initial
begin
    CLEAR = `TRUE;
    repeat (5) @(negedge CLOCK);
    CLEAR = `FALSE;
end

//apply stimulus
initial
begin
    CAR_ON_CNTRY_RD = `FALSE;

    repeat(20)@(negedge CLOCK); CAR_ON_CNTRY_RD = `TRUE;
    repeat(10)@(negedge CLOCK); CAR_ON_CNTRY_RD = `FALSE;

    repeat(20)@(negedge CLOCK); CAR_ON_CNTRY_RD = `TRUE;
    repeat(10)@(negedge CLOCK); CAR_ON_CNTRY_RD = `FALSE;


    repeat(20)@(negedge CLOCK); CAR_ON_CNTRY_RD = `TRUE;
    repeat(10)@(negedge CLOCK); CAR_ON_CNTRY_RD = `FALSE;

    repeat(10)@(negedge CLOCK); $stop;
end
endmodule
```


# Sample Counter

---

- Design an up/down counter

 

# Up/Down Counter ASM

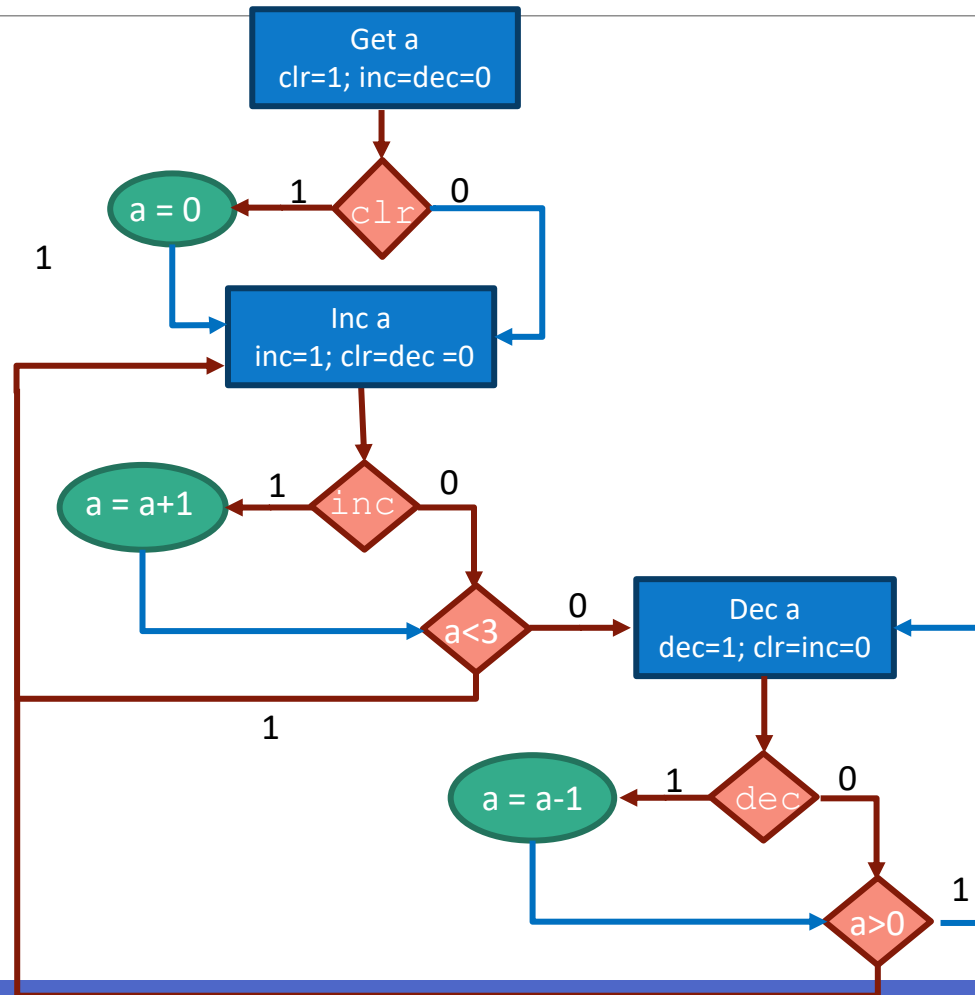

# Up/Down Counter: DataPath

---

```
module updown(c, inc, dec, clr)
  output reg [2:0] c;
  input  inc, dec, clr;
  reg    [2:0] a;

  always @(a)
    c = a;
  always@ (inc, dec, clr)
    begin
      if(inc) a = a + 1;
      if(dec) a = a - 1;
      if(clr) a = 0;
    end
endmodule
```



# Up/Down Counter: Control

```
module ctl_updown(input a, output inc, output dec, output clr)
  reg [1:0] state, next_state;

  always @(posedge clk)
    if( reset) state <= 0;
    else state <= next_state;

  always@ (state)
    case (state)
      2'b00:
        begin clr =1; inc = dec =0; end
      2'b01:
        begin inc =1; clr = dec =0; end
      2'b10:
        begin dec =1; clr = inc =0; end
      default: begin clr =1; inc = dec =0; end

  always@ (state)
    case (state)
      2'b00: next_state = 1;
      2'b01: next_state = (a<3)? 1: 2;
      2'b10: next_state = (a>0)? 2: 1;

endmodule
```

# Thank You

---

