




Digital System Design


Hajar Falahati

hfalahati@ipm.ir
hfalahati@ce.sharif.edu


Review: Module May Includes...

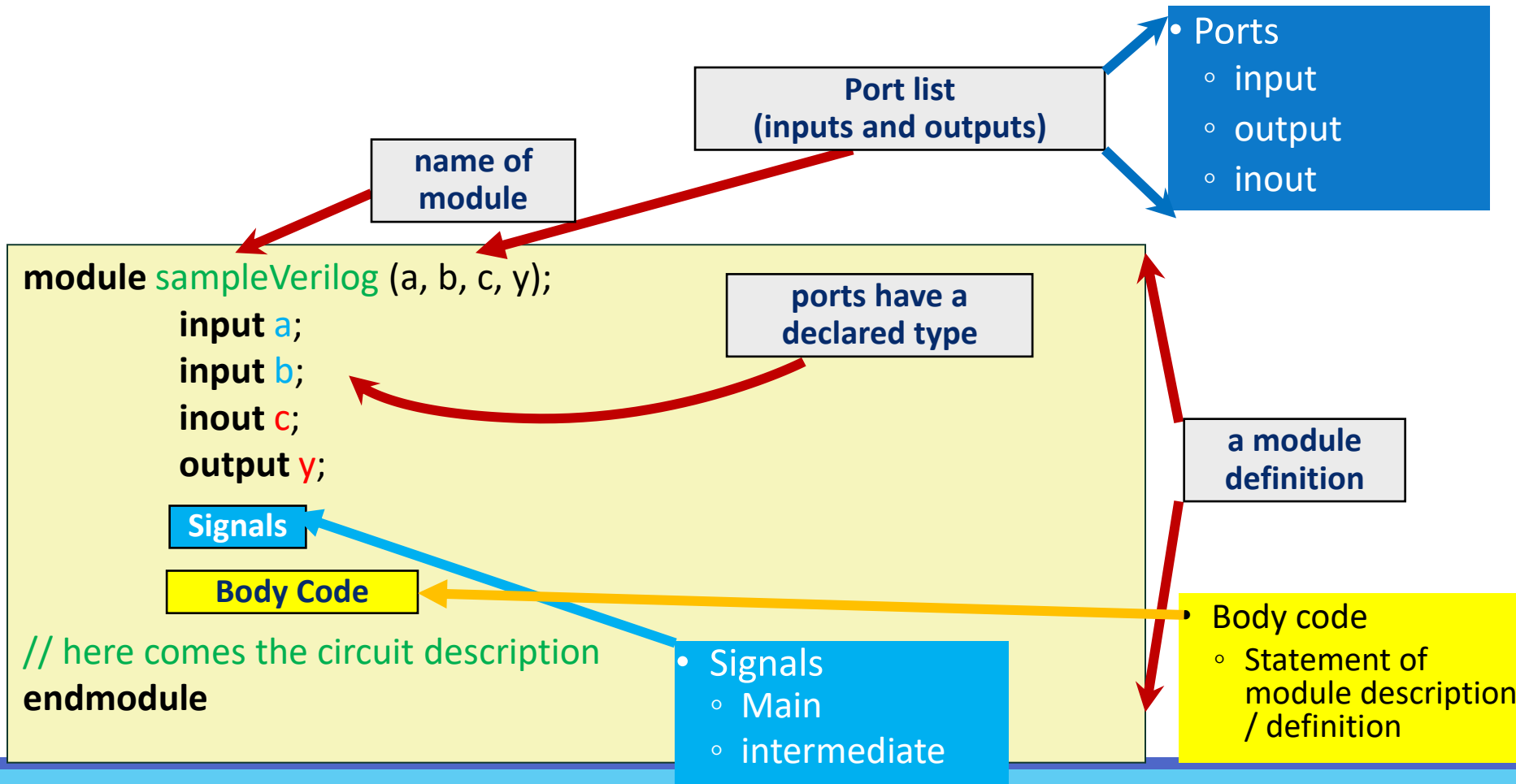

Review: Signal Value

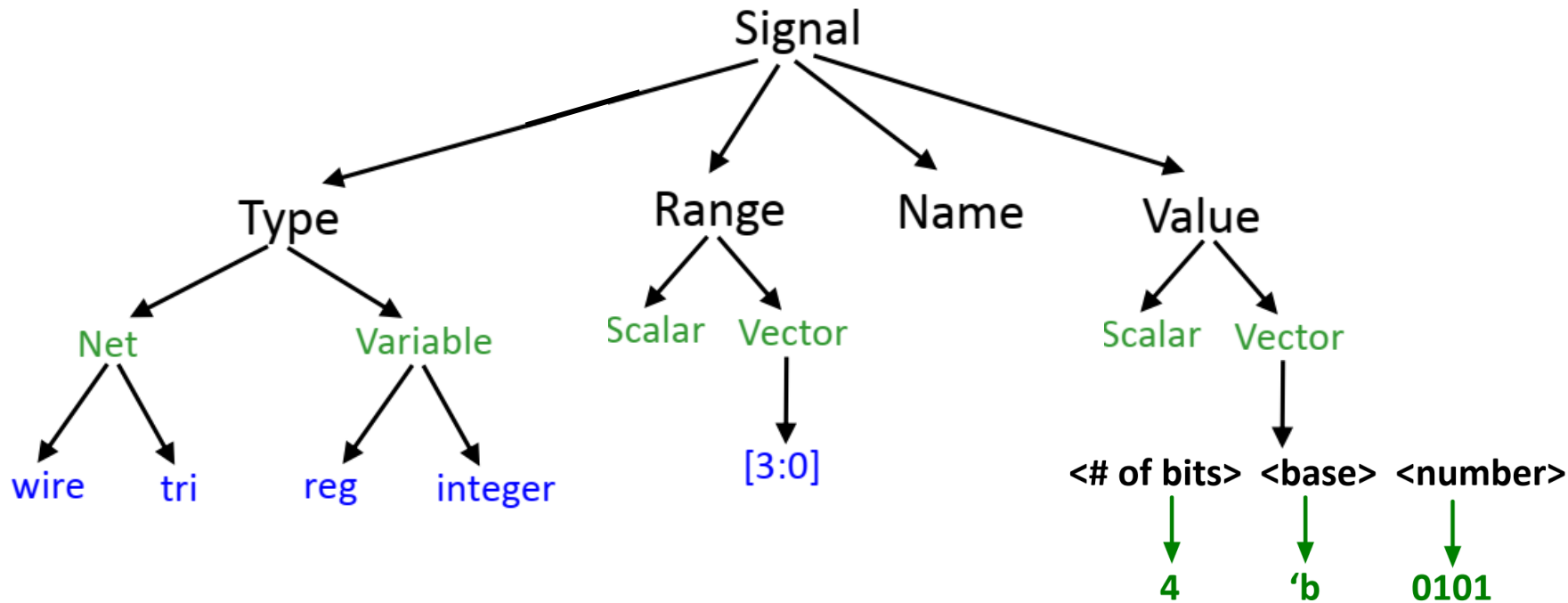

Review: Verilog Statement

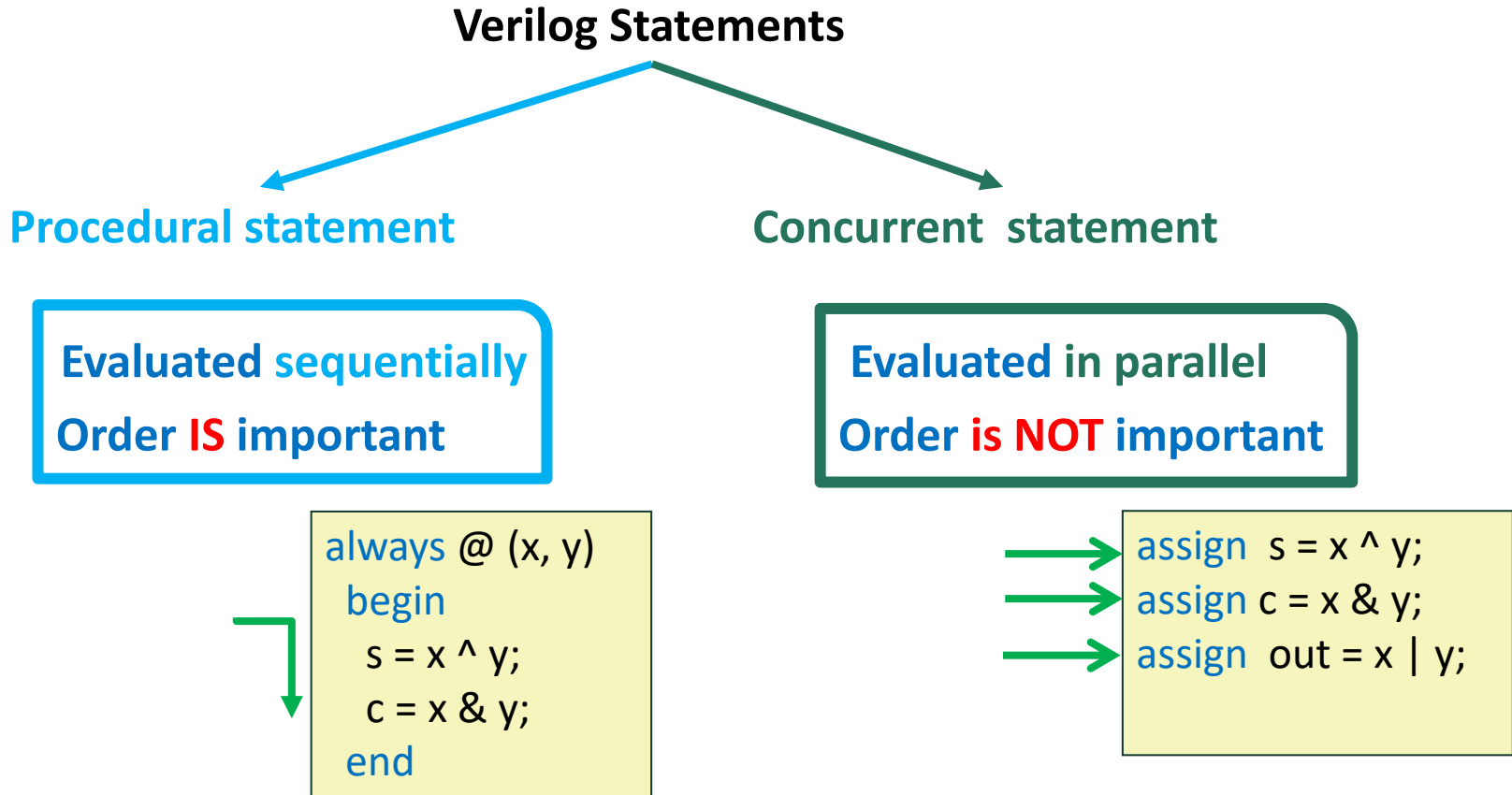

Outline

- Behavioral-level programming
 - Initial blocks
 - Always Blocks
- How to implement a combinational logic at behavioral-level?
- How to implement a sequential logic at behavioral-level?
- Writing a testbench



Verilog:


A language for All Abstraction Levels!

Behavioral

- Describe the behavior of a design without implying any specific internal architecture
- Define the behavior of the design as seen as its ports
 - Using high-level constructs
 - @, case, if, repeat, wait, while
 - Using any behavioral construct of the HDL in your testbench
 - Synthesis tools accept only a limited subset of these behavioral constructs


Behavioral Code
 
```
module sampleBehavioral (out, in, clk);  
    input in, clk;  
    output out;  
    reg out;  
  
    always @(in  
        @(posedge clk)  
            out <= repeat (2) @(posedge clk) in;  
endmodule
```




RTL

 
- Functional level
- Describe a design architecture in sufficient detail that a synthesis tool can construct the circuit
- RTL is the closet one to the actual hardware implementation
- RTL code includes a subset of all Verilog syntax
 - Not all Verilog syntax are synthesizable



RTL Code

 

 
```
module sampleBehavioral (out, in, clk);  
  input in, clk;  
  output out;  
  reg out;  
  always @(in)  
    @(posedge clk)  
      out<=repeat (2) @(posedge clk) in;  
endmodule
```



```
module sampleRTL (out, in, clk);  
  input in, clk;  
  output out;  
  reg out;  
  reg one, two;  
  always @(posedge clk)  
  begin  
    out <= two;  
    two <= one;  
    one <= in;  
  end  
endmodule
```

Structural Recall

 - Structural design description
- Appropriate for small library components
 - Using built-in Verilog primitives, such as the and gate
 - Describe your own User defined primitives (UDPs)




```
module sampleStructural (out, in, clk);  
    input in, clk;  
    output out;  
  
    FD1 one_reg (.Q(one), .D(in), .CP(clk));  
    FD1 one_reg (.Q(two), .D(one), .CP(clk));  
    FD1 one_reg (.Q(out), .D(two), .CP(clk));  
  
endmodule
```

Verilog:

A language for All Abstraction Levels!

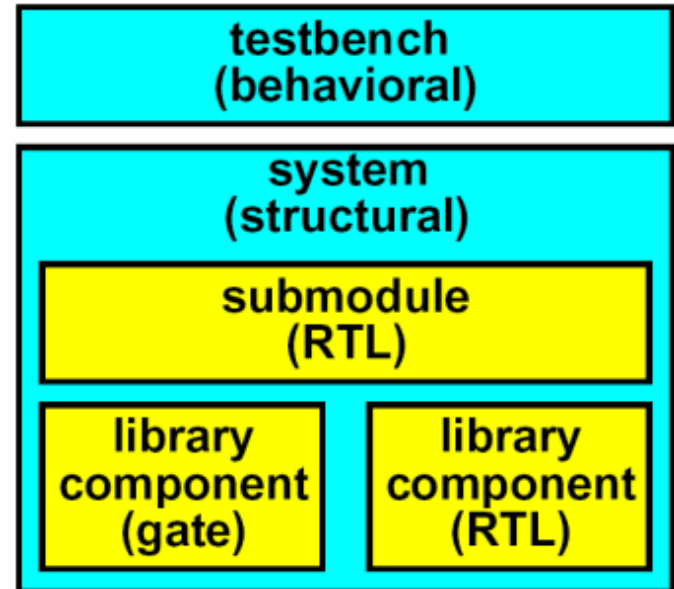- Designers usually mix levels of abstraction within a simulation
- RTL and gate-level library components
- RTL functional submodule descriptions
- Structural system netlist
- Behavioral system testbench



Operators

Operators 1, 2

Bitwise:

Operation	Result
1010 & 1100	1000
1010 1100	1110
~ 1010	0101
1101 ^ 0100	1001

```

&  1 0 1 0
    1 1 0 0
-----
    ↓ ↓ ↓ ↓
    1 0 0 0
  
```

Logical:

X || 1 = 1
X && 0 = 0

Operation	Result
1010 && 1100	1
2'b11 2'b00	1
! 0010	0
2'b1X && 2'b11	X

Non-zero operand=logical "1"

Any operand X/Z, result is X

Operators 3, 4

Reduction:

Operation	Result
& 1100	0
& 111	1
^ 0100	1

Relational:

A=2'b10

Operation	Result
B=(A == 2'b10)	B=1
B=(A == 2'b11)	B=0
B=(A === 2'b1x)	B=0
B=(A <= 2'b11)	B=1

== Used only with 0 and 1

=== Used with x and z

Operators 5, 6

Logical Shift:

A=6'b001100

Operation	Result
C = A >> 1	C = 000110
D = A << 2	D = 110000
F = A >> 3	F = 000001

Concatenation:

A=2'b11

B=3'b010

Operation	Result
{A, B}	5'b11010
{3{A}}	6'b111111
{B, B}	6'b010010
{{3{A}}, {2{B}}}	12'b111111010010

Be generous in {}




Operators 7


Conditional: (? , :)

- $D = S ? B : C;$
 
$$D = \begin{cases} B & \text{if } S=1; \\ C & \text{if } S=0; \end{cases}$$



 - $D = (\{S_1, S_2\} == 2'b00) ? F :$
 $(\{S_1, S_2\} == 2'b01) ? E :$
 $(\{S_1, S_2\} == 2'b10) ? C : B;$
 - $D = (\{S_1, S_2\} == 2'b00) ? F :$
 $(\{S_1, S_2\} == 2'b01) ? E :$
 $(\{S_1, S_2\} == 2'b10) ? C :$
 $(\{S_1, S_2\} == 2'b11) ? B : B;$
- Default



**4-input
Multiplexer
(MUX)**


Operators: All in one

Type of Operators	Symbols					
Concatenate & replicate	{ }	{ { } }				
Unary	!	~	&	^	^~	
Arithmetic	*	/	%			
	+	-				
Logical shift	<<	>>				
Relational	<	<=	>	>=		
Equality	==	!=	===	!==		
Binary bit-wise	&	^	^~			
Binary logical	&&					
Conditional	? :					

Behavioral-Level


Procedure Statements

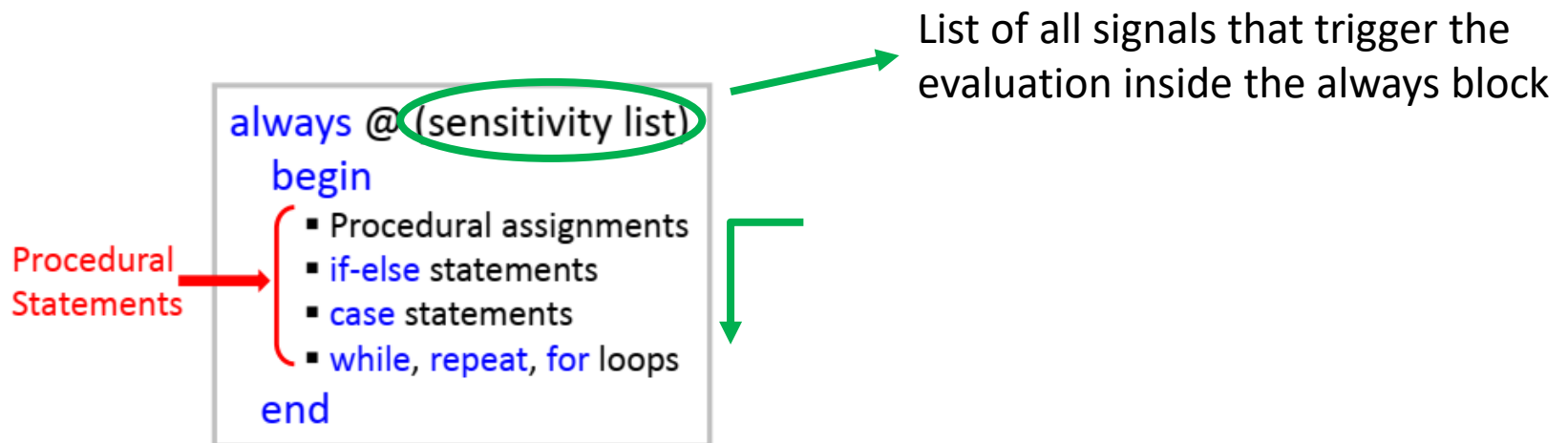- Evaluated in the order in which they appear in the code
 - Sequential
- Should be inside an “always” block
- An “always” block contains one or more procedural statements
- No nesting



Always Block: Structure

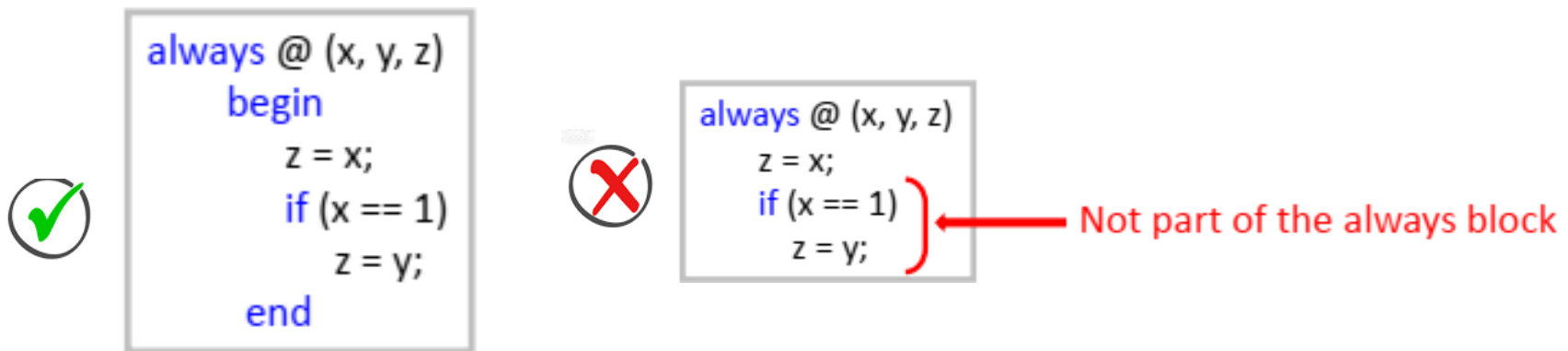- Requires **begin-end** only if there are multiple statements in the block



Always Block Value

- Any signal assigned inside an always block **have to** be a variable of type
 - reg
 - integer
- i.e., value remains unchanged until another procedural assignment updates it

< value> = <expression >

Always Block Value (cont'd)

< value> = <expression >

- *value*
 - reg, integer, real, time
 - A bit-select of the above (e.g., `addr[0]`)
 - A part-select of the above (e.g., `addr[31:16]`)
 - A concatenation of any of the above
- *expression*
 - Any type (register, net) or function
- What happens if the widths do not match?
 - LHS wider than RHS
 - RHS is zero-extended
 - RHS wider than LHS
 - RHS is truncated (Least significant part is kept)


Always Block Value (cont'd)

< value> = <expression >


- What happens if the widths do not match?
 - LHS wider than RHS
 - RHS is zero-extended
 - RHS wider than LHS
 - RHS is truncated (Least significant part is kept)

Always Block: Rule

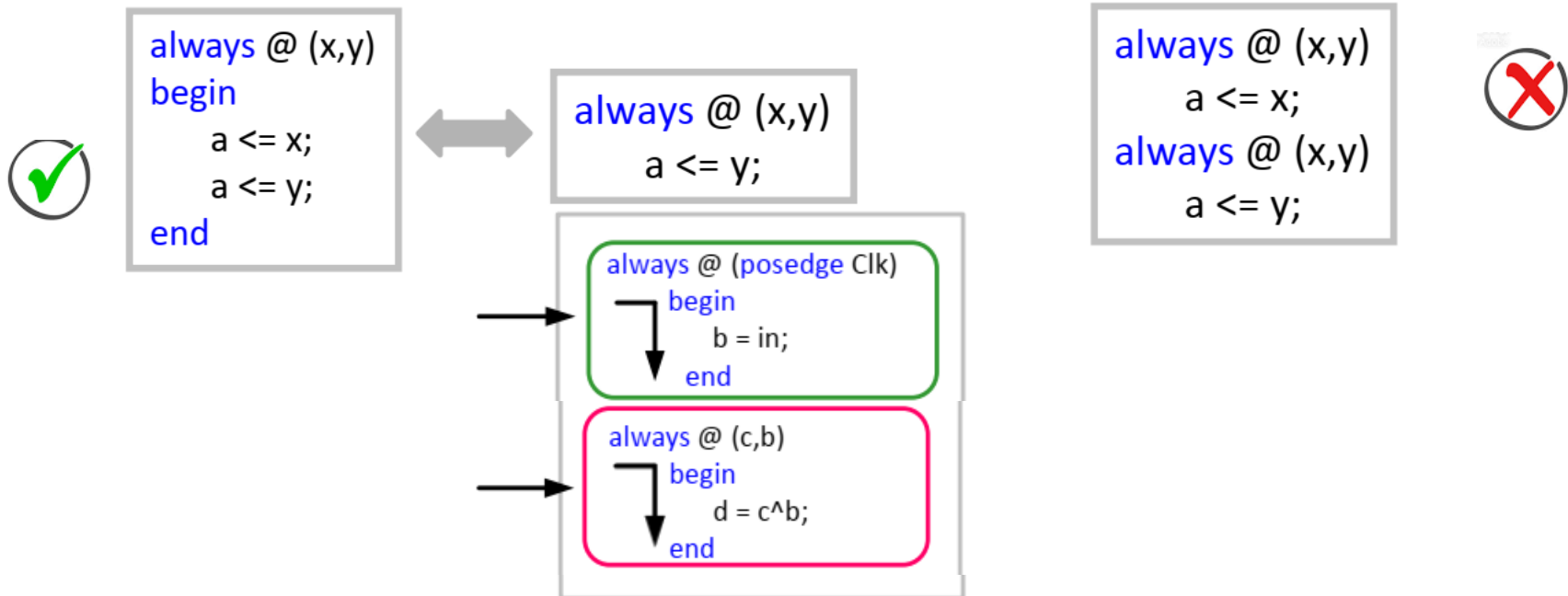- A given variable should **never be assigned** a value in more than one always block
 - Always blocks are concurrent with respect to one another
 - Start from simulation time 0



Procedural Statement Types

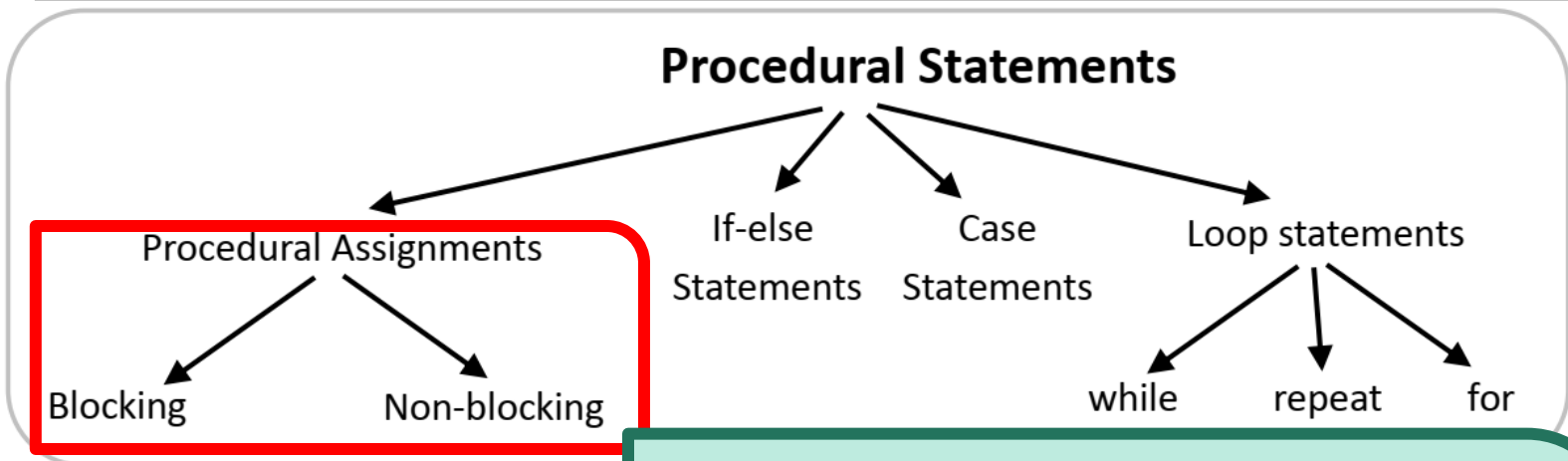


Procedural Assignment

- Assume S=2

Blocking


```
always @ (*)  
begin  
  S = 4;  
  a = S;  
end
```



S=4 & a=4
(sequential)

Non-Blocking

```
always @ (*)  
begin  
  S <= 4;  
  a <= S;  
end
```



S=4 & a=2
(Parallel)

- Evaluated and assigned in a single step
- Sequential nature
- Assignment ordering is important

- Evaluated and assigned in two steps
 - All RHSs are evaluated in parallel
 - Assignment to LHSs are performed together
- They are evaluated all at once
- Assignment ordering is NOT important
- S <=4 and a<=S evaluated in parallel

Procedural Assignment: Sample

- Swap bytes in words



- Evaluated and assigned in a single step
- Sequential nature
- Assignment ordering is important
- Evaluated and assigned in two steps
 - All RHSs are evaluated in parallel
 - Assignment to LHSs are performed together
- They are evaluated all at once
- Assignment ordering is NOT important
- $S \leq 4$ and $a \leq S$ evaluated in parallel

Procedural Assignment: Swap bytes in words

- Which one is correct?



Blocking

```
always @ (*)  
begin  
    B[15:8] = B[7:0];  
    B[7:0] = B[15:8] ;  
end
```

Non-Blocking


```
always @ (*)  
begin  
    B[15:8] <= B[7:0];  
    B[7:0] <= B[15:8] ;  
end
```

Procedural Assignment: Swap bytes in words ?

- Which one is correct?


Blocking
 
```
always @ (*)  
begin  
    B[15:8] = B[7:0];  
    B[7:0] = B[15:8];  
end
```





Non-Blocking
 
```
always @ (*)  
begin  
    B[15:8] <= B[7:0];  
    B[7:0] <= B[15:8];  
end
```





Procedural Assignment: After Synthesis

 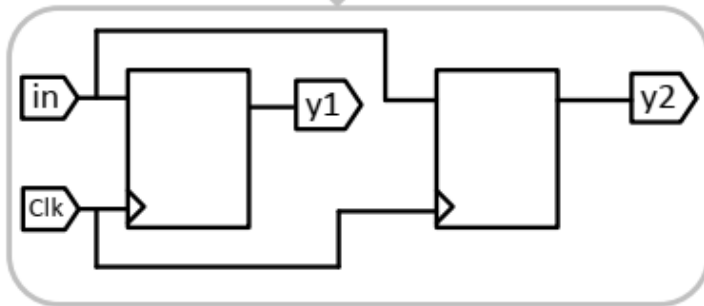
```
always @ (posedge Clk)
begin
    y1 = in;
    y2 = y1 ;
end
```



  
```
always @ (posedge Clk)
begin
    y1 <= in;
    y2 <= y1 ;
end
```


 
```
always @ (*)
begin
    y1 = in;
    y2 = y1 ;
end
```




Procedural Statement Types

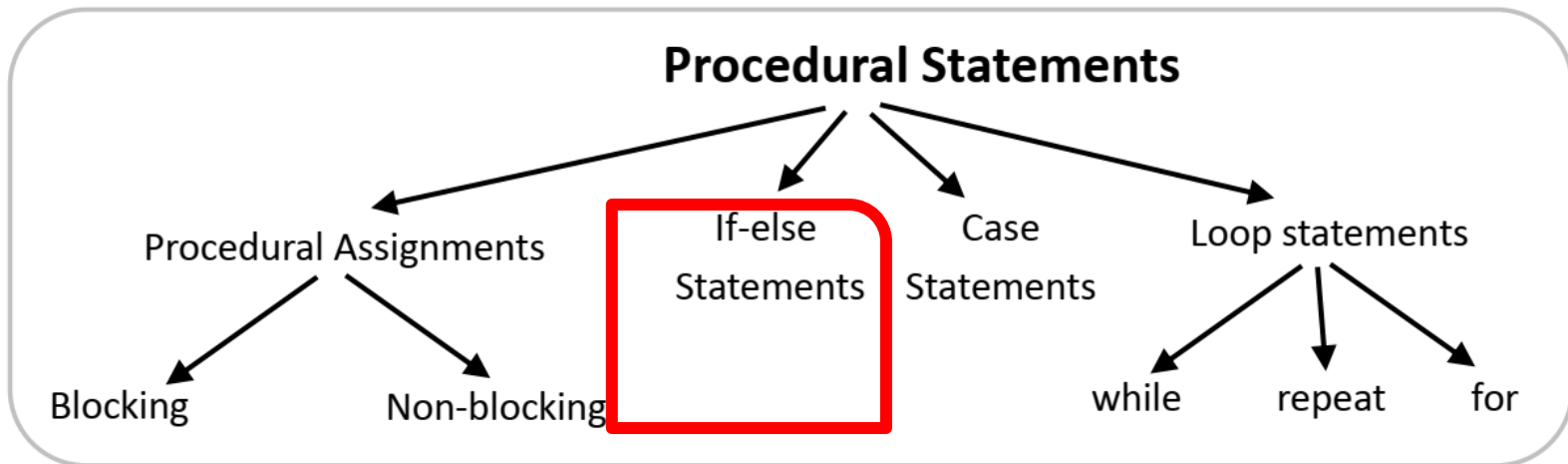

```
If (expression1)  
    statement1;  
else if (expression2)  
    statement2;  
else  
    statement3;
```

Single statement no need for **begin-end**
Multiple statements, **begin-end** is needed

Procedural Statement: If-else Sample

 


```
module Mux21 (in1, in2, s, out)
  input in1, in2, s;
  output reg out;

  always @ (in1, in2, s)
    if (s==0)
      out = in1;
    else
      out = in2;
endmodule
```



```
module Mux21 (in1, in2, s, out)
  input in1, in2, s;
  output reg out;
  always @ (in1, in2, s)
    begin
      out = in1;
      if (s==1)
        out = in2;
    end
endmodule
```

Procedural Statement Types

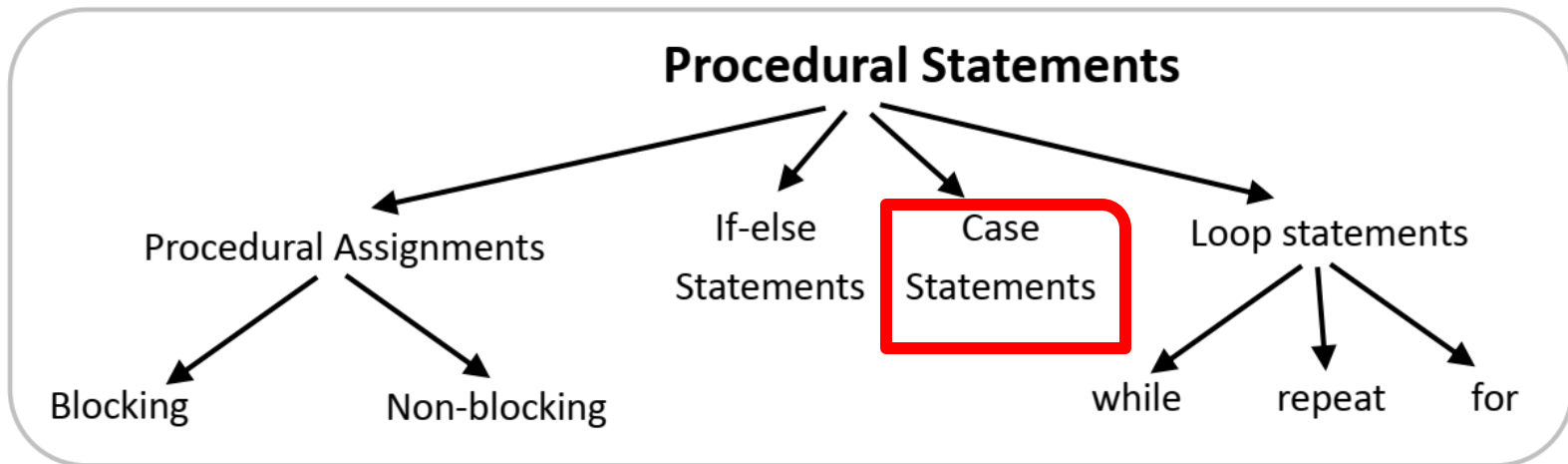

case (expression)

alternative1: statement1;

alternative2: **begin**

statement2;

end


default: statementn;

endcase

Single statement no need for **begin-end**

Multiple statements, **begin-end** is needed

 Procedural Statement: Case Statement Sample



```
module Mux21 (in1, in2, s, out)
  input in1, in2, s;
  output reg out;

  always @ (in1, in2, s)
    case (s)
      1'b0: out = in1;
      1'b1: out = in2;
    endcase
endmodule
```



```
module Mux21 (in1, in2, s, out)
  input in1, in2, s;
  output reg out;

  always @ (in1, in2, s)
    case (s)
      1'b0: out = in1;
      default: out = in2;
    endcase
endmodule
```

Procedural Statement: Case Statement: don't care

In case statements, each alternative is compared for an exact match
Synthesis tools are only concerned about matching of "0" and "1" while
"Z" and "X" are not important

If "X" or "Z" are needed to be added, `casex` is used (`casex` is synthesizable)

In fact `casex` treats them as don't care

w3	w2	w1	w0	y1	y0	f
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1



```
module Priority (W, Y, f)
  input [3:0] W;
  output reg [1:0] Y;
  output f;
  assign f = (W!=0)
  always @ (W)
    begin
      casex (W)
        'b1xxx: Y = 3;
        'b01xx: Y = 2;
        'b001x: Y = 1;
        default: Y = 0;
      endcase
    end
endmodule
```

Procedural Statement: Case Statement: don't care


casez allows use of wildcard “?” character for don't

w3	w2	w1	w0	y1	y0	f
0	0	0	0	d	d	0
0	0	0	1	0	0	1
0	0	1	X	0	1	1
0	1	X	X	1	0	1
1	X	X	X	1	1	1



```
module Priority (W, Y, f)
  input [3:0] W;
  output reg [1:0] Y;
  output f;
  assign f = (W!=0)
  always @ (W)
    begin
      casez (W)
        'b1??? : Y = 3;
        'b01?? : Y = 2;
        'b001? : Y = 1;
        default: Y = 0;
      endcase
    end
endmodule
```

Procedural Statement Types

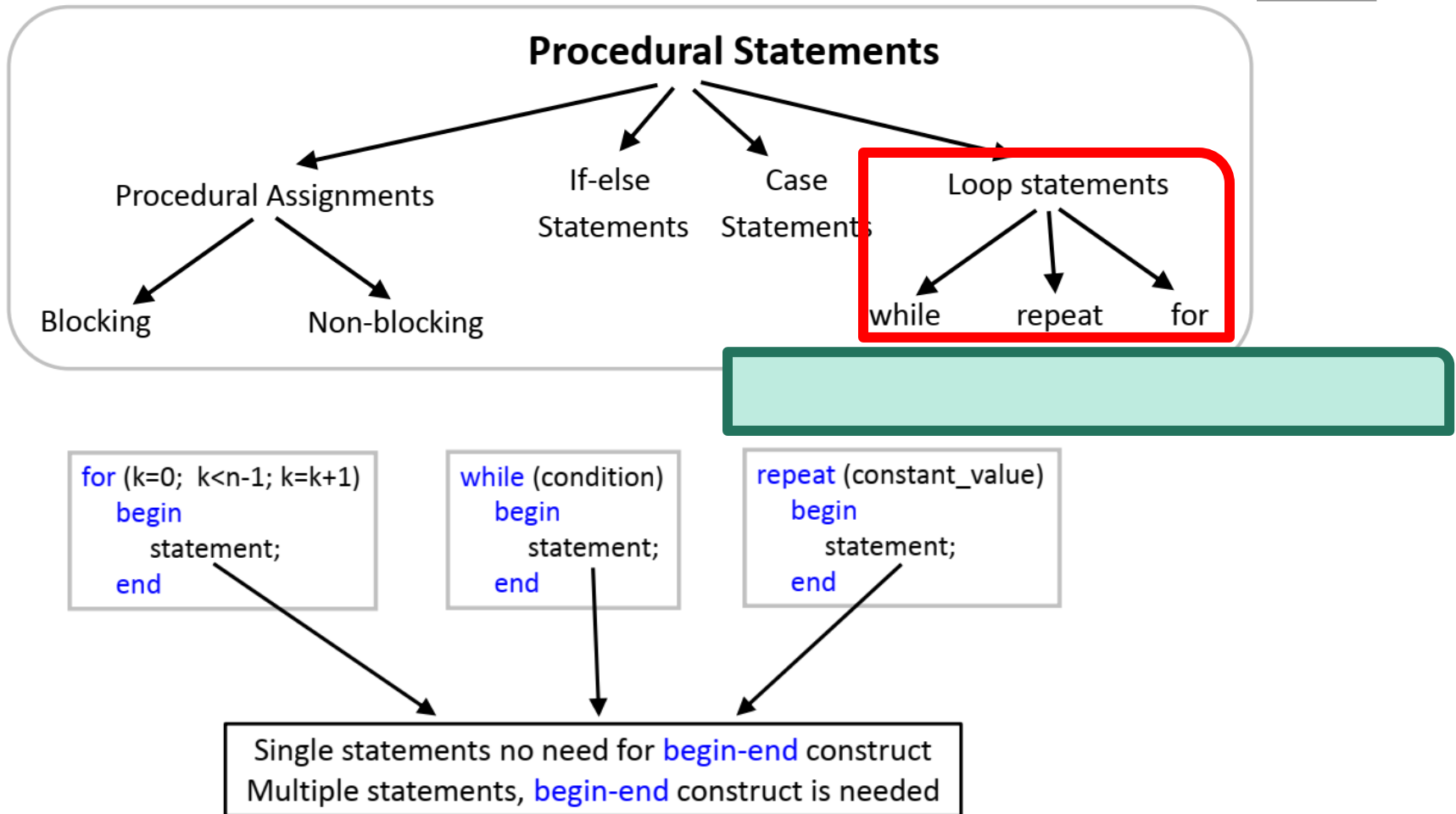

Sample 1:

How to implement a function like: $F(a,b,c,d) = ab + cd$?

```
module F (input a,b,c,d, output
reg out);
always @(a,b,c,d)
begin
    out = (a & b) | (c & d);
end
endmodule
```

```
module F (input a,b,c,d, output
reg out);
always @(*)
begin
    out = (a & b) | (c & d);
end
endmodule
```

Write a testbench for “F” module


```
module testbench;
reg a, b, c, d;
wire out;
F inst (a, b, c, d, out);
initial
begin
{a,b,c,d} = 4'b0001;
#5
{a,b,c,d} = 4'ha;
endmodule
```


Sample 2:

N-bit ripple carry adder

```
module RippleCarryAdder1 (Cin, X, Y, S, Cout)
  parameter n = 4;
  input Cin;
  input [n-1:0] X, Y;
  output reg [n-1:0] S;
  output reg Cout;
  reg [n:0] C;
  integer k;
  always @(X, Y, Cin)
  begin
    C[0] = Cin;
    for (k=0;k<=n-1;k=k+1)
      begin
        S[k] = X[k] ^ Y[k] ^ C[k];
        C[k+1] = (X[k] & Y[k])
          | (X[k] & C[k]) | (Y[k] & C[k]);
      end
    Cout = C[n];
  end
endmodule
```

Sequential
Structure

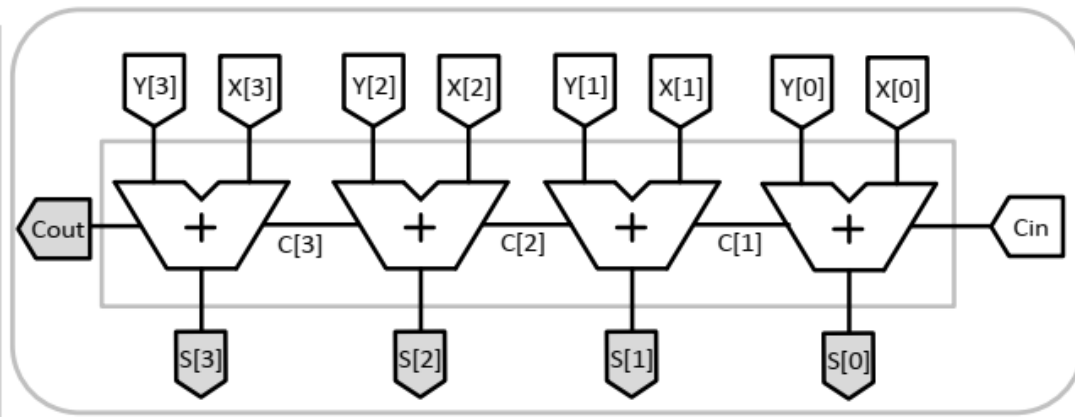

Breaking one statement in two lines is allowed!

Thank You

