




Digital System Design

Hajar Falahati

hfalahati@ipm.ir
hfalahati@ce.sharif.edu

RTL

 - Functional level
- Describe a design architecture in sufficient detail that a synthesis tool can construct the circuit
- RTL is the closet one to the actual hardware implementation



Operators: All in one

Type of Operators	Symbols
Concatenate & replicate	{ } { { } }
Unary	! ~ & ^ ^~
Arithmetic	* / % + -
Logical shift	<< >>
Relational	< <= > >=
Equality	== != === !==
Binary bit-wise	& ^ ^~
Binary logical	&&
Conditional	? :

Outline


- How to implement a combinational logic at behavioral-level?
- How to implement a sequential logic at behavioral-level?



Combinational Logic

Logic Circuits

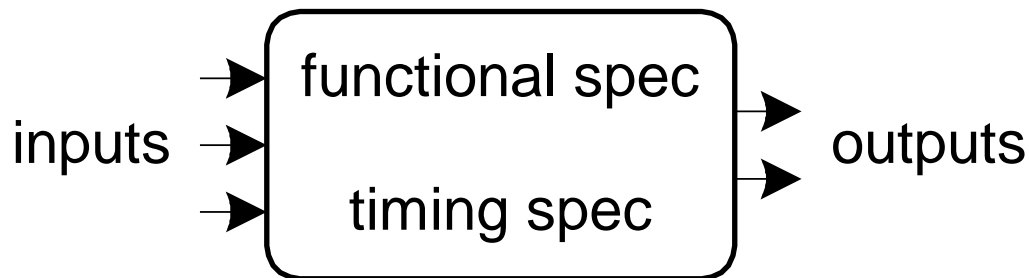- A logic circuit is composed of:
 - Inputs
 - Outputs
- *Functional specification* (describes relationship between inputs and outputs)
- *Timing specification* (describes the delay between inputs changing and outputs responding)



Combinational Logic & Verilog

- Use **always block** + “**blocking**” assignments
 - Normally for high-complexity Comb. Logic
 - When output depends on several conditions, which requires if-else

Which one is correct?

- Implement an accumulator

```
always @ (*)  
begin  
  for (k=0; k<4; k=k+1)  
    Count = Count + k;  
end
```

```
always @ (*)  
begin  
  for (k=0; k<4; k=k+1)  
    Count <= Count + k;  
end
```



Let's Check Their Behavior?

```
always @ (*)  
begin  
  for (k=0; k<4; k=k+1)  
    Count = Count + k;  
end
```

```
always @ (*)  
begin  
  for (k=0; k<4; k=k+1)  
    Count <= Count + k;  
end
```



Count = Count + 0;
Count = 0 + 1;
Count = 0 + 1 + 2;
Count = 0 + 1 + 2 + 3;
Result: Count = 6



Count <= Count + 0;
Count <= Count + 1;
Count <= Count + 2;
Count <= Count + 3;
Result: Count = 3

Use only blocking assignments for
combinational logic

In multiple concurrent non-blocking assignments
to a variable
the last one executes

An **always** Block Does **NOT** Always Remember

- This statement describes what happens to the signal **result**
 - When **inv** is 1, **result** is \sim **data**
 - When **inv** is not 1, **result** is **data**
- The circuit is combinational (no memory)

```
module comb (input      inv,
             input [3:0] data,
             output reg [3:0] result);

    always @ (inv, data)           // trigger with inv, data
    if (inv) result = ~data;       // result is inverted data
    else    result = data;         // result is data
endmodule
```

Sample 1

- Implement a 2-1 MUX



Sample 1

Implement a 2-1 MUX

```
module Mux (a,b, sel, result)
    output reg [31:0] result;
    input [31:0] a, b;
    input sel,

    always @ (a, b, sel) // trigger with a, b, sel
        if (sel) result = a; // result is a
        else result = b; // result is b

endmodule
```

Sample 2

- Implement a full adder



Sample 2

- Implement a full adder

```
module Adder (x, y, S, C)
  input x,y;
  output S,C;
  reg S, C;
  always @ (x, y)
    begin
      S = x ^ y;
      C = x & y;
    end
endmodule
```


Summary

- An **always** block defines a **combinational logic** if:
 - All outputs are always (**continuously**) updated
 1. All right-hand side signals are in the sensitivity list
 - You can use **always @*** for short
 2. All left-hand side signals get assigned in every possible condition of **if .. else** and **case** blocks
- It is easy to make mistakes and unintentionally describe memorizing elements (latches)
 - Vivado will most likely warn you.
 - Make sure you check the warning messages
- **Always** blocks allow powerful combinational logic statements
 - **if .. else**
 - **case**

Sequential Logic

Combinational + Memory = Sequential

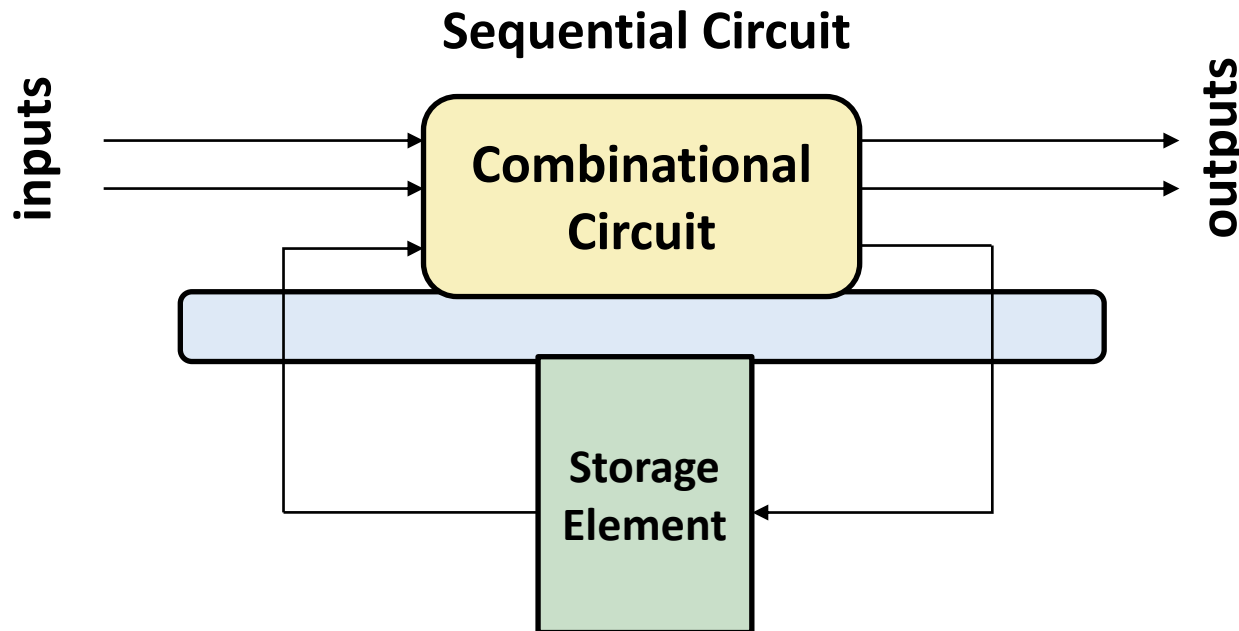- Sequential logic can **only** be realized using an **always block**
- When using the **always block** for the sequential Logic, “**Non-blocking**” assignments are used



Sequential Circuits in Verilog

- Define blocks that have memory

- *Flip-Flops*

- *Positive edge of the clock (posedge)*

- *Negative edge of the clock (negedge)*

- *Latches*

- Sensitive to level of the signal

- *Finite State Machines*

→ `always @ (posedge Clk)`

→ `always @ (negedge Clk)`

- Sequential Logic state transition is triggered by a 'CLOCK' event

Sample: D Flip-Flop

- `posedge` defines a rising edge (transition from 0 to 1).
- Statement executed when the `clk` signal rises (`posedge` of `clk`)
- Once the `clk` signal rises: the value of `d` is copied to `q`

```
module flop(input          clk,
            input  [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <= d;                // pronounced "q gets d"

endmodule
```

Sample: D Flip-Flop

- Only procedural statements are used within an always block
- “Non-blocking” assignments

```
module flop(input          clk,
            input    [3:0] d,
            output reg [3:0] q);

    always @ (posedge clk)
        q <= d;                // pronounced “q gets d”

endmodule
```

Sample: D Flip-Flop

- Assigned variables need to be declared as `reg`

```
module flop(input          clk,
            input          [3:0] d,
            output reg [3:0] q);


    always @ (posedge clk)
        q <= d;                // pronounced "q gets d"

endmodule
```

Sample 1: D Flip-Flop

- **Reset** signals are used to **initialize** the hardware to a known state
 - Usually activated **at system start** (on power up)
- **Asynchronous Reset**
 - The reset signal is sampled **independent** of the clock
 - Reset gets the highest priority
 - Sensitive to **glitches**, may have **metastability** issues
- **Synchronous Reset**
 - The reset signal is sampled **with respect to the clock**
 - The reset **should be active long enough** to get sampled at the clock edge
 - Results in **completely synchronous circuit**

D Flip-Flop with Asynchronous Reset

 

D Flip-Flop with Asynchronous Reset

- In this example: two events can trigger the process:
 - A *rising edge* on clk
 - A *falling edge* on reset

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0)    q <= 0;    // when reset
        else                q <= d;    // when clk
    end
endmodule
```

 

D Flip-Flop with Asynchronous Reset

- First **reset** is checked: if **reset** is 0, **q** is set to 0.
 - This is an **asynchronous** reset as the reset can happen **independently** of the clock (on the negative edge of reset signal)
- If there is no reset, then regular assignment takes effect

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);

    always @ (posedge clk, negedge reset)
    begin
        if (reset == 0)    q <= 0;    // when reset
        else                q <= d;    // when clk
    end
endmodule
```

D Flip-Flop with Synchronous Reset



D Flip-Flop with Synchronous Reset


- The process is sensitive to only **clock**
 - Reset **happens only** when the **clock rises**. This is a **synchronous** reset

```
module flop_ar (input          clk,
                input          reset,
                input    [3:0] d,
                output reg [3:0] q);


    always @ (posedge clk)
    begin
        if (reset == 0)    q <= 0;    // when reset
        else                q <= d;    // when clk
    end
endmodule
```

NOTE !

- Use reset-able FFs only where needed
 - FFs are a little larger and higher power
 - Requires the global routing of the high-fanout reset signal

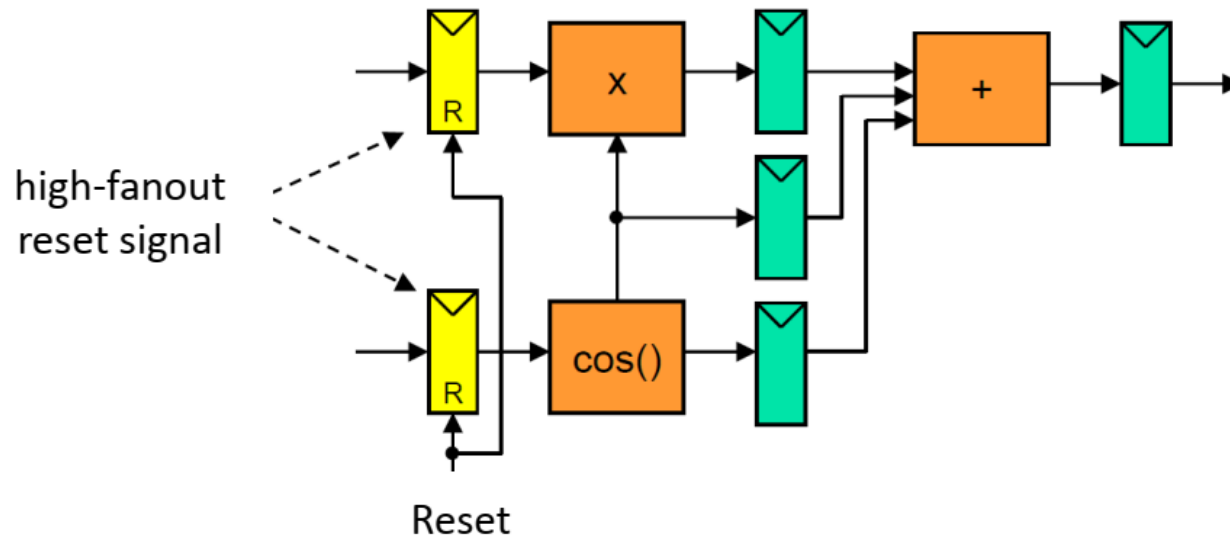

Sample2: D- Latch

 

Sample2: D- Latch

```
module flop_ar (input          clk,  
                input    [3:0] d,  
                output reg [3:0] q);  
  
    always @ (clk, d)  
        if (clk)    q <= d;    // Latch is transparent when  
                                // clock is 1  
  
endmodule
```

An **always** Block Remember



- This statement describes what happens to signal **q**
- ... but what happens when the clock is not rising?
- The value of **q** is preserved (remembered)

```
module flop (input          clk,
              input          [3:0] d,
              output reg [3:0] q);

    always @ (posedge clk)
        begin
            q <= d; // when clk rises copy d to q
        end
endmodule
```



Shift Register
  
```
wire [n:0] d;  
reg [n:0] q;  
...  
always @ (posedge Clk)  
    q<=d;
```





Memory

  - A two-dimensional array of bits
- Declared in Verilog as a two-dimensional variable (reg)



- 3-D memory

  

Which one is correct?

- Implement a shift register

```
always @ (A)
begin
  for (k=0; k<3;k=k+1)
    A[k]=A[k+1];
  A[3] = A[0];
end
```

```
always @ (A)
begin
  for (k=0; k<3;k=k+1)
    A[k]<=A[k+1];
  A[3] <= A[0];
end
```




Which one is correct?

- Implement a shift register



```
always @ (A)
begin
  for (k=0; k<3;k=k+1)
    A[k]=A[k+1];
  A[3] = A[0];
end
```
 
```
always @ (A)
begin
  for (k=0; k<3;k=k+1)
    A[k]<=A[k+1];
  A[3] <= A[0];
end
```



Thank You

