



# Digital System Design

---


Hajar Falahati

[hfalahati@ipm.ir](mailto:hfalahati@ipm.ir)  
[hfalahati@ce.sharif.edu](mailto:hfalahati@ce.sharif.edu)
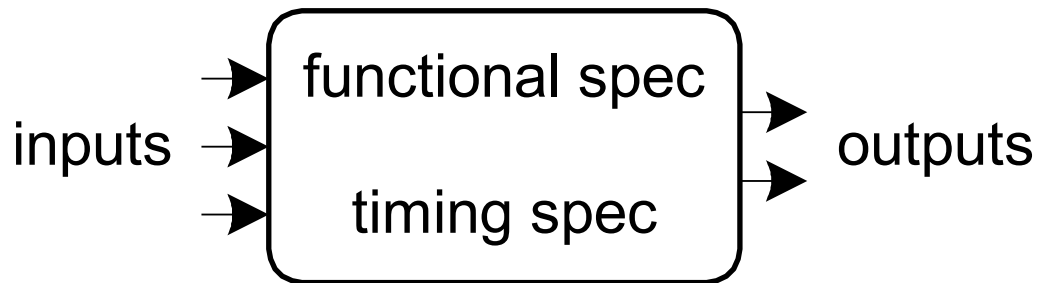
# Specifications



---

- A logic circuit is composed of:
  - Inputs
  - Outputs
- *Functional specification* (describes relationship between inputs and outputs)
- *Timing specification* (describes the delay between inputs changing and outputs responding)



# Sequential Timing Summary

$t_{ccq} / t_{pcq}$	clock-to-q delay (contamination/propagation)
$t_{cd} / t_{pd}$	combinational logic delay (contamination/propagation)
$t_{setup}$	time that FF inputs must be stable before next clock edge
$t_{hold}$	time that FF inputs must be stable after a clock edge
$T_c$	clock period

  

# Outline

---


- Dataflow
- Gate-level



# Concurrent Statement



---

# Recall: Verilog Statement

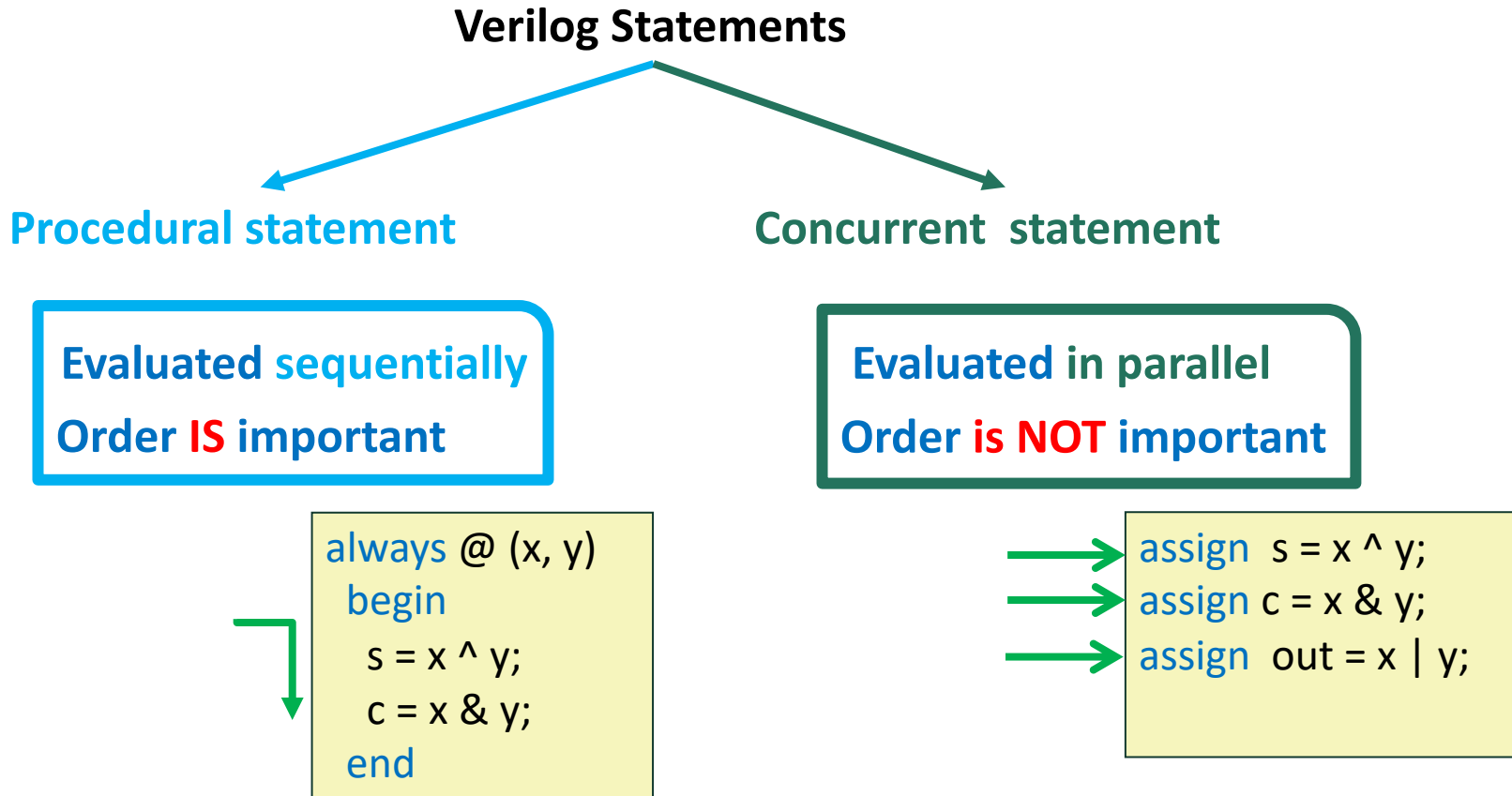
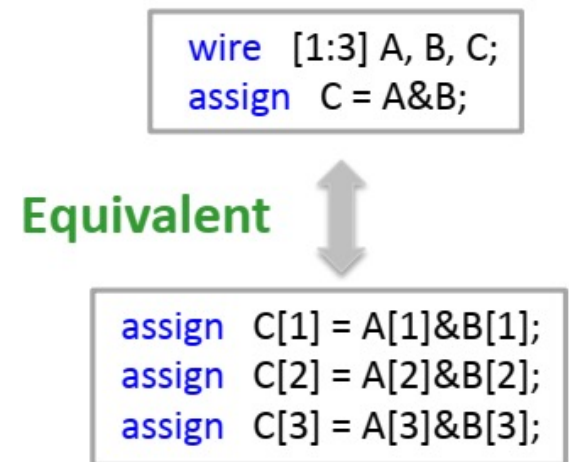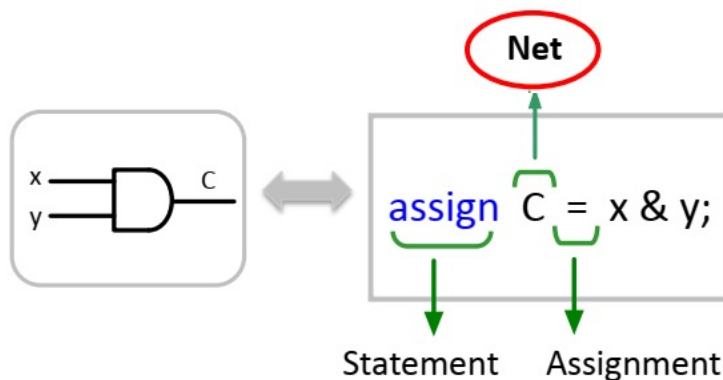
# Concurrent Statement

- Evaluated in parallel
- Each statement describes part of the circuit, thus, it is concurrent
- Realized as **connection** or **wire** in the design
- **Format**



- **assign** used only for nets (to be synthesizable)

# Sample: Full Adder

X	Y	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	0	1

```

module Adder (Cin, x, y, S, Cout)
  input x, y, Cin;
  output S, Cout;
  wire S, Cout;

  assign S = x ^ y ^ Cin;

  assign Cout = (x & y) | (x & Cin) | (y & Cin);

endmodule

```


```

module Adder (Cin, x, y, S, Cout)
  input x, y, Cin;
  output S, Cout;
  wire S, Cout;

  assign {Cout, S} = x + y + Cin;


endmodule

```

 



# Sample: 4-1 MUX

 


s1	s0	out
0	0	I0
0	1	I1
1	0	I2
1	1	I3


```

module mux4_1(out,i0,i1,i2, i3,s0,s1);
  input    i0,i1,i2,i3,s0,s1;
  output   out;
  wire     s1n,s0n,y0,y1,y2,y3;
  assign out = (~s1 & ~s0 & i0) |
               (~s1 &  s0 & i1) |
               ( s1  & ~s0 & i2) |
               ( s1  &  s0 & i3);
endmodule

```

 

# Sample: 4-1 MUX

 

```
module mux4_1(out,i0,i1,i2,i3,s0,s1);
```


```
    input  i0,i1,i2,i3,s0,s1;
```

```
    output out;
```

```
    assign out = s1? (s0 ? i3:i2) : (s0 ?  
i1:i0);
```

```
endmodule
```

s1	s0	out
0	0	I0
0	1	I1
1	0	I2
1	1	I3

 

# Dataflow: Delay

---

- Delay can be used with continuous assignments by using the “#” sign
  - 2 time unit of delay on wire S
  - 5 time units of delay for AND gate
  - Any change in x or y reflects on S after ? time unit delay

```
wire #2 S;  
assign #5 S = x&y;
```

# Dataflow: Delay

---

- Delay can be used with continuous assignments by using the “#” sign
  - 2 time unit of delay on wire S
  - 5 time units of delay for AND gate
  - Any change in x or y reflects on S after 7 time unit delay

```
wire #2 S;  
assign #5 S = x&y;
```

# Delays at Dataflow Level

---

- Regular assignment delay

```
assign #10 out = in1 & in2;
```

- Implicit continuous assignment delay

```
wire #10 out = in1 & in2;
```

```
//same as  
wire out;  
assign #10 out = in1 & in2;
```

- Net declaration delay


```
wire #10 out ;
```

```
assign out = in1 & in2;
```

# Gate


---

# Primitive Gates: and, nand (cont'd)

 

and	$i_1$			
	0	1	x	z
$i_2$	0	0	0	0
	1	0	1	x
	x	0	x	x
	z	0	x	x


**and g0 (out,  $i_1$ ,  $i_2$ )**

 

nand	$i_1$			
	0	1	x	z
$i_2$	0	1	1	1
	1	1	0	x
	x	1	x	x
	z	1	x	x

**nand g1 (out,  $i_1$ ,  $i_2$ )**


# Primitive Gates: or, nor (cont'd)

 

		$i_1$			
$i_2$	or	0	1	x	z
	0	0	1	x	x
	1	1	1	1	1
	x	x	1	x	x
	z	x	1	x	x

or g0 (out,  $i_1$ ,  $i_2$ )

or (out,  $i_1$ ,  $i_2$ )

 


		$i_1$			
$i_2$	nor	0	1	x	z
	0	1	0	x	x
	1	0	0	0	0
	x	x	0	x	x
	z	x	0	x	x

nor g1 (out,  $i_1$ ,  $i_2$ )

nor (out,  $i_1$ ,  $i_2$ )




# Primitive Gates: xor, xnor (cont'd)

 

		$i_1$			
xor		0	1	x	z
$i_2$	0	0	1	x	x
	1	1	0	x	x
	x	x	x	x	x
	z	x	x	x	x

xor g0 (out,  $i_1$ ,  $i_2$ )


 


		$i_1$			
xnor		0	1	x	z
$i_2$	0	1	0	x	x
	1	0	1	x	x
	x	x	x	x	x
	z	x	x	x	x

xnor g1 (out,  $i_1$ ,  $i_2$ )


# Gate-Level Design Sample ?

---

 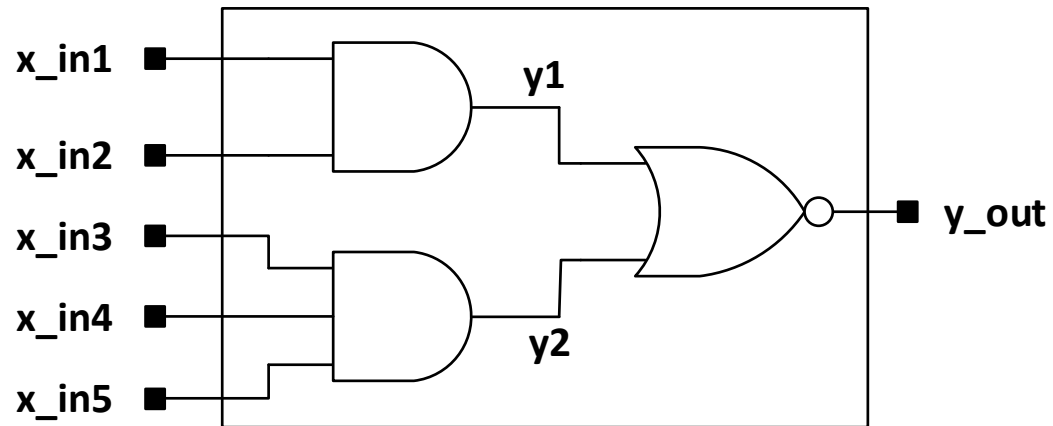


# Sample: Step1

---

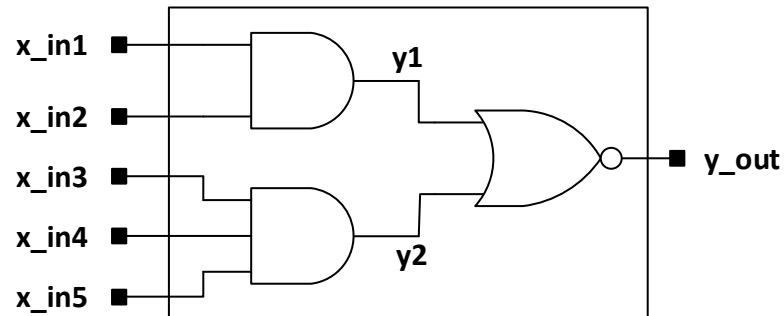


```
module gateLevelSample(y_out,x_in1,x_in2,x_in3,x_in4,x_in5);  
endmodule
```

# Sample: Step2

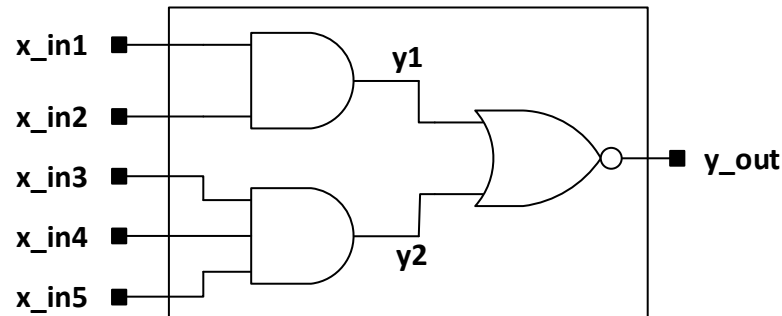


```
module gateLevelSample (y_out,x_in1,x_in2,x_in3,x_in4,x_in5) ;  
    output y_out;  
    input  x_in1 , x_in2 , x_in3 , x_in4 , x_in5;  
  
endmodule
```

# Sample: Step3

 


```
module gateLevelSample (y_out,x_in1,x_in2,x_in3,x_in4,x_in5) ;  
    output y_out;  
    input  x_in1 , x_in2 , x_in3 , x_in4 , x_in5;  
  
    wire  y1 , y2;  
  
endmodule
```

# Sample: Step4

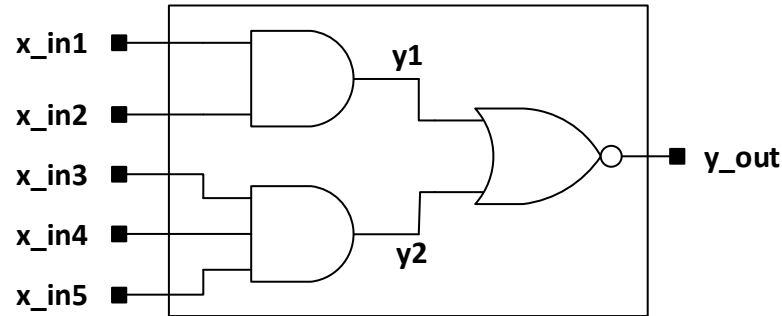


```
module gateLevelSample (y_out,x_in1,x_in2,x_in3,x_in4,x_in5);  
    output y_out;  
    input  x_in1 , x_in2 , x_in3 , x_in4 , x_in5;  
  
    wire   y1 , y2;  
  
    and    (y1 , x_in1 , x_in2);  
  
endmodule
```

# Sample: Step5

 

```
module gateLevelSample (y_out,x_in1,x_in2,x_in3,x_in4,x_in5);  
    output y_out;  
    input  x_in1 , x_in2 , x_in3 , x_in4 , x_in5;  
  
    wire   y1 , y2;  
  
    and     (y1 , x_in1 , x_in2);  
    and     (y2 , x_in3 , x_in4 , x_in5);  
endmodule
```


# Sample: Step6

 

```
module gateLevelSample (y_out,x_in1,x_in2,x_in3,x_in4,x_in5);  
    output y_out;  
    input  x_in1 , x_in2 , x_in3 , x_in4 , x_in5;  
  
    wire   y1 , y2;  
  
    and     (y1 , x_in1 , x_in2);  
    and     (y2 , x_in3 , x_in4 , x_in5);  
    nor     (y_out , y1 , y2);  
endmodule
```



# Sample: Is this code correct?

 

```
module gateLevelSample (y_out,x_in1,x_in2,x_in3,x_in4,x_in5);  
    output y_out;  
    input  x_in1 , x_in2 , x_in3 , x_in4 , x_in5;  
  
    wire  y1 , y2;  
  
    nor    (y_out , y1 , y2);  
    and    (y1 , x_in1 , x_in2);  
    and    (y2 , x_in3 , x_in4 , x_in5);  
endmodule
```



# Design a 1-bit Full Adder in Gate Level

---

- Design a 1-bit half adder
- Design a 1-bit full adder
- **xor gate**
  - delay: 3
- **and gate**
  - delay: 1
- **or gate**
  - delay: 2
- **``timescale 1ns/100ps`**



# FA: Gate-level Description

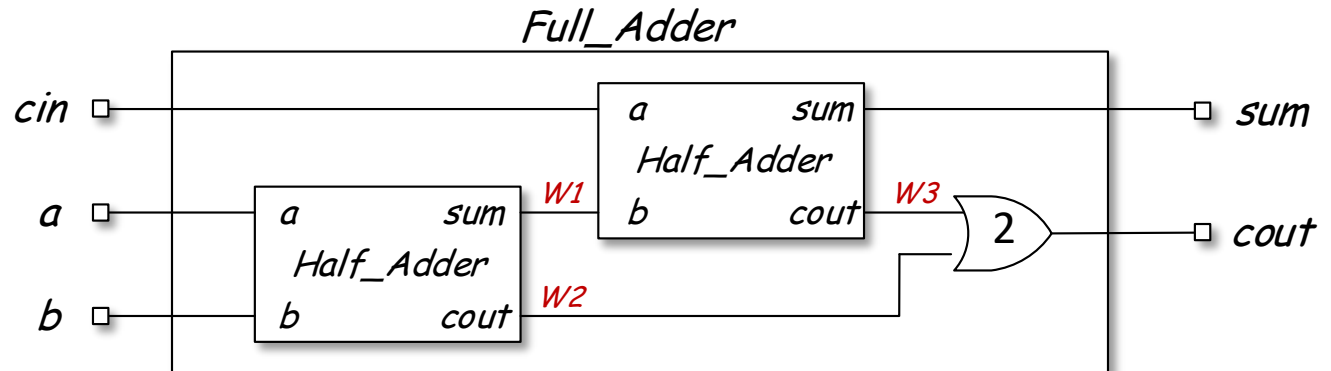 




# FA: Design Block

```
module Half_Adder(sum , cout , a , b);  
    input      a , b;  
    output     sum , cout;  
  
    xor #3(sum , a , b);  
    and #1(cout , a , b);  
endmodule
```

- xor gate
  - delay: 3
- and gate
  - delay: 1
- or gate
  - delay: 2
- `timescale  
1ns/100ps

```
module Full_Adder(sum , cout , a , b , c_in);  
    input      a , b , C_in;  
    output     sum , cout;  
    wire      w1 , w2 , w3;  
  
    Half_Adder M1(w1 , w2 , a , b);  
    Half_Adder M1(sum , w3 , c_in , w1);  
    or #2 (cout , w2 , w3);  
endmodule
```

# FA: Delay analysis

 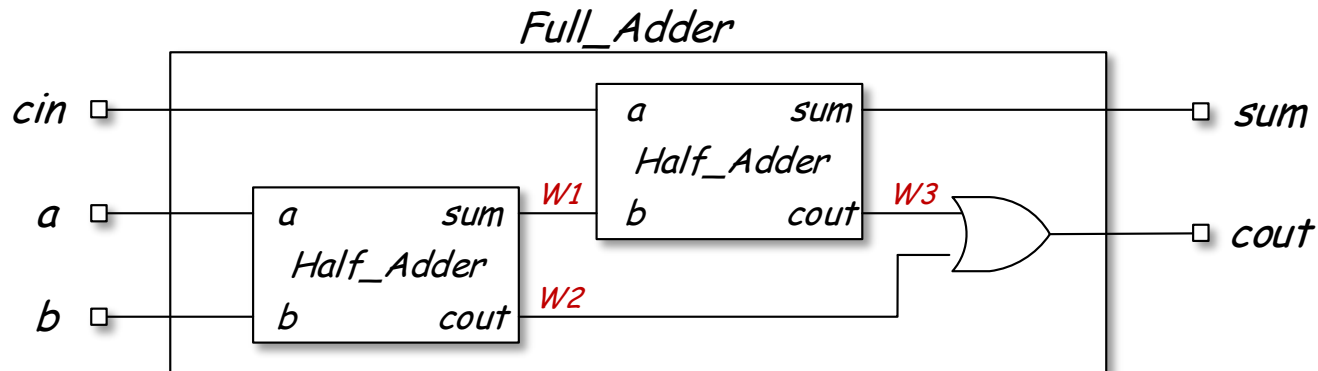 

# Design a 3-input XOR

---

- **nand gate**

- Tplh: 2, 4, 6
- Tphl: 3, 5, 7

- **not gate**

- Tplh: 1, 3, 5
- Tphl: 2, 4, 6

- **``timescale 1ns/100ps`**



# 3-input XOR: Truth Table

---

a	b	c	y	
0	0	0	0	
0	0	1	1	$\sim a \sim b c$
0	1	0	1	$\sim a b \sim c$
0	1	1	0	
1	0	0	1	$a \sim b \sim c$
1	0	1	0	
1	1	0	0	
1	1	1	1	$abc$

$\sim a \sim b c + \sim a b \sim c + a \sim b \sim c + abc$

# 3-input XOR: Functionality

---

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$\sim a \sim b c + \sim a b \sim c + a \sim b \sim c + a b c$$

$$\sim a ( \sim b c + b \sim c ) + a ( \sim b \sim c + b c )$$

$$\sim a ( b \text{ xor } c ) + a ( b \text{ xnor } c )$$



# 3-input XOR: Nand-Not Expression

a	b	c	y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1


$$\sim a \sim b c + \sim a b \sim c + a \sim b \sim c + a b c$$

$$A + B == \sim(\sim A . \sim B)$$

$$\sim( \sim(\sim a \sim b c) . \sim(\sim a b \sim c) . \sim(a \sim b \sim c) . \sim(a b c) )$$

# 3-input XOR: Gate-level Description

---

 


# 3-input XOR: Design Block

```
`timescale 1ns/100ps
module xor3(y, a, b, c);
  input  a, b, c;
  output y;
  wire im1, im2, im3, im4;
  wire a_, b_, c_;
```

```
  not #(1:3:5, 2:4:6)
    (a_, a), (b_, b), (c_, c);
  nand #(2:4:6, 3:5:7)
    (im1, a_, b_, c), (im2, a_, b, c_);
  (im3, a, b_, c_), (im4, a, b, c);
```
 
```
  nand #(2:4:6, 3:5:7) (y, im1, im3, im3, im4);
endmodule
```



- **nand gate**
  - Tplh: 2, 4, 6
  - Tphl: 3, 5, 7
- **not gate**
  - Tplh: 1, 3, 5
  - Tphl: 2, 4, 6
- **`timescale**  
1ns/100ps

# Sample 4



- **and gate**

- Tplh: 2
- Tphl: 4

- **or gate**

- Tplh: 3
- Tphl: 5

- ``timescale 1ns/100ps`

  

# Sample 4: Design Block

```
`timescale 1ns/100ps

module sample2(y, a, b, c);
    input      a, b, c;
    output out;
    wire im1, im2, im3;

    and #(2,4)
        (im1, a, b),
        (im2, b, c),
        (im3, a, c);
    or #(3,5) (y, im1, im2, im3);

endmodule
```


- **and gate**

- Tplh: 2
- Tphl: 4

- **or gate**

- Tplh: 3
- Tphl: 5

- **`timescale 1ns/100ps**

 

# Multiple instantiations

---

## Array of gate instances

```
wire [7:0] OUT, IN1, IN2;  
nand n0(OUT[0], IN1[0],IN2[0]);  
nand n1(OUT[1], IN1[1],IN2[1]);  
nand n2(OUT[2], IN1[2],IN2[2]);  
nand n3(OUT[3], IN1[3],IN2[3]);  
nand n4(OUT[4], IN1[4],IN2[4]);  
nand n5(OUT[5], IN1[5],IN2[5]);  
nand n6(OUT[6], IN1[6],IN2[6]);  
nand n7(OUT[7], IN1[7],IN2[7]);
```


```
wire [7:0] OUT, IN1, IN2;  
nand n[7:0] (OUT, IN1,IN2);
```

# Modeling

---
 
# Using sub-circuits


- A design can use multiple submodules or a module multiple times
- Using a module in another is called “**instantiation**”
- **Top-level module**: the module that has not been instantiated
- To use a module inside another, it should be explicitly instantiated




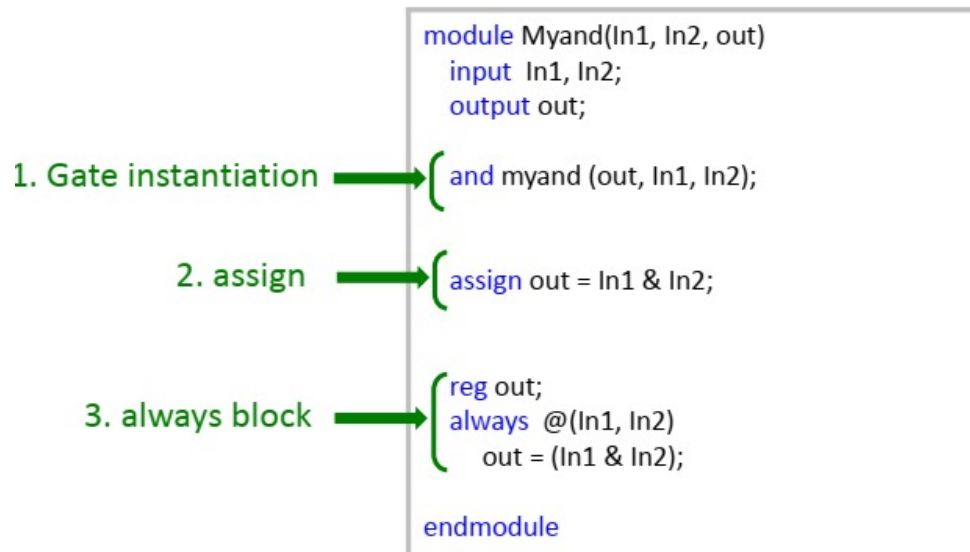
# Using modules

- There are some built-in primitive logic gates in Verilog that can be instantiated
  - Built-in primitives means there is no need to define a module for these gates
  - and, or, nor, ....



# Thank You

---

