




Digital System Design

Hajar Falahati

hfalahati@ipm.ir
hfalahati@ce.sharif.edu


Abstraction Levels

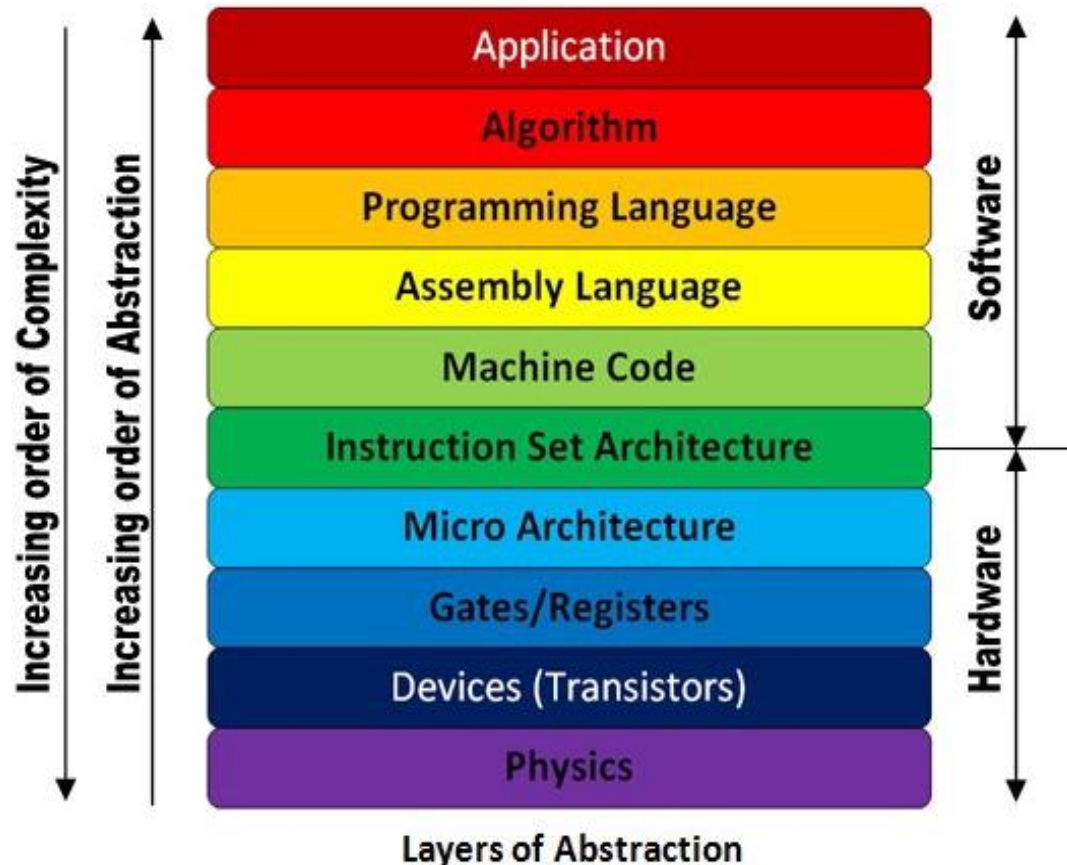- To comprehend these complicated systems





Design Approaches

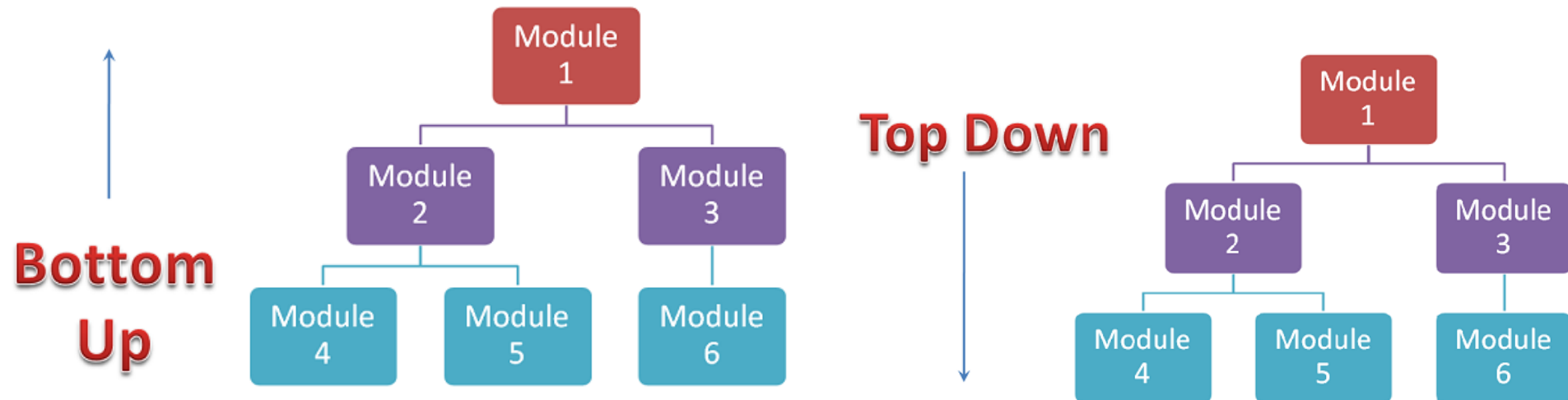- Piecing together of systems to give rise to more complex systems
- More optimized
- More realistic



Modeling

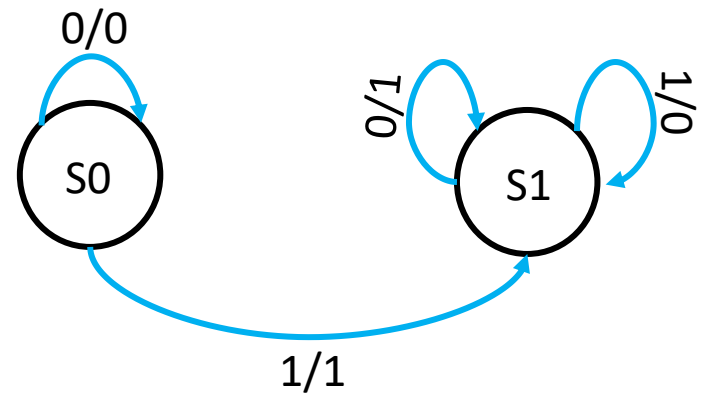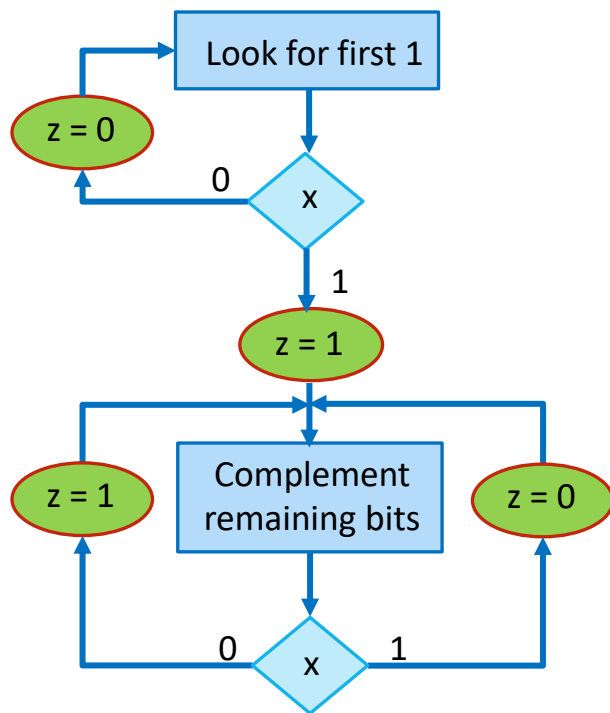

Outline

- Samples



Vendor Realization

Vending Machine: FSM

- **Insert coin**

- Default state
- No money has been inserted

- **5 Rials**


- A 5 Rial coin has been inserted

- **10 Rials**

- A 10 Rial coin has been inserted


- **15 Rials**

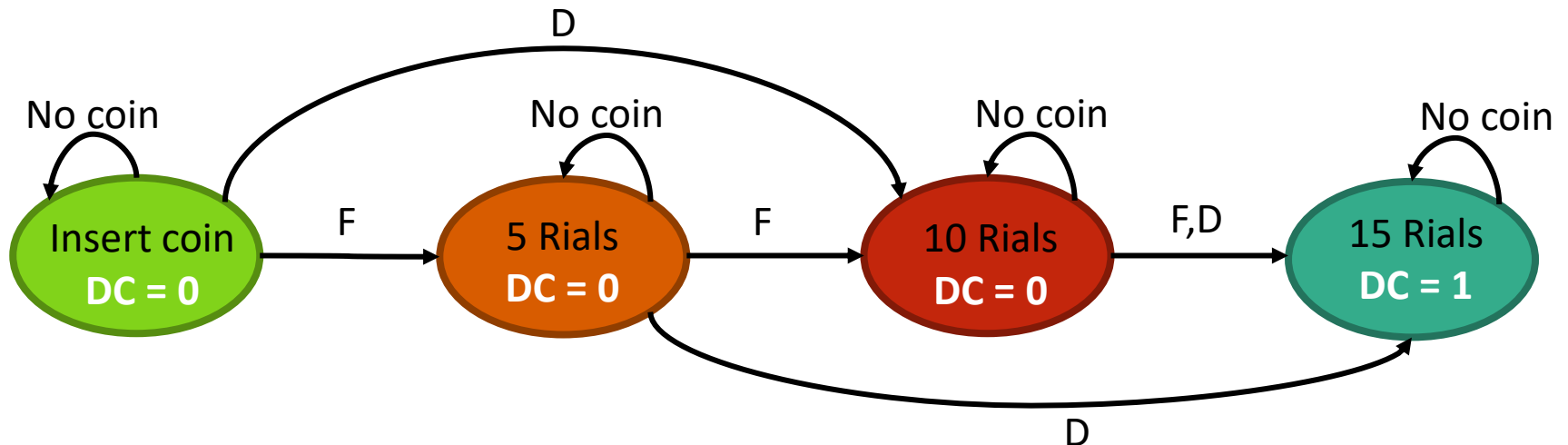- Total money has been reached to 15 Rial
- Done!




Vending Machine: Excitation Table

State Inputs		Insert coin	5 Rial	10 Rial	15 Rial
D	F	Next State/ Output	Next State/ Output	Next State/ Output	Next State/ Output
0	0	Insert coin/ DC=0	5 Rial/ DC=0	10 Rial/ DC=0	15 Rial/ DC=1
0	1	5 Rial/ DC=0	10 Rial/ DC=0	15 Rial/ DC=0	15 Rial/ DC=1
1	0	10 Rial/ DC=0	15 Rial/ DC=0	15 Rial/ DC=0	15 Rial/ DC=1
1	1				

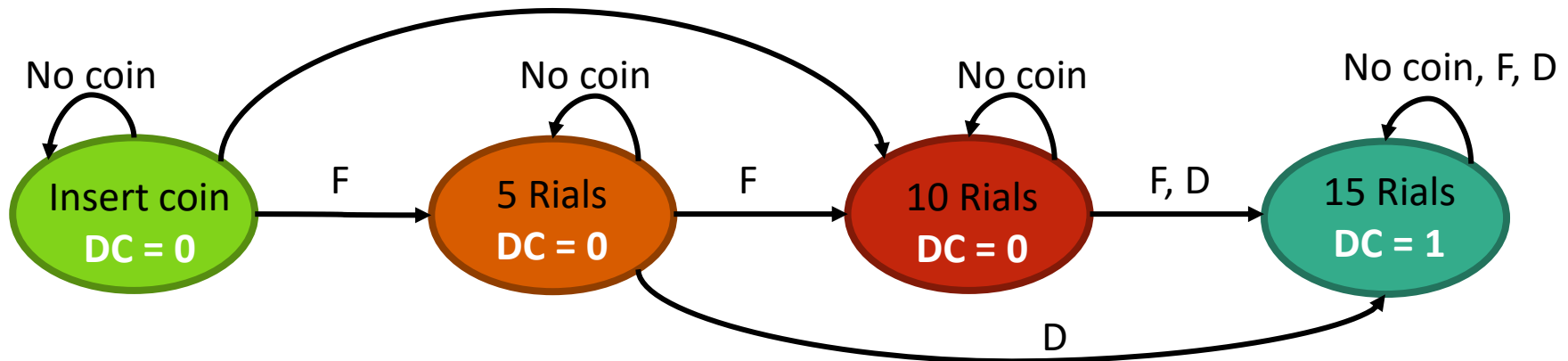


Vending Machine: Coded Excitation Table

State Inputs		0 0	0 1	1 0	1 1
D	F	Next State/ Output	Next State/ Output	Next State/ Output	Next State/ Output
0	0	0 0 / 0	0 1 / 0	1 0 / 0	1 1 / 1
0	1	0 1 / 0	1 0 / 0	1 1 / 0	1 1 / 1
1	0	1 0 / 0	1 1 / 0	1 5 / 0	1 1 / 1
1	1				

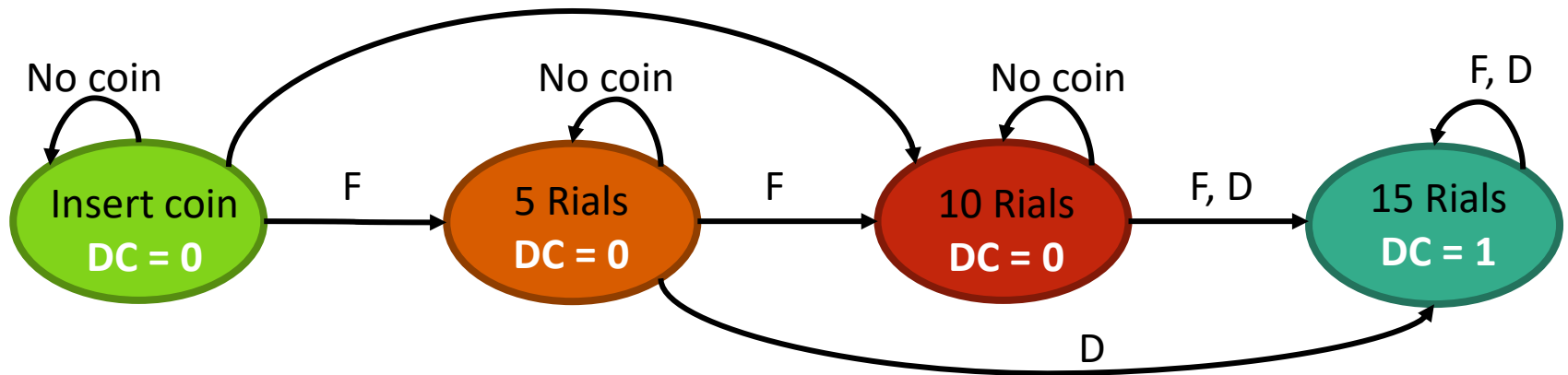


Vending Machine: D1

Inputs		State (Q_0Q_1)			
		00	01	10	11
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00/0	01/0	10/0	11/1
0	1	01/0	10/0	11/0	11/1
1	0	10/0	11/0	11/0	11/1
1	1				

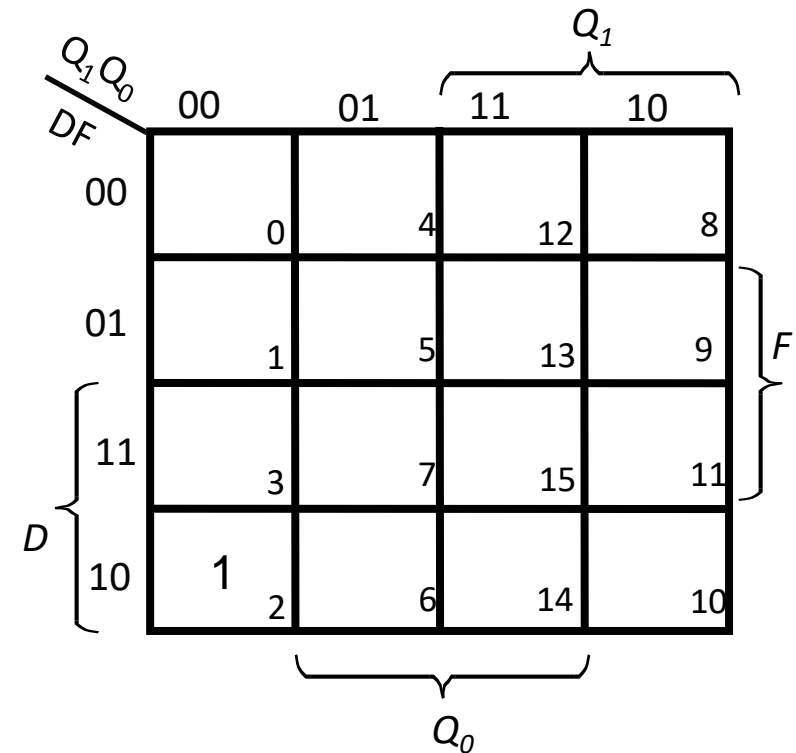


Vending Machine: D1

Inputs		State (Q_0Q_1)			
		00	01	10	11
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00/0	01/0	10/0	11/1
0	1	01/0	10/0	11/0	11/1
1	0	10/0	11/0	11/0	11/1
1	1				

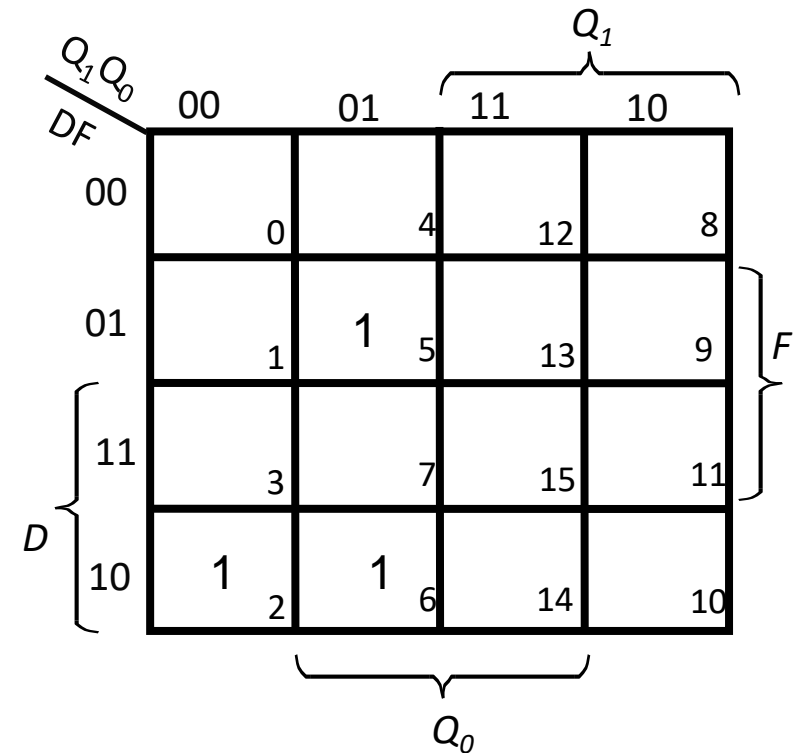


Vending Machine: D1

Inputs		State (Q_0Q_1)			
		0 0	0 1	1 0	1 1
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00 / 0	01 / 0	10 / 0	11 / 1
0	1	01 / 0	10 / 0	11 / 0	11 / 1
1	0	10 / 0	11 / 0	11 / 0	11 / 1
1	1				

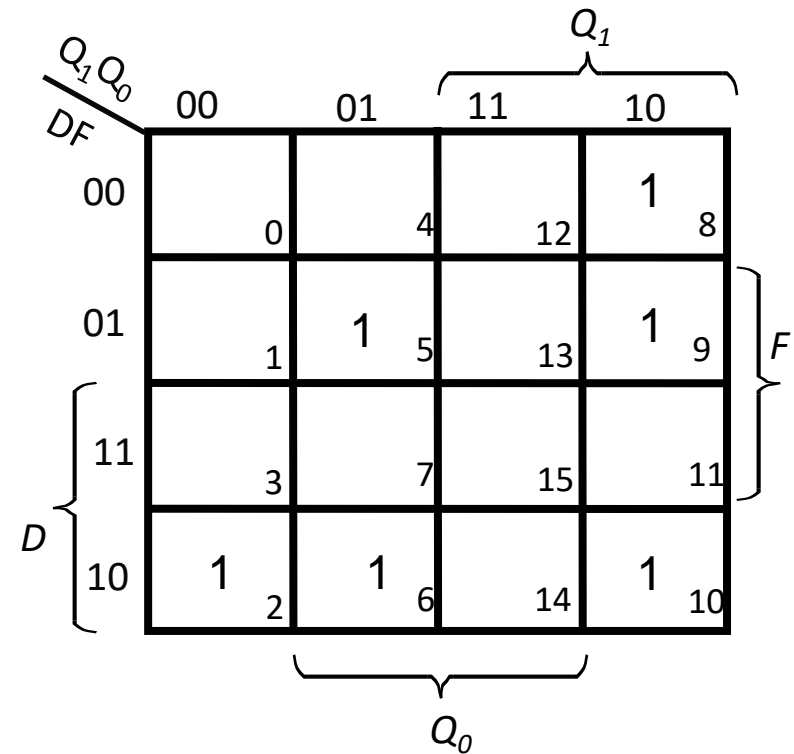


Vending Machine: D1

Inputs		State (Q_0Q_1)			
		0 0	0 1	1 0	1 1
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00 / 0	01 / 0	10 / 0	11 / 1
0	1	01 / 0	10 / 0	11 / 0	11 / 1
1	0	10 / 0	11 / 0	11 / 0	11 / 1
1	1				

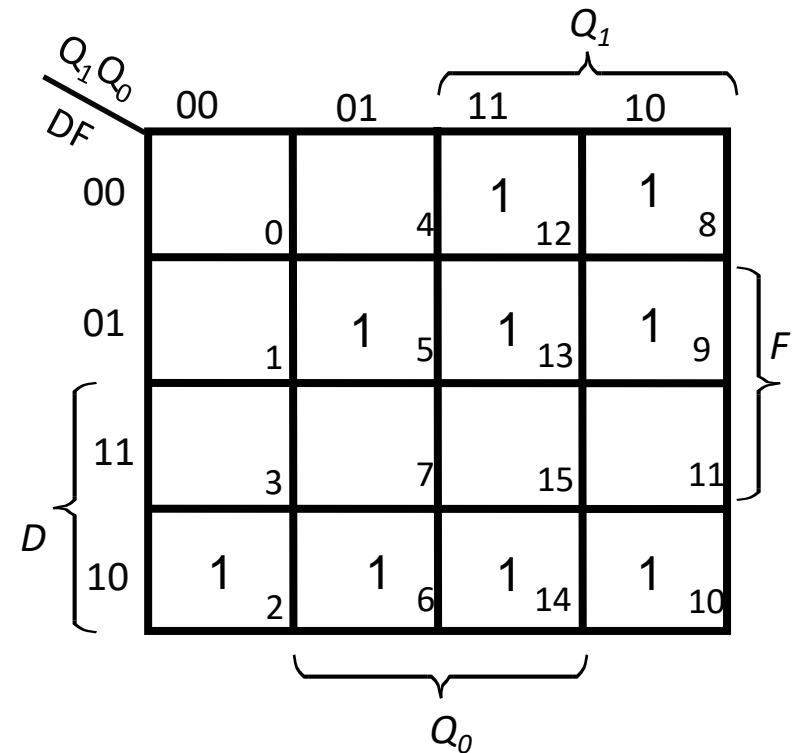

Vending Machine: D1


Inputs		State (Q_0Q_1)			
		0 0	0 1	1 0	1 1
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00 / 0	01 / 0	10 / 0	11 / 1
0	1	01 / 0	10 / 0	11 / 0	11 / 1
1	0	10 / 0	11 / 0	11 / 0	11 / 1
1	1				

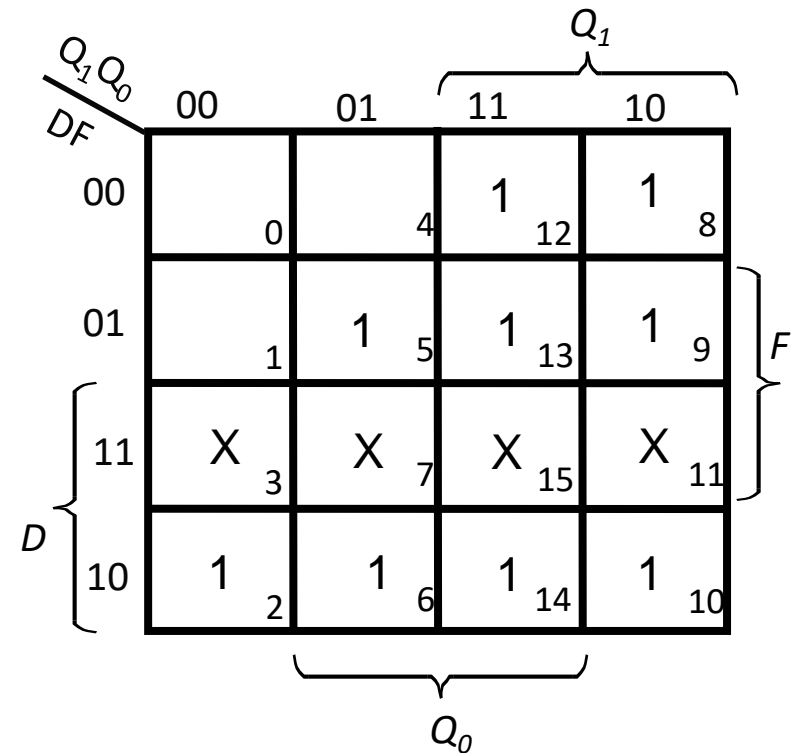

Vending Machine: D1


Inputs		State (Q_0Q_1)			
		00	01	10	11
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00/0	01/0	10/0	11/1
0	1	01/0	10/0	11/0	11/1
1	0	10/0	11/0	11/0	11/1
1	1				

$$D_1 = Q_1 + D + Q_0F$$

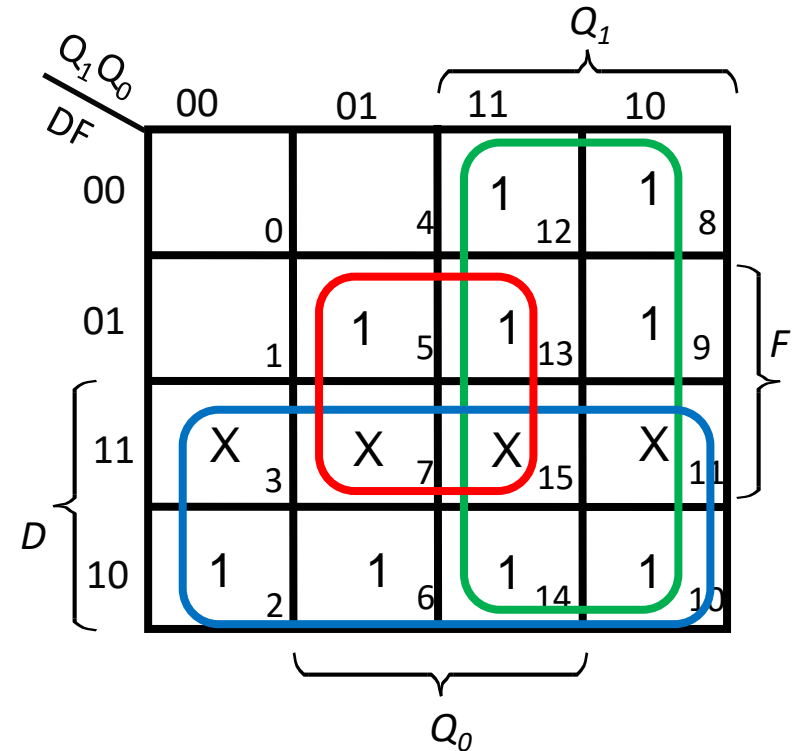


Vending Machine: D0

Inputs		State (Q_0Q_1)			
		0 0	0 1	1 0	1 1
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00 / 0	01 / 0	10 / 0	11 / 1
0	1	01 / 0	10 / 0	11 / 0	11 / 1
1	0	10 / 0	11 / 0	11 / 0	11 / 1
1	1				

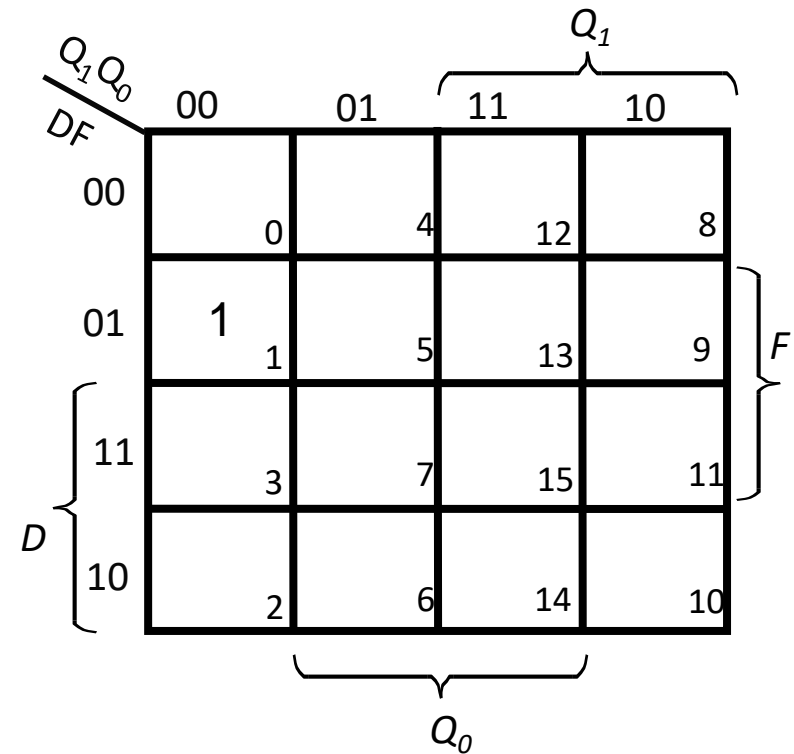


Vending Machine: D0

Inputs		State (Q_0Q_1)			
		0 0	0 1	1 0	1 1
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00 / 0	01 / 0	10 / 0	11 / 1
0	1	01 / 0	10 / 0	11 / 0	11 / 1
1	0	10 / 0	11 / 0	11 / 0	11 / 1
1	1				

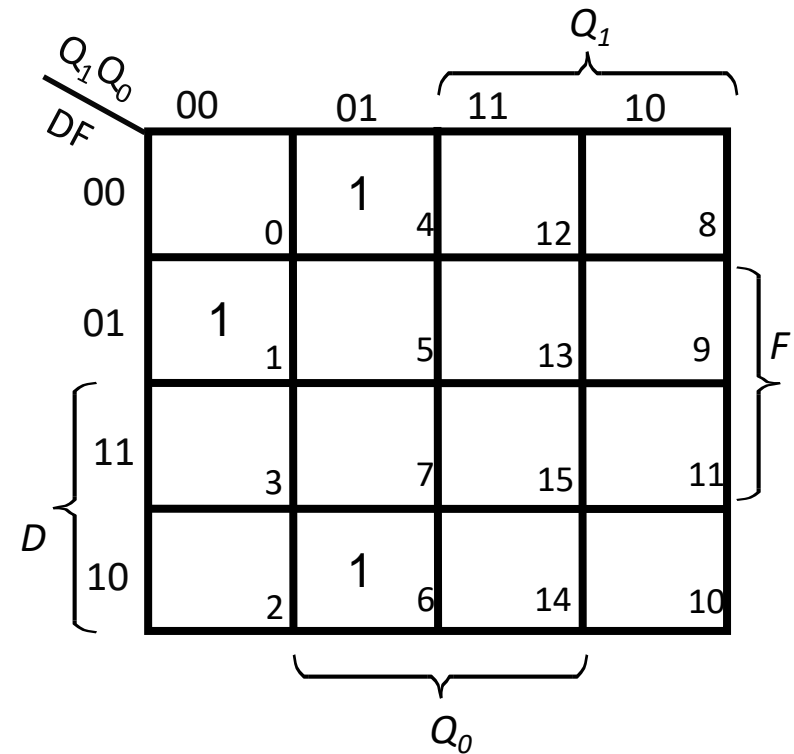


Vending Machine: D0

Inputs		State (Q_0Q_1)			
		0 0	0 1	1 0	1 1
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00 / 0	01 / 0	10 / 0	11 / 1
0	1	01 / 0	10 / 0	11 / 0	11 / 1
1	0	10 / 0	11 / 0	11 / 0	11 / 1
1	1				

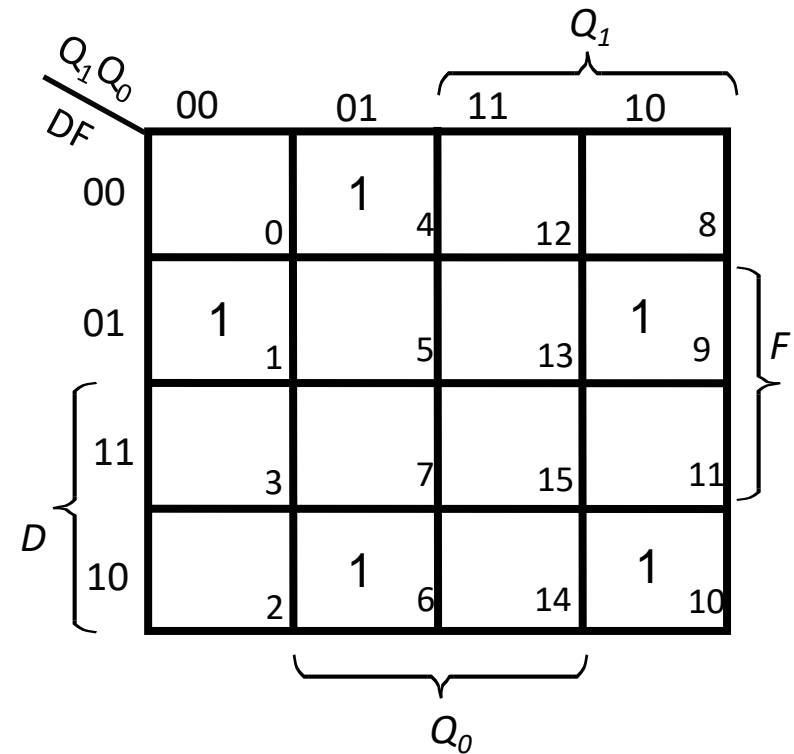


Vending Machine: D0

Inputs		State (Q_0Q_1)			
		0 0	0 1	1 0	1 1
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00 / 0	01 / 0	10 / 0	11 / 1
0	1	01 / 0	10 / 0	11 / 0	11 / 1
1	0	10 / 0	11 / 0	11 / 0	11 / 1
1	1				

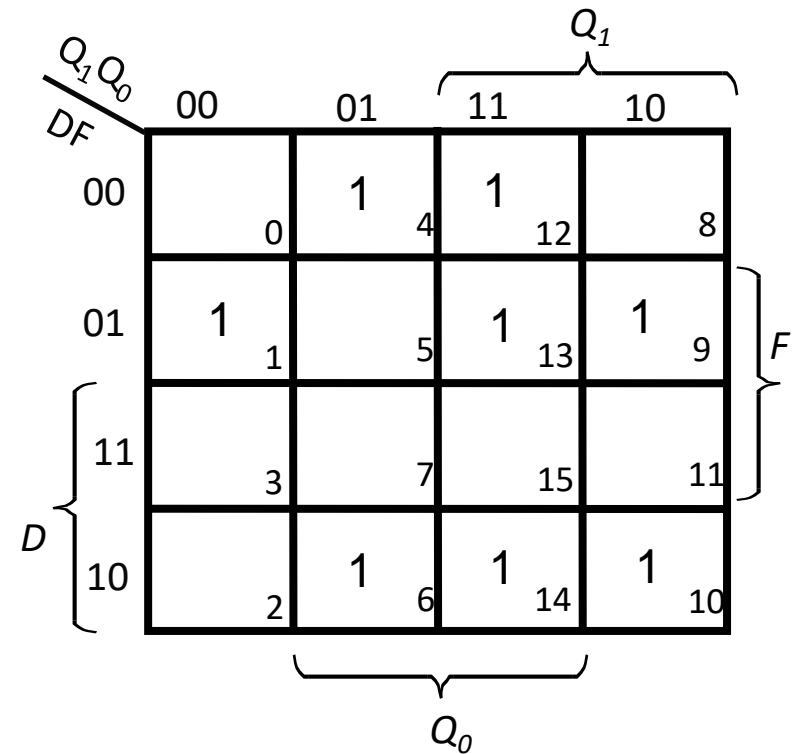


Vending Machine: D0

Inputs		State (Q_0Q_1)			
		00	01	10	11
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00/0	01/0	10/0	11/1
0	1	01/0	10/0	11/0	11/1
1	0	10/0	11/0	11/0	11/1
1	1				

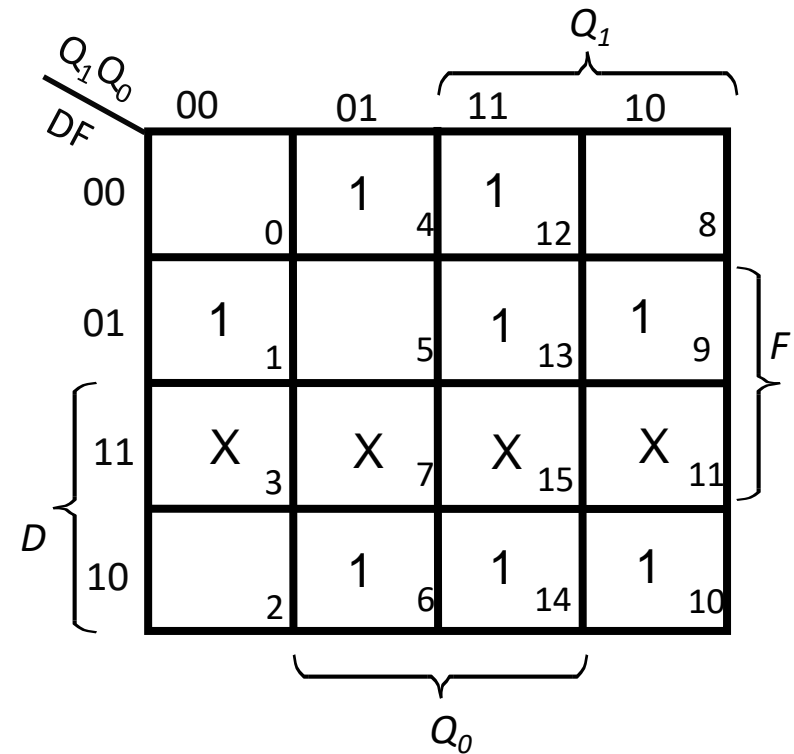

Vending Machine: D0

Inputs		State (Q_0Q_1)			
		00	01	10	11
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00/0	01/0	10/0	11/1
0	1	01/0	10/0	11/0	11/1
1	0	10/0	11/0	11/0	11/1
1	1				

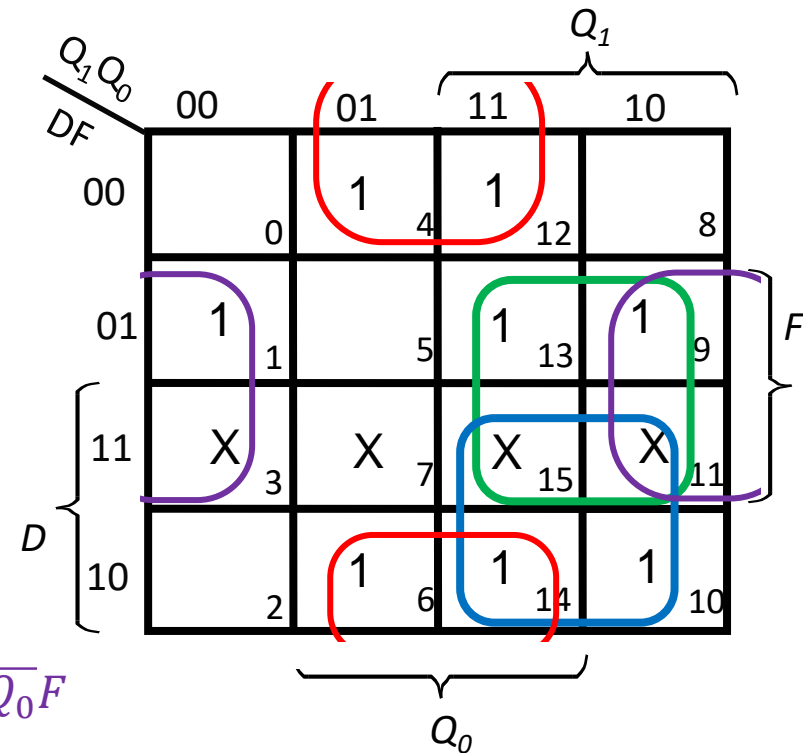


$$D_0 = Q_1F + Q_1D + Q_0\bar{F} + \bar{Q}_0F$$

Vending Machine: DC

Inputs		State (Q_0Q_1)			
		00	01	10	11
D	F	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out	Q_1Q_0 / Out
0	0	00/0	01/0	10/0	11/1
0	1	01/0	10/0	11/0	11/1
1	0	10/0	11/0	11/0	11/1
1	1				

$$Open = Q_1Q_0$$

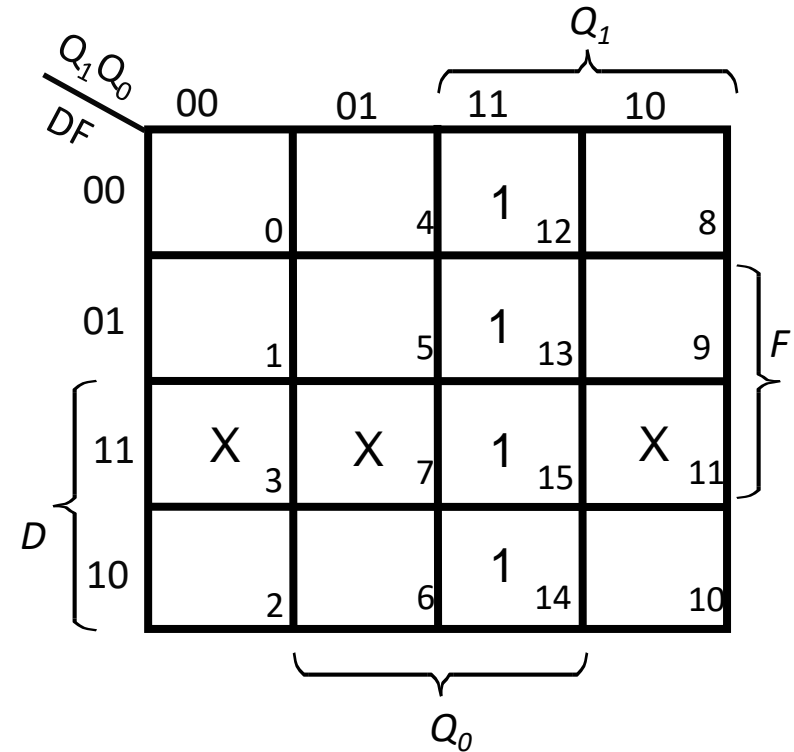


Vending Machine: DC

$$D_1 = Q_1 + D + Q_0 F$$

$$D_0 = Q_1 F + Q_1 D + Q_0 \bar{F} + \bar{Q}_0 F$$


$$Open = Q_1 Q_0$$

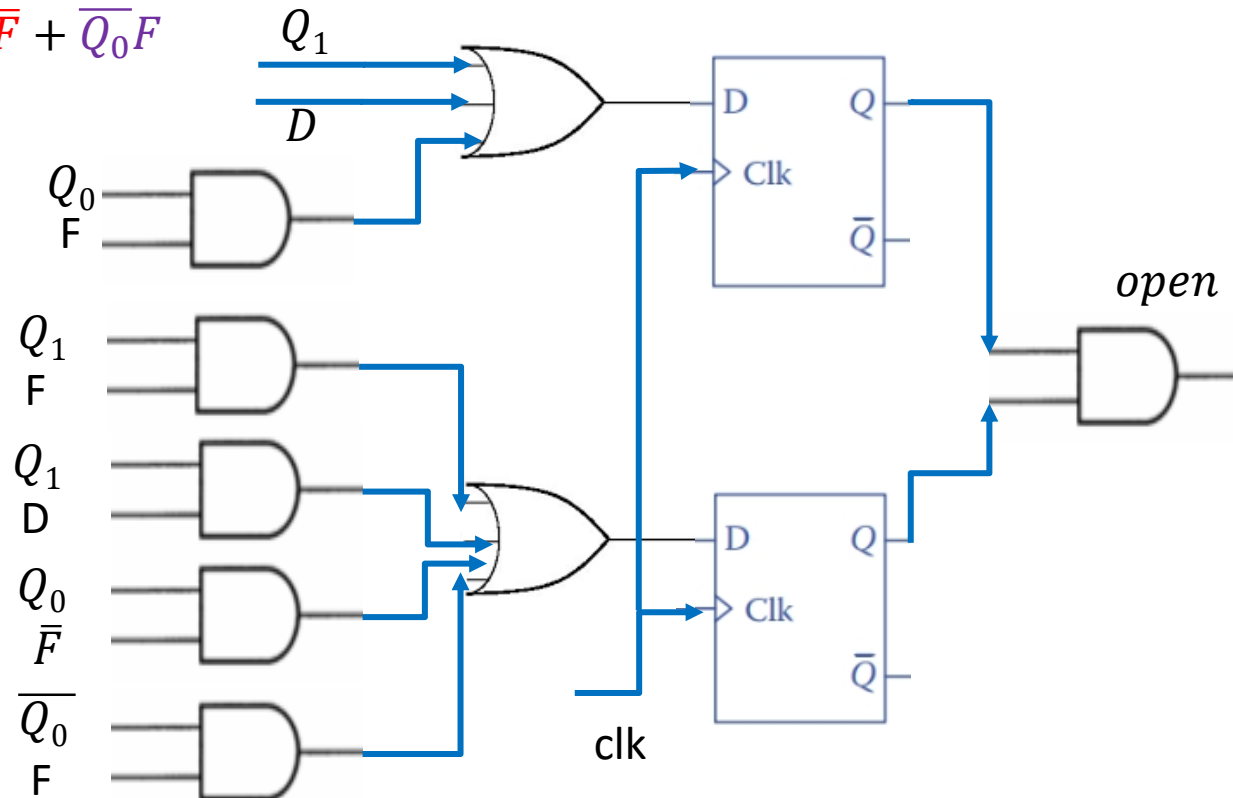

Check Yourself 😊

Vending Machine

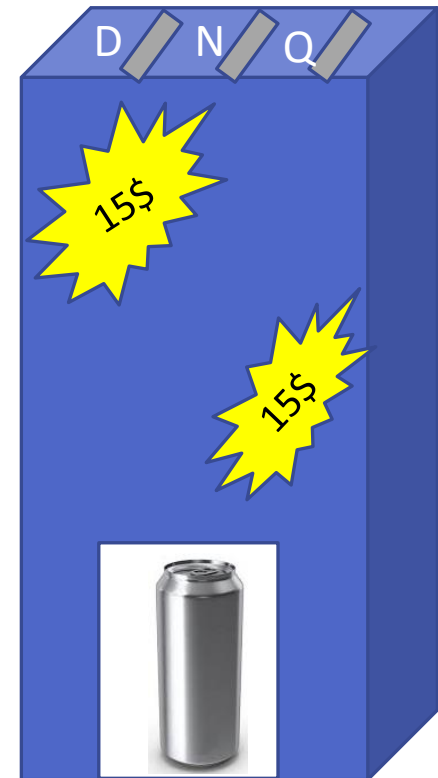- The computer department need a new soda machine.
- Please define a controller for new vending machine.
- **Characteristics**
 - All selections cost **30** cent
 - **Machine returns changes!**
- **Input**
 - Q: quarter inserted (25 cent)
 - D: dim inserted (10 cent)
 - N: nickle inserted (5 cent)
- **Output**
 - DC: dispense can



Chess Match Timer

- We want to measure how much time each chess player thinks to select next moves in a chess match and show the thinking time of each player at the end of the match.
- We have a limited money budget and can afford only the cost of one timer for both players!
- Upload by Sunday 1399/1/17



Thank You

