



# Digital System Design

---

Hajar Falahati

[hfalahati@ipm.ir](mailto:hfalahati@ipm.ir)  
[hfalahati@ce.sharif.edu](mailto:hfalahati@ce.sharif.edu)

# Combinational Logic & Verilog


---

- Combinational Logic
  - Use **always block** + “**blocking**” assignments
    - Normally for high-complexity Comb. Logic
    - When output depends on several conditions, which requires if-else
- Sequential Logic
  - Can **only** be realized using an **always block**
  - When using the **always block** for the sequential Logic, “**Non-blocking**” assignments are used
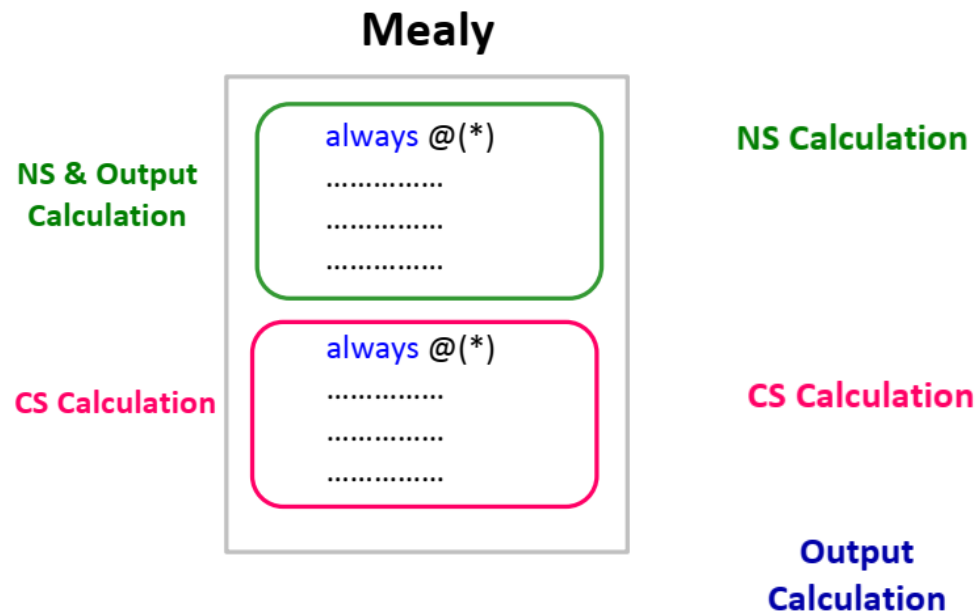
# FSM Code Structure

- Mealy


- Output depends on input
- Output declared as **reg**



- Moore

- Output does not depends on input
- Output declared as **wire**

## Moore

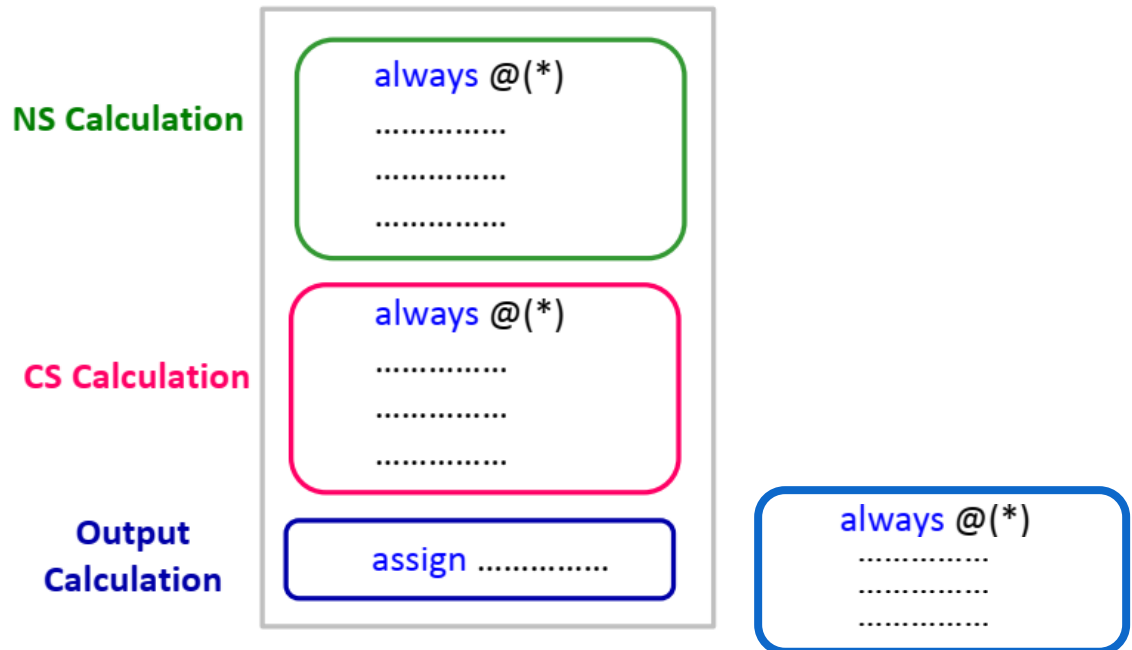

# Function vs. Task

---

Functions	Tasks
A function can enable another function but not another task.	A task can enable other tasks and functions.
Functions always execute in 0 simulation time.	Tasks may execute in non-zero simulation time.
Functions must not contain any delay, event, or timing control statements.	Tasks may contain delay, event, or timing control statements.
Functions must have at least one input argument. They can have more than one input.	Tasks may have zero or more arguments of type input, output, or inout.
Functions always return a single value. They cannot have output or inout arguments.	Tasks do not return with a value, but can pass multiple values through output and inout arguments.

# Outline

---

- Timing
- Testbench



# Tradeoffs in Circuit Design

---


# Circuit Design is a Tradeoff Between:

---

- Area
  - Circuit **area** is proportional to the **cost** of the device
- Speed / Throughput
  - We want **faster**, more **capable** circuits
- Power / Energy
  - Mobile devices need to work with a **limited** power supply
  - High performance devices **dissipate** more than 100 W/cm<sup>2</sup>
- Design Time
  - Designers are **expensive** in *time* and *money*
  - The **competition** will not wait for you

# Requirements and Goals Depend On Application

---

 



# Circuit Timing

---

- Until now, we investigated **logical functionality**
- What about **timing**?
  - How **fast** is a circuit?
  - How can we make a circuit **faster**?
  - What happens if we run a circuit **too fast**?
- A design that is logically correct can still **fail** because of real-world **implementation issues**!



# Combinational Circuit Timing

---
  
# Digital Logic Abstraction



---

- “**Digital logic**” is a convenient **abstraction**
  - Output changes *immediately* with the input



  
# Combinational Circuit Delay

- In reality, **outputs** are **delayed** from **inputs**
  - Transistors take a finite amount of time to switch



# Real Inverter Delay Example

 

# Circuit Delay and Its Variation

---


- Delay is fundamentally caused by
  - **Capacitance** and **resistance** in a circuit
- **Anything** affecting these quantities can change delay:
  - **Rising** (i.e., 0 → 1) vs. **falling** (i.e., 1 → 0) inputs
  - Different **inputs** have different **delays**
  - Changes in **environment** (e.g., temperature)
  - **Aging** of the circuit
- We have a **range of possible delays** from input to output




# Delays from Input to Output

- **Contamination delay ( $t_{cd}$ )**: delay until Y *starts changing*
- **Propagation delay ( $t_{pd}$ )**: delay until Y *finishes changing*

## Example Circuit

 


## Effect of Changing Input 'A'

 

**Cross-hatching  
means value is changing**
 
# Calculating Long/Short Paths

- We care about **both** the *longest* and *shortest* paths in a circuit





**Critical (Longest) Path:**  $t_{pd} = 2 t_{pd\_AND} + t_{pd\_OR}$

**Shortest Path:**  $t_{cd} = t_{cd\_AND}$


  
# Example $t_{pd}$ for a Real NAND-2 Gate



Symbol	Parameter	Conditions	25 °C			−40 °C to +125 °C		Unit
			Min	Typ	Max	Max (85 °C)	Max (125 °C)	
74HC00								
t <sub>pd</sub>	propagation delay	nA, nB to nY; see <a href="#">Figure 6</a> <a href="#">[1]</a>						
		V <sub>CC</sub> = 2.0 V	-	25	-	115	135	ns
		V <sub>CC</sub> = 4.5 V	-	9	-	23	27	ns
		V <sub>CC</sub> = 5.0 V; C <sub>L</sub> = 15 pF	-	7	-	-	-	ns
		V <sub>CC</sub> = 6.0 V	-	7	-	20	23	ns

Heavy **dependence** on **voltage** and **temperature**!


# Example Worst-Case $t_{pd}$

- Two different **implementations** of a **4:1 multiplexer**


## Gate Delays

Gate	$t_{pd}$ (ps)
NOT	30
2-input AND	60
3-input AND	80
4-input OR	90
tristate (A to Y)	50
tristate (enable to Y)	35

## Implementation 1

 

## Implementation 2

 

Different designs lead to very  
**different delays**


# Example Worst-Case $t_{pd}$

- Two different **implementations** of a **4:1 multiplexer**

## Gate Delays

Gate	$t_{pd}$ (ps)
NOT	30
2-input AND	60
3-input AND	80
4-input OR	90
tristate (A to Y)	50
tristate (enable to Y)	35

## Implementation 1

 


$$t_{pd_{sy}} = t_{pd\_INV} + t_{pd\_AND3} + t_{pd\_OR4}$$

$$= 30 \text{ ps} + 80 \text{ ps} + 90 \text{ ps}$$

(a)  $t_{pd_{dy}} = t_{pd\_AND3} + t_{pd\_OR4}$

$$= 170 \text{ ps}$$

## Implementation 2

 

$$t_{pd_{sy}} = t_{pd\_INV} + t_{pd\_AND2} + t_{pd\_TRI\_SY}$$

$$= 30 \text{ ps} + 60 \text{ ps} + 35 \text{ ps}$$

(b)  $t_{pd_{dy}} = t_{pd\_TRI\_AY}$

$$= 50 \text{ ps}$$

**Different designs lead to very different delays**

# Calculating Long/Short Paths

---

- It's **not** always this easy to determine the long/short paths!
  - Not all **input transitions** affect the **output**
  - Can have **multiple different paths** from an input to output
- In reality, circuits are **not** all built equally
  - Different instances of the **same gate** have **different delays**
  - **Wires** have **nonzero delay** (increasing with length)
  - Temperature/voltage affect circuit speeds
    - Not all circuit elements are affected the same way
    - Can even **change the critical path**!
- Designers assume “**worst-case**” **conditions** and run many **statistical simulations** to balance yield/performance

# Combinational Timing Summary

---

- Circuit outputs change some time **after** the inputs change
  - Delay is dependent on inputs, environmental state, etc.
- The range of possible delays is characterized by:
  - **Contamination delay ( $t_{cd}$ )**: *minimum possible delay*
  - **Propagation delay ( $t_{pd}$ )**: *maximum possible delay*
- Delays **change** with:
  - Circuit design (e.g., topology, materials)
  - Operating conditions


# Sequential Circuit Timing

---
 
# Recall: D Flip-Flop

---


- Flip-flop **samples D** at the **active clock edge**
  - It outputs the **sampled value** to Q
  - It **“stores”** the **sampled value** until the next active clock edge



- The D flip-flop is **made** from **combinational** elements
- **D, Q, CLK all have timing requirements!**
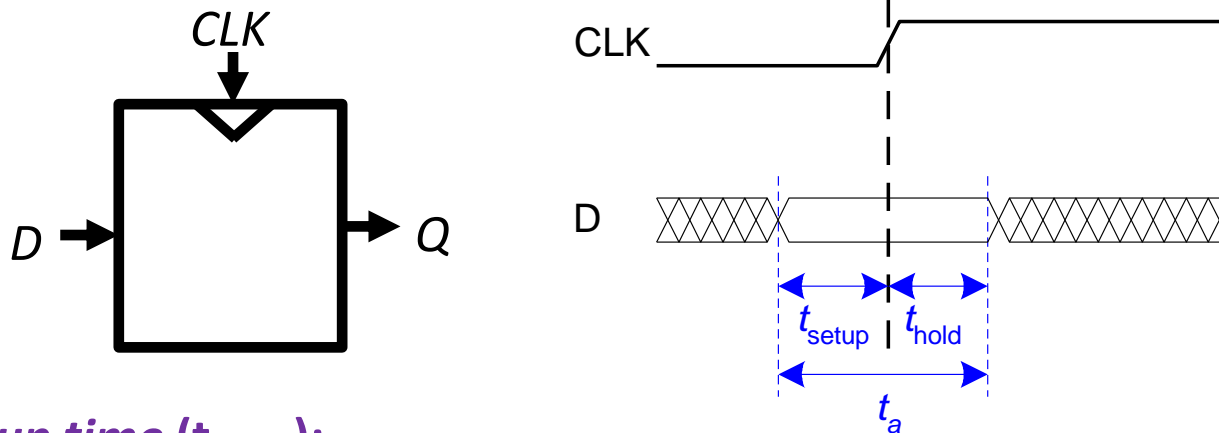
# D Flip-Flop Input Timing Constraints

- D must be **stable** when **sampled** (i.e., at active clock edge)



- **Setup time ( $t_{\text{setup}}$ ):**
  - Time **before** the clock edge that data must be stable (i.e. not changing)
- **Hold time ( $t_{\text{hold}}$ ):**
  - Time **after** the clock edge that data must be stable
- **Aperture time ( $t_a$ ):**
  - Time **around** clock edge that data must be stable ( $t_a = t_{\text{setup}} + t_{\text{hold}}$ )




# Violating Input Timing: Metastability

- If D is **changing** when sampled, **metastability** can occur
  - Flip-flop output is **stuck** somewhere between '1' and '0'
  - Output eventually settles **non-deterministically**


Example Timing  
Violations (NAND  
RS Latch)

CLK

Q

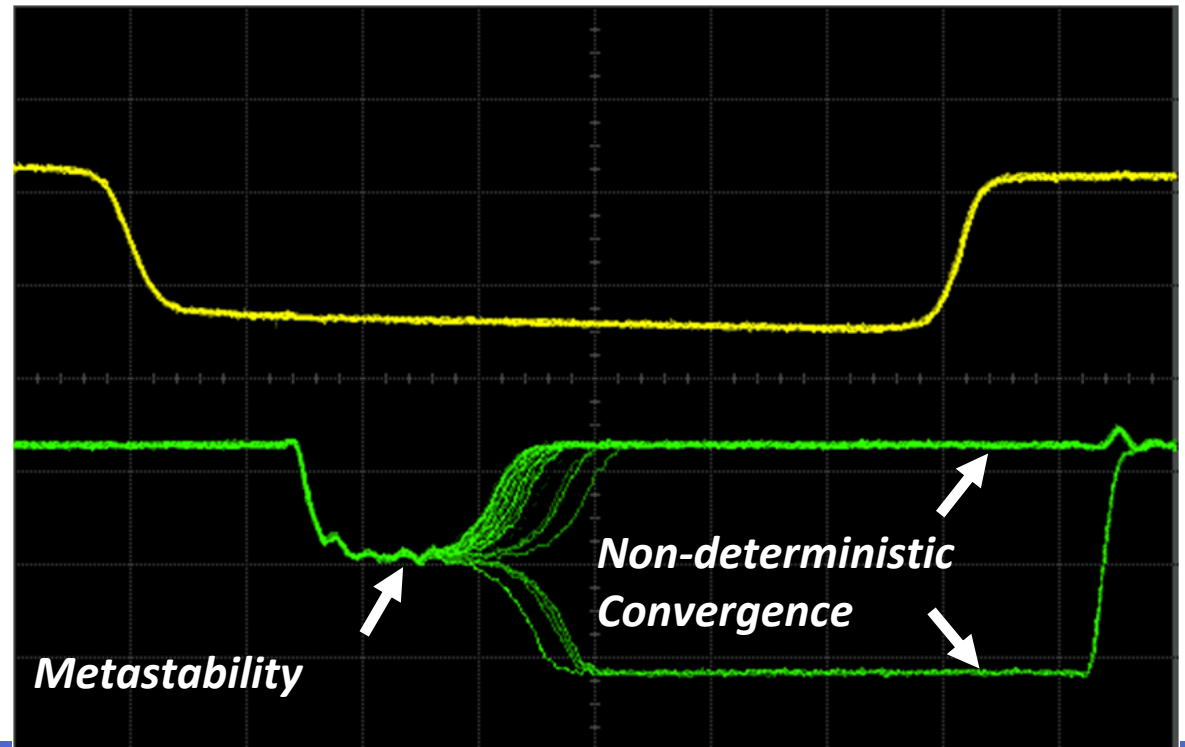


# Flip-Flop Output Timing

 

- **Contamination delay clock-to-q ( $t_{ccq}$ ):**
  - Earliest time after the clock edge that  $Q$  starts to change (i.e., is unstable)
- **Propagation delay clock-to-q ( $t_{pcq}$ ):**
  - Latest time after the clock edge that  $Q$  stops changing (i.e., is stable)

# Recall: Sequential System Design

---


 


- Multiple **flip-flops** are connected with **combinational logic** **Clock** runs with period  $T_c$  (cycle time)

**Must meet timing requirements for both R1 and R2!**
  
# Ensuring Correct Sequential Operation

- Need to ensure correct input timing on **R2**
- Specifically, **D2** must be **stable**:
  - at least  $t_{\text{setup}}$  **before** the clock edge
  - at least until  $t_{\text{hold}}$  **after** the clock edge




# Ensuring Correct Sequential Operation

---

- This means there is both a **minimum** and **maximum** delay between two flip-flops


 
# Ensuring Correct Sequential Operation: FAST CL

- This means there is both a **minimum** and **maximum** delay between two flip-flops
- CL **too fast** -> R2  $t_{\text{hold}}$  violation


  
# Ensuring Correct Sequential Operation: FAST CL

- This means there is both a **minimum** and **maximum** delay between two flip-flops
- CL **too fast** -> R2  $t_{\text{hold}}$  violation





# Ensuring Correct Sequential Operation: FAST CL

- This means there is both a **minimum** and **maximum** delay between two flip-flops

- CL **too fast** -> R2  $t_{\text{hold}}$  violation

**Potential**


**$R2$   $t_{\text{HOLD}}$  VIOLATION!**

  



 
# Ensuring Correct Sequential Operation: SLOW CL

- This means there is both a **minimum** and **maximum** delay between two flip-flops
- CL **too slow** -> R2  $t_{\text{setup}}$  violation


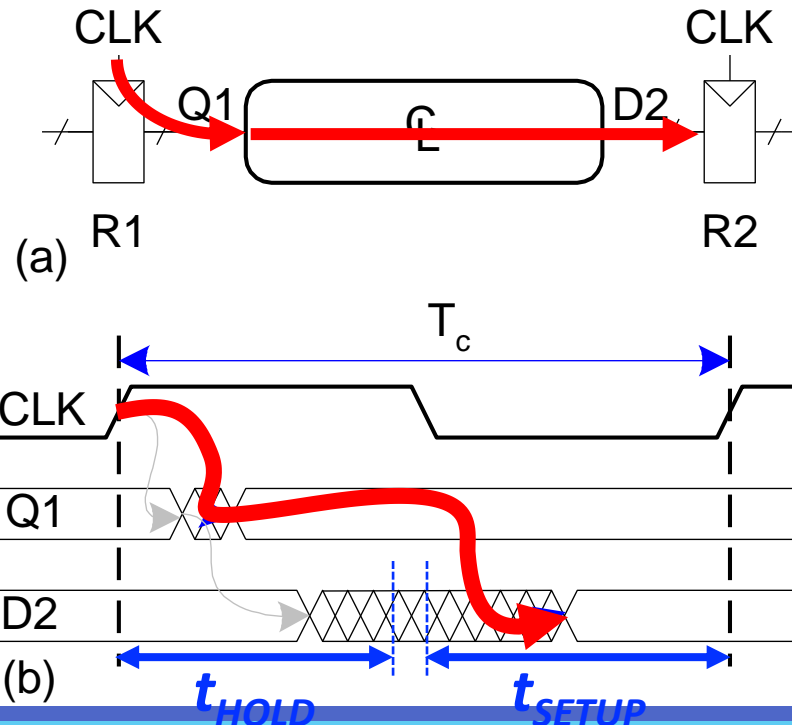
# Ensuring Correct Sequential Operation: SLOW CL

- This means there is both a **minimum** and **maximum** delay between two flip-flops
- CL **too slow** -> R2  $t_{\text{setup}}$  violation





# Ensuring Correct Sequential Operation: SLOW CL

- This means there is both a **minimum** and **maximum** delay between two flip-flops

- CL **too slow** -> R2  $t_{\text{setup}}$  violation


**Potential**

**R2  $t_{\text{SETUP}}$  VIOLATION!**

  


 
# Ensuring Correct Sequential Operation

- This means there is both a **minimum** and **maximum** delay between two flip-flops
- CL **too fast** -> R2  $t_{\text{hold}}$  violation
- CL **too slow** -> R2  $t_{\text{setup}}$  violation



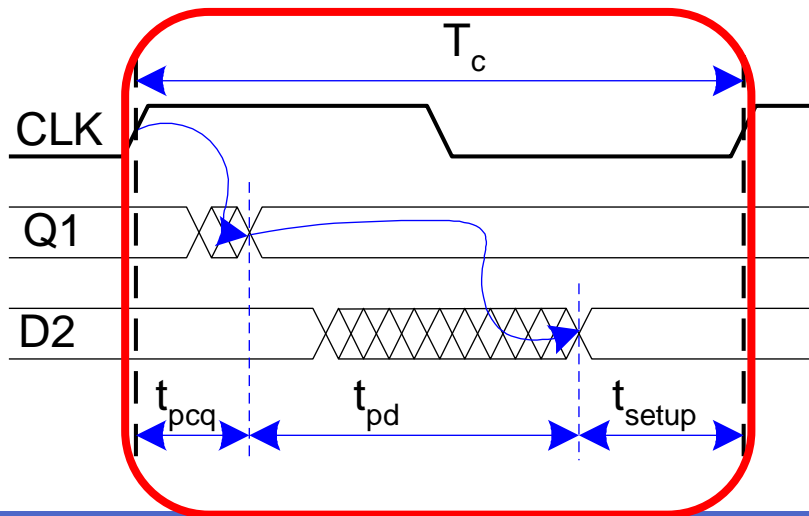 
# Setup Time Constraint

- **Safe timing** depends on the **maximum** delay from R1 to R2
- The input to R2 must be stable at least  $t_{\text{setup}}$  **before** the clock edge.



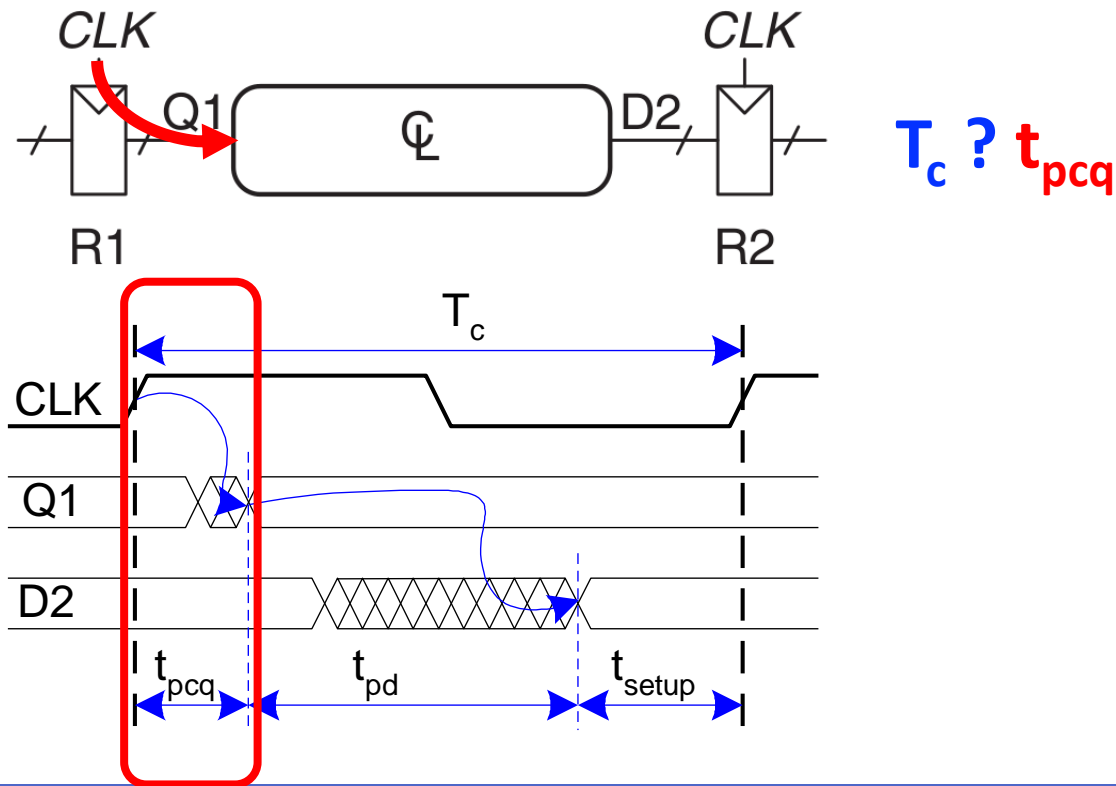
# Setup Time Constraint

- **Safe timing** depends on the **maximum** delay from R1 to R2
- The input to R2 must be stable at least  $t_{\text{setup}}$  **before** the clock edge.



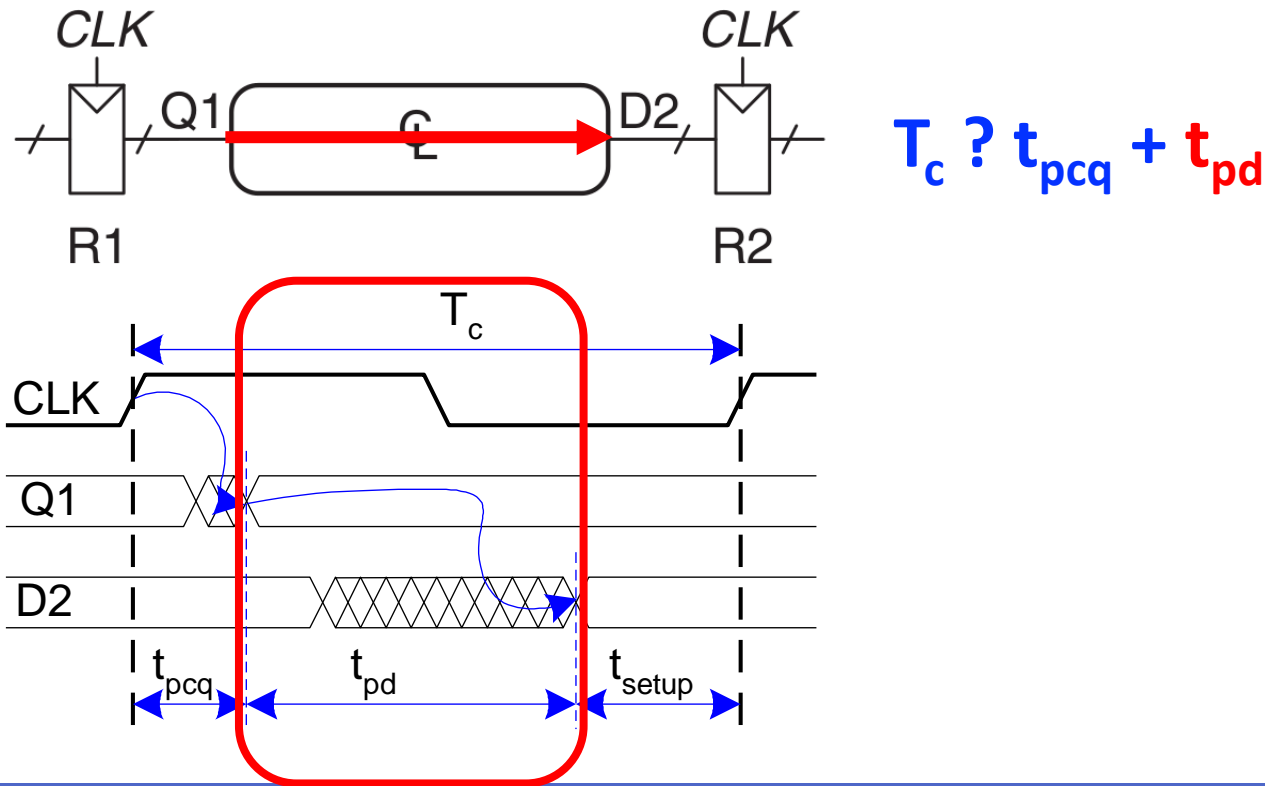
# Setup Time Constraint

- **Safe timing** depends on the **maximum** delay from R1 to R2
- The input to R2 must be stable at least  $t_{\text{setup}}$  **before** the clock edge.



 
# Setup Time Constraint

- **Safe timing** depends on the **maximum** delay from R1 to R2
- The input to R2 must be stable at least  $t_{\text{setup}}$  **before** the clock edge.



 
$$T_c \geq t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}}$$





 
# Setup Time Constraint

- **Safe timing** depends on the **maximum** delay from R1 to R2
- The input to R2 must be stable at least  $t_{\text{setup}}$  **before** the clock edge.



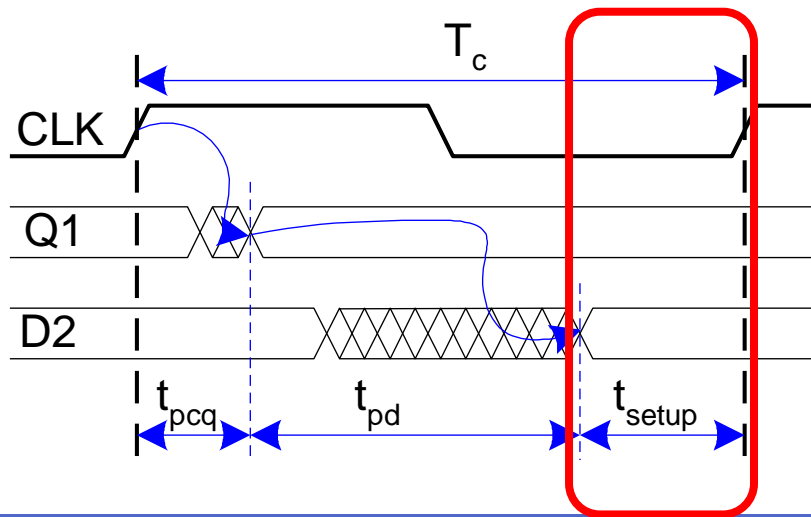
$$T_c > t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}}$$


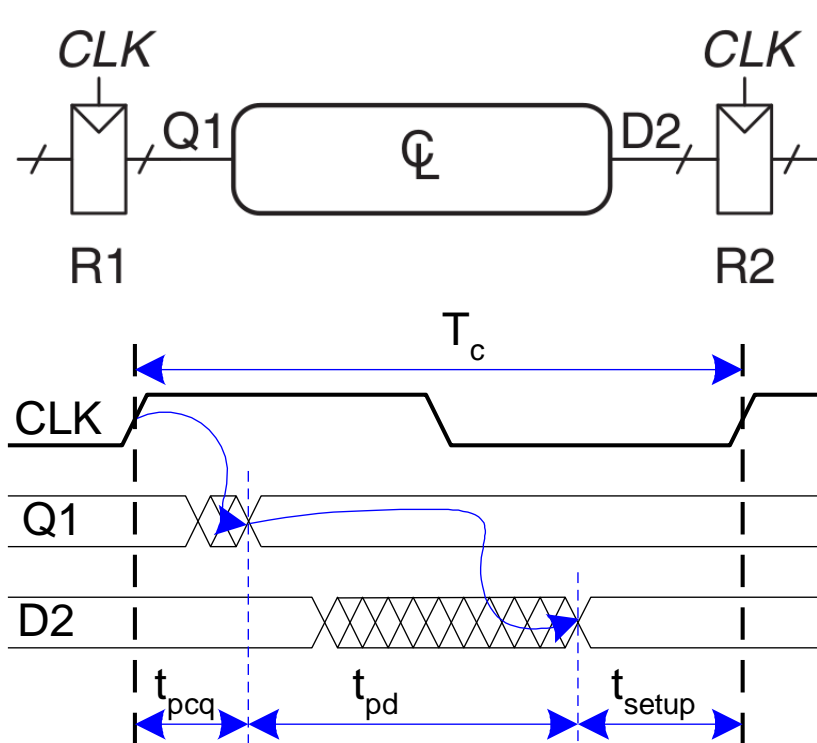
# Setup Time Constraint

- **Safe timing** depends on the **maximum** delay from R1 to R2
- The input to R2 must be stable at least  $t_{\text{setup}}$  **before** the clock edge.



$$T_c > t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}}$$

Wasted work


Useful work

**Sequencing overhead:**  
amount of time **wasted**  
each cycle due to sequencing  
element timing requirements
 
# $t_{\text{setup}}$ Constraint and Design Performance

- **Critical path:** path with the longest  $t_{\text{pd}}$


$$T_c > t_{\text{pcq}} + t_{\text{pd}} + t_{\text{setup}}$$



- Overall design performance is determined by the critical path  $t_{\text{pd}}$ 
  - Determines the **minimum clock period** (i.e., **max operating frequency**)
  - If the critical path is too **long**, the design will run **slowly**
  - If critical path is too **short**, each cycle will do very **little useful work**
    - i.e., most of the cycle will be **wasted** in sequencing overhead
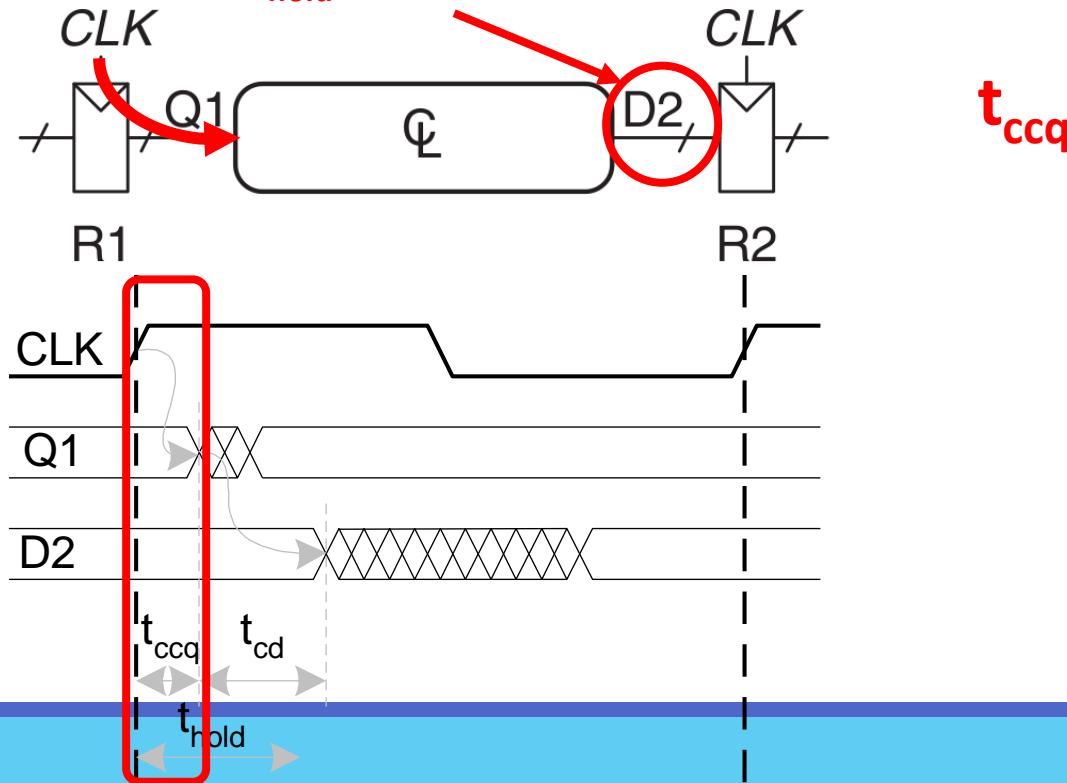
# Hold Time Constraint


- **Safe timing** depends on the **minimum** delay from R1 to R2
- **D2** (i.e., R2 input) must be stable for at least  $t_{\text{hold}}$  **after** the clock edge  
*Must not change until  $t_{\text{hold}}$  after the clock*


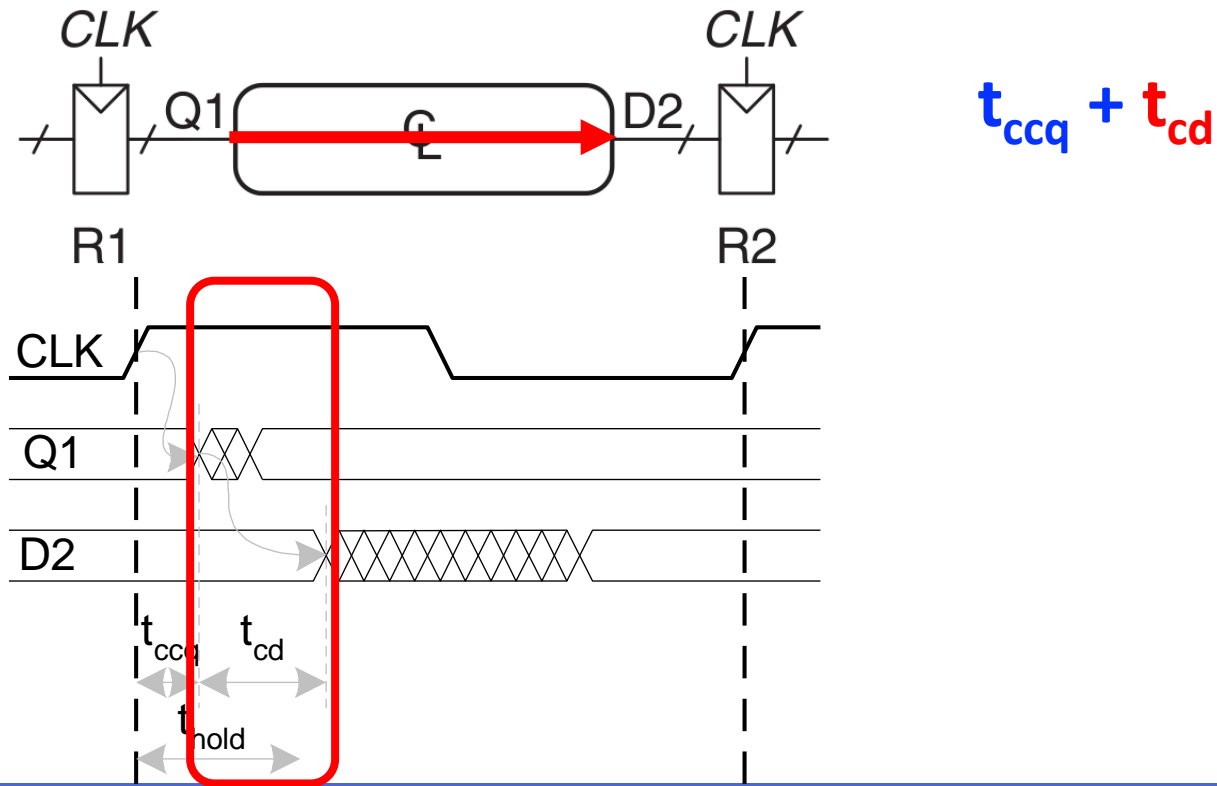
# Hold Time Constraint

**Safe timing** depends on the **minimum** delay from R1 to R2


**D2** (i.e., R2 input) must be stable for at least  $t_{\text{hold}}$  **after** the clock edge


 
# Hold Time Constraint

**Safe timing** depends on the **minimum** delay from R1 to R2

**D2** (i.e., R2 input) must be stable for at least  $t_{\text{hold}}$  **after** the clock edge




$$t_{\text{ccq}} + t_{\text{cd}} > t_{\text{hold}}$$
 
# Hold Time Constraint

**Safe timing** depends on the **minimum** delay from R1 to R2

**D2** (i.e., R2 input) must be stable for at least  $t_{\text{hold}}$  **after** the clock edge



$$t_{\text{ccq}} + t_{\text{cd}} > t_{\text{hold}}$$


$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}}$$

We need to have a **minimum** combinational delay!
 
# Hold Time Constraint

**Safe timing** depends on the **minimum** delay from R1 to R2

**D2** (i.e., R2 input) must be stable for at least  $t_{\text{hold}}$  **after** the clock edge



$$t_{\text{ccq}} + t_{\text{cd}} > t_{\text{hold}}$$

$$t_{\text{cd}} > t_{\text{hold}} - t_{\text{ccq}}$$

Does **NOT** depend on  $T_c$ !





**Very hard** to fix  $t_{\text{hold}}$  violations after manufacturing- must modify circuits!




# Sequential Timing Summary

$t_{ccq} / t_{pcq}$	clock-to-q delay (contamination/propagation)
$t_{cd} / t_{pd}$	combinational logic delay (contamination/propagation)
$t_{setup}$	time that FF inputs must be stable before next clock edge
$t_{hold}$	time that FF inputs must be stable after a clock edge
$T_c$	clock period

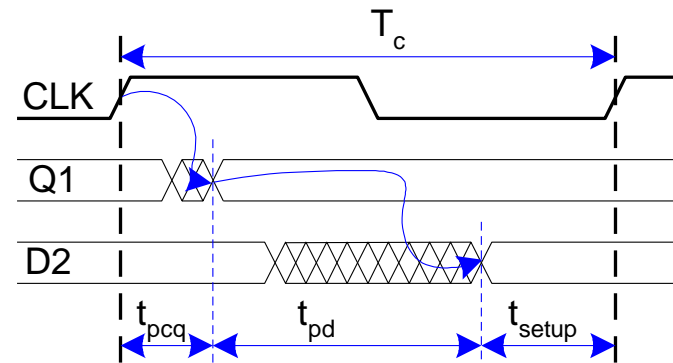 

# Example: Timing Analysis

 

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$


$$t_{\text{hold}} = 90 \text{ ps}$$

per gate

$$\left[ \begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right.$$

# Example: Timing Analysis

## Timing Characteristics

 

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

per gate

# Example: Timing Analysis

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$


$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

 

per gate

$$t_{pd} =$$

$$t_{cd} =$$

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{\text{setup}}$$


$$T_c >$$

$$f_{\text{max}} = 1/T_c =$$

Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

# Example: Timing Analysis

 

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

per gate

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} =$$

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{\text{setup}}$$


$$T_c >$$

$$f_{\text{max}} = 1/T_c =$$

Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

# Example: Timing Analysis

 
$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$
$$t_{cd} = 25 \text{ ps}$$

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$
$$t_{pcq} = 50 \text{ ps}$$
$$t_{\text{setup}} = 60 \text{ ps}$$
$$t_{\text{hold}} = 70 \text{ ps}$$
$$\text{per gate} \begin{bmatrix} t_{pd} \\ t_{cd} \end{bmatrix} = \begin{bmatrix} 35 \text{ ps} \\ 25 \text{ ps} \end{bmatrix}$$

## Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{setup}$$


$T_c >$

$$f_{max} = 1/T_c =$$

### Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{hold} ?$$

# Example: Timing Analysis

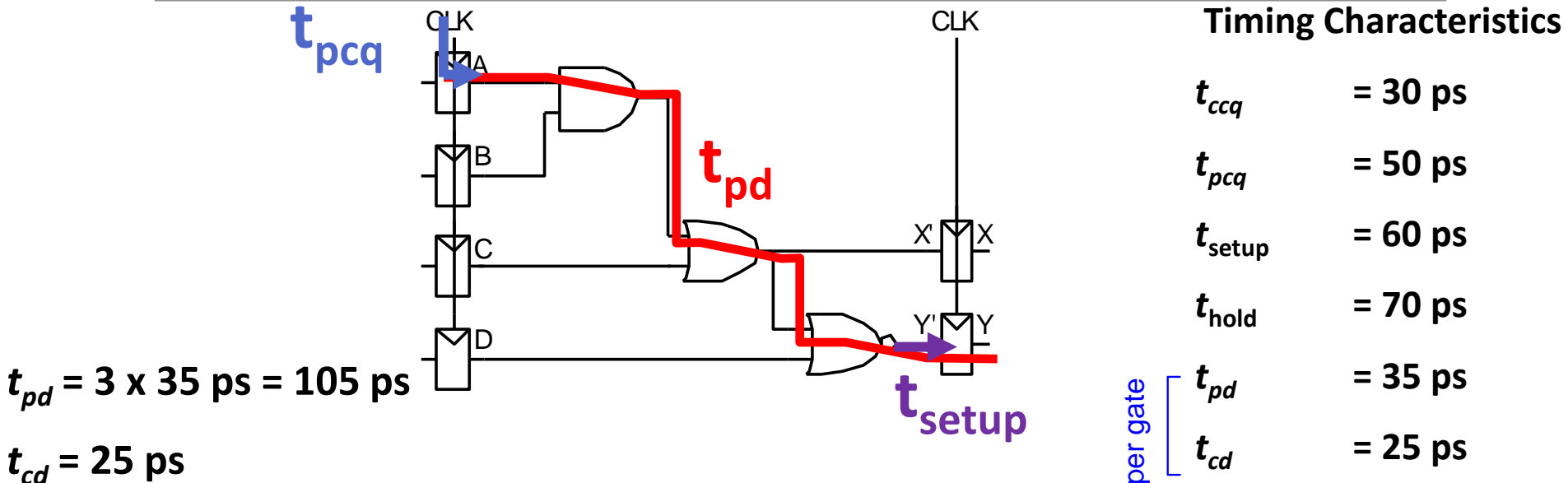

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{setup}$$


$$T_c > (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_{max} = 1/T_c = 4.65 \text{ GHz}$$

Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{hold} ?$$

# Example: Timing Analysis

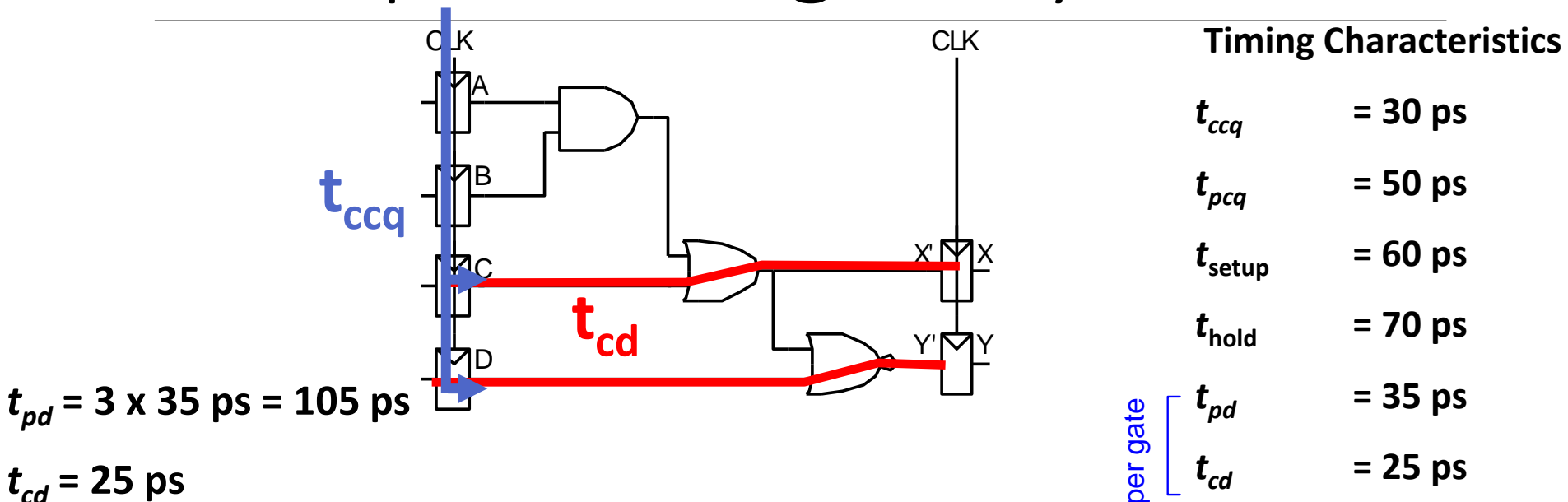

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{setup}$$

$$T_c > (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_{max} = 1/T_c = 4.65 \text{ GHz}$$


Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{hold} ?$$

$$(30 + 25) \text{ ps} > 70 \text{ ps} ?$$



# Example: Timing Analysis

 

## Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

per gate

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{\text{setup}}$$

$$T_c > (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_{\text{max}} = 1/T_c = 4.65 \text{ GHz}$$

Check hold time constraints:


$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 25) \text{ ps} > 70 \text{ ps} ?$$

**FAIL**

# Example: Fixing Hold Time Violation

## Add buffers to the short paths:

 

## Timing Characteristics

$t_{ccq}$	= 30 ps
$t_{pcq}$	= 50 ps
$t_{\text{setup}}$	= 60 ps
$t_{\text{hold}}$	= 70 ps
$t_{pd}$	= 35 ps
$t_{cd}$	= 25 ps

per gate

 $t_{pd} =$  $t_{cd} =$ 

## Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{setup}$$

$T_c >$


$$f_c =$$

### Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{hold} ?$$

# Example: Fixing Hold Time Violation

Add buffers to the short paths:

 

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

per gate

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{setup}$$

$$T_c >$$


$$f_c =$$

Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{hold} ?$$

# Example: Fixing Hold Time Violation

Add buffers to the short paths:

 

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

per gate

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{\text{setup}}$$

$$T_c > (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$


$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

# Example: Fixing Hold Time Violation

Add buffers to the short paths:

 

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

per gate

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{\text{setup}}$$

$$T_c > (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$


Note: no change to max frequency!

Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

# Example: Fixing Hold Time Violation

Add buffers to the short paths:

 

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{setup} = 60 \text{ ps}$$

$$t_{hold} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

per gate

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{setup}$$

$$T_c > (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$


Check hold time constraints:

$$t_{ccq} + t_{cd} > t_{hold} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ?$$

# Example: Fixing Hold Time Violation

Add buffers to the short paths:

 

Timing Characteristics

$$t_{ccq} = 30 \text{ ps}$$

$$t_{pcq} = 50 \text{ ps}$$

$$t_{\text{setup}} = 60 \text{ ps}$$

$$t_{\text{hold}} = 70 \text{ ps}$$

$$t_{pd} = 35 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

per gate

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Check setup time constraints:

$$T_c > t_{pcq} + t_{pd} + t_{\text{setup}}$$

$$T_c > (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

Check hold time constraints:


$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$

$$(30 + 50) \text{ ps} > 70 \text{ ps} ?$$

**PASS**
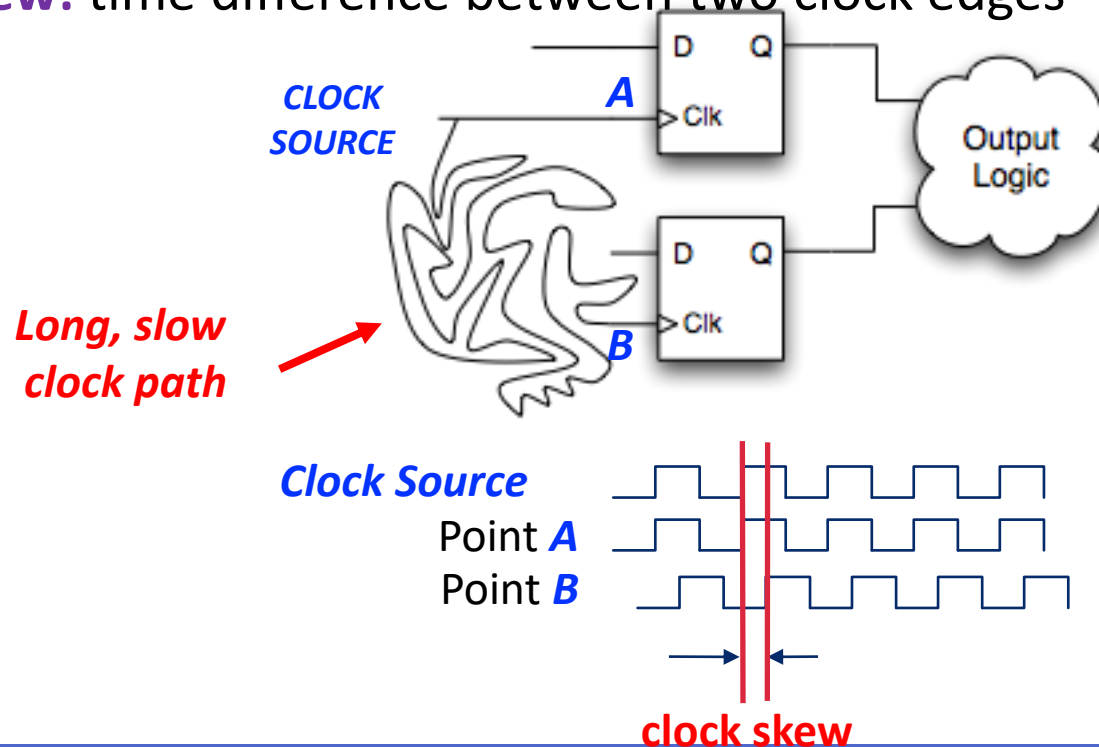
# Clock Skew


- To make matters worse, **clocks have delay** too!
  - The clock does **not** reach all parts of the chip at the same time!
- **Clock skew**: time difference between two clock edges







# Clock Skew Example

 Example of the **Alpha 21264** clock skew spatial distribution


 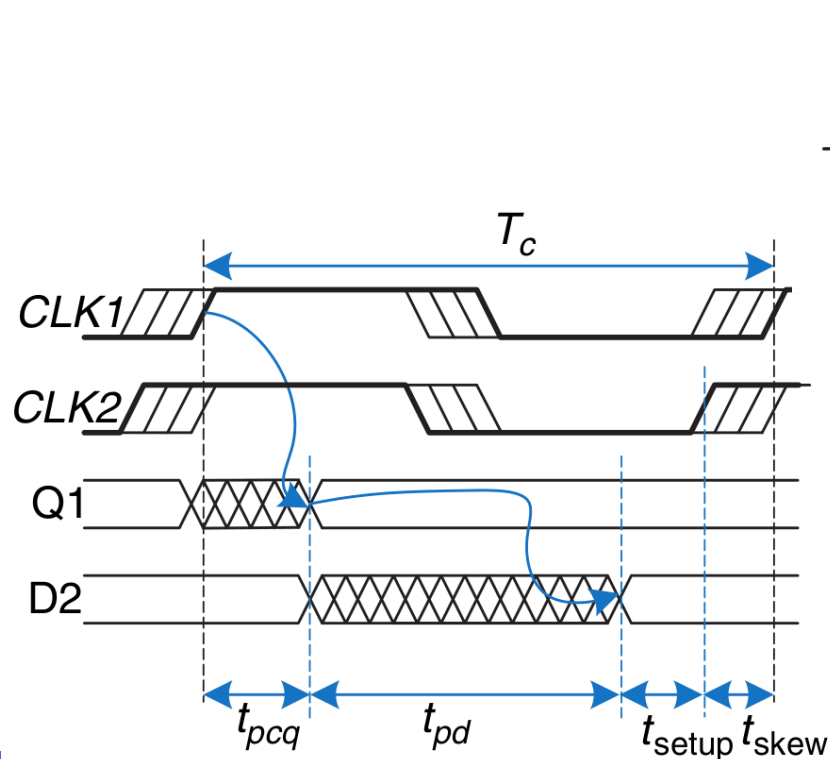
# Clock Skew: Setup Time Revisited

- **Safe timing** requires considering the **worst-case skew**
  - Clock arrives at **R2 before R1**
  - Leaves **as little time as possible** for the **combinational logic**



Signal must arrive at D2 **earlier!**



This effectively **increases**  $t_{setup}$ :

$$T_c > t_{pcq} + t_{pd} + \underbrace{t_{setup} + t_{skew}}_{\text{effective setup time}}$$

$$T_c > t_{pcq} + t_{pd} + t_{setup, \text{effective}}$$
  
# Clock Skew: Hold Time Revisited

- **Safe timing** requires considering the **worst-case skew**
  - Clock arrives at **R2 *after* R1**
  - Increases the **minimum required delay** for the **combinational logic**



Signal must arrive at D2 **later!**

This effectively *increases*  $t_{\text{hold}}$ :

$$t_{cd} + t_{ccq} > \underbrace{t_{hold} + t_{skew}}$$


$$t_{cd} + t_{ccq} > t_{hold, effective}$$

# Clock Skew: Summary

- **Skew** effectively **increases** both  $t_{\text{setup}}$  and  $t_{\text{hold}}$ 
  - Increased **sequencing overhead**
  - i.e., less useful work done per cycle

Designers must keep skew to a **minimum**

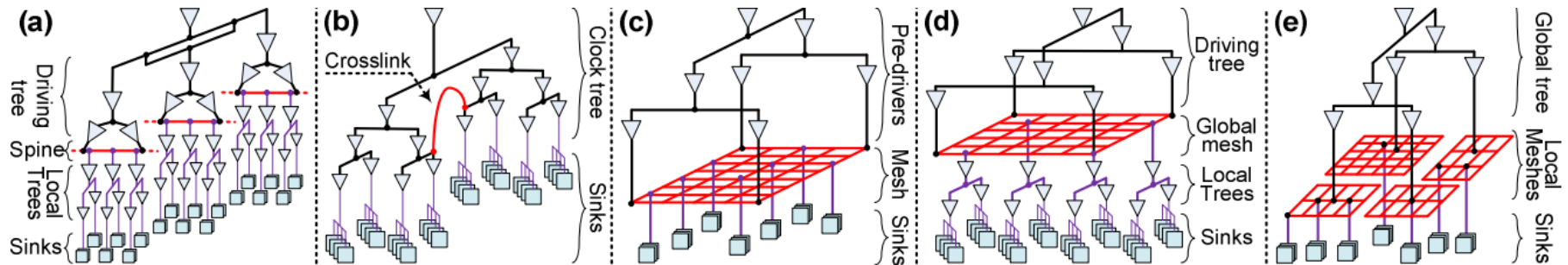- Requires intelligent **"clock network"** across a chip
- **Goal: clock** arrives at all locations at roughly the **same time**




Source: Abdelhadi, Ameer, et al. "Timing-driven variation-aware nonuniform clock mesh synthesis." GLSVLSI'10.

# Delay in Verilog


---
 
# Gate Delay in Verilog

- Rise **delay**
  - Associated with a gate output transition to a **1** from another value.



 - Fall **delay**
  - Associated with a gate output transition to a **0** from another value.



# Gate Delay in Verilog

---

- Turn-off **delay**
  - Associated with a gate output transition to the **high impedance value (z)** from another value
- **Delay** for value change to x
  - Associated with a gate output transition to **unknown value (x)** from another value
  - The minimum of the three delays is considered

# Single Delay

---


- Delay for **all transistors**
  - **buf #(delay\_time)** a1(out, i)
  - **buf #(5)** a1(out, i)
  - **buf #(mindelays:typdelays:maxdelays)** a1(out, i)
  - **buf #(4:5:6)** a1(out, i)


 
# Single Delay (cont'd)

```
`timescale 1ns/100ps
module buf_gate();
reg      in;
wire     out;
buf #(5) (out, in)
initial begin
$monitor ("Time = %g in = %b out=%b", $time, in, out);
    in = 0;
    #10 in = 1;
    #10 in = 0;
    #10 $finish;
end
endmodule
```

Time = 0 in = 0  
out=x  
Time = 5 in = 0  
out=0  
Time = 10 in = 1  
out=0  
Time = 15 in = 1



# Two Delays


---

- Delay for **rise and fall specifications**
  - **and #(rise\_val, fall\_val)** a1(out, i1, i2)
  - **and #(4, 6)** a1(out, i1, i2)
  - **and #(mindelays: typdelays: maxdelays, mindelays: typdelays: maxdelays)** a1(out, i1, i2)
  - **and #(3:4:5, 5:6:7)** a1(out, i1, i2)
 
# Two Delays (cont'd)

```
`timescale 1ns/100ps
module buf_gate();
reg      in;
wire     out;
buf #(2,3) (out, in);
initial begin
$monitor ("Time = %g in = %b out=%b", $time, in, out);
    in = 0;
    #10 in = 1;
    #10 in = 0;
    #10 $finish;
end
endmodule
```

Time = 0 in = 0  
out=x  
Time = 3 in = 0  
out=0  
Time = 10 in = 1  
out=0  
Time = 12 in = 1  
out=1  
Time = 20 in = 0  
out=1  
Time = 23 in = 0



# Three Delays

---

- Delay for **rise, fall, and turn-off specifications**
  - **bufif0 #(rise\_val, fall\_val, turnoff\_val) a1(out, in, control)**
  - **bufif0 #(3, 4, 5) a1(out, in, control)**
  - **bufif0 #(mindelay: typdelay: maxdelay, .., mindelay: typdelay: maxdelay) a1(out, i1, i2)**
  - **bufif0 #(2:3:4, 3:4:5, 4:5:6) a1(out, i1, control)**


# All Delays (cont'd)

```
`timescale 1ns/100ps
module buf_gate();
reg in;
wire rise_delay;
wire fall_delay;
wire all_delay;

buf #(1,0) U_rise (rise_delay, in);
buf #(0,1) U_fall (fall_delay, in);
buf #1 U_all (all_delay, in);

initial begin
in = 0;
#10 in = 1;
#10 in = 0;
#20 $finish;
end
endmodule
```

 Time = 0 in = 0 rise\_delay = 0 fall\_delay = x all\_delay = x  
Time = 1 in = 0 rise\_delay = 0 fall\_delay = 0 all\_delay = 0  
Time = 10 in = 1 rise\_delay = 0 fall\_delay = 1 all\_delay = 0  
Time = 11 in = 1 rise\_delay = 1 fall\_delay = 1 all\_delay = 1  
Time = 20 in = 0 rise\_delay = 0 fall\_delay = 1 all\_delay = 1  
Time = 21 in = 0 rise\_delay = 0 fall\_delay = 0 all\_delay = 0



# #`num`

---

- Number of ticks simulator should delay current statement execution
  - **# 1 bufif0 #(3, 4, 5) a1(out, in, control)**

# Delay Specification in Verilog (cont'd)

---

- Method of choosing a min/typ/max value may vary for different simulators.

Example:

ModelSim SE 6.0

Simulate -> Start Simulation: Tab -> Verilog:

Box -> delay selection

- ``timescale` Time Unit/Simulation Precision
- ``timescale` 1ns/100ps

# Delay Specification in Verilog (cont'd)

The screenshot displays the ModelSim SE vlog 6.5b Compiler interface. The top-left pane shows the project hierarchy with instances of the 'gt' module. The top-right pane shows the Verilog code for 'alaki.v'. The bottom pane shows the simulation transcript.

**Instance Hierarchy:**

Instance	Design unit	De
gt	gt(fast)	Mo
bb[0]	gt(fast)	Pro
bb[1]	gt(fast)	Pro
bb[2]	gt(fast)	Pro

**Verilog Code (alaki.v):**

```
Ln# 1 module gt(output c, o, [7:0] t);
Ln# 2 wire d,e;
Ln# 3 reg a,b;
Ln# 4
```

**Simulation Transcript:**

```
VSIM8> vlog alaki.v
# Model Technology ModelSim SE vlog 6.5b Compiler 2009.05 May 21 2009
# -- Compiling module gt
# -- Compiling module testbench
# -- Compiling module adder
# -- Compiling module test
# -- Compiling module testadder
# -- Compiling module adder8
#
# Top level modules:
#   gt
#   testbench
#   test
#   testadder
VSIM9> vsim gt +maxdelays
# vsim +maxdelays gt
# ** Note: (vsim-3812) Design is being optimized...
# Loading work.gt(fast)


VSIM10>
```

**Status Bar:** "alaki.v" was modified after it was compiled | Ln: 1 Col: 23 | Project : alaki | Now: 0 ns Delta: 0 | sim:/gt - Limited Visibility Region



# Sample 1

---

 


# Sample 1: Design Block

---

```
`timescale 1ns/100ps
module D(out, a, b, c);
  input  a, b, c;
  output out;
  wire  e;


  and #5(e, a, b);
  or  #4(out, e, c);

endmodule
```

 
 
# Sample 1: Test Block

```
module top;  
    reg      A, B, C;  
    wire     OUT;  
  
    D d1(OUT, A, B, C);  
  
    initial  
        begin  
            A= 1'b0; B= 1'b0; C= 1'b0;  
            #10 A= 1'b1; B= 1'b1; C=  
1'b1;  
            #10 A= 1'b1; B= 1'b0; C=  
1'b0;  
            #20 $finish;  
  
endmodule
```





# Sample 1: Timing Analysis

```
module top;
```

```
...  
A= 1'b0; B= 1'b0; C= 1'b0;  
#10 A= 1'b1; B= 1'b1; C= 1'b1;  
#10 A= 1'b1; B= 1'b0; C= 1'b0;  
#20 $finish;  
...
```

```
endmodule
```

  

# Thank You

---

