




Digital System Design

Hajar Falahati


hfalahati@ipm.ir
hfalahati@ce.sharif.edu

System Design

 - You are **expert** in designing 🧐
- Conventional design approach is challenging



Automated Design Flow

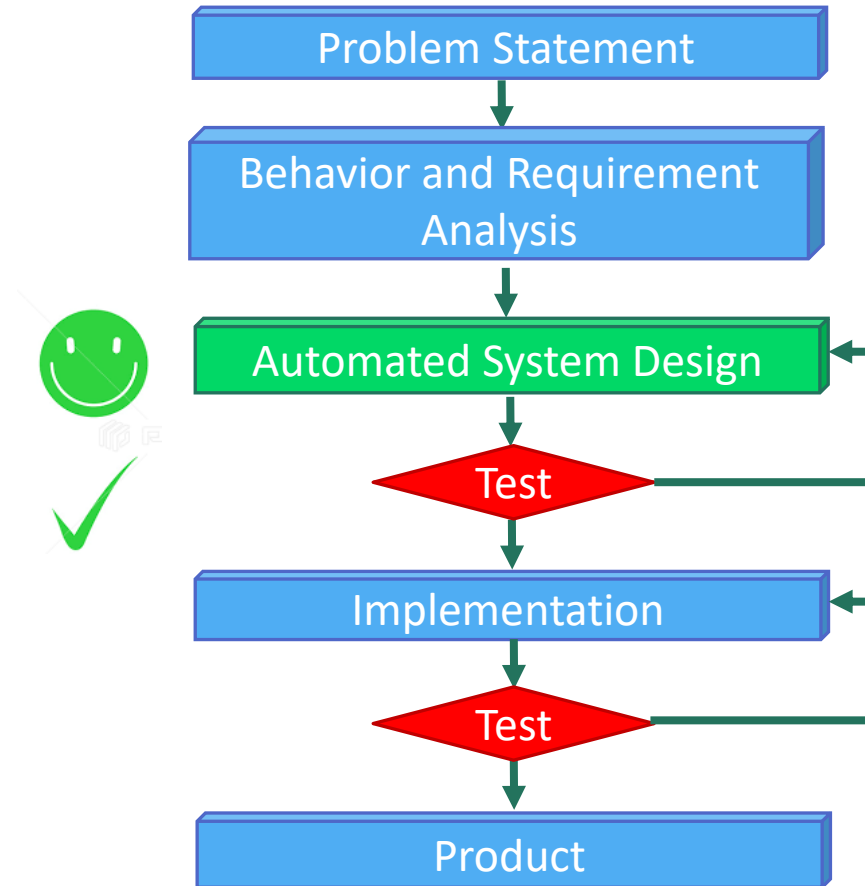


Outline

- Hello Verilog
 - Big picture
 - Levels




Hello Verilog


VERILOG: Hello Friends 😊

 

Design Flow



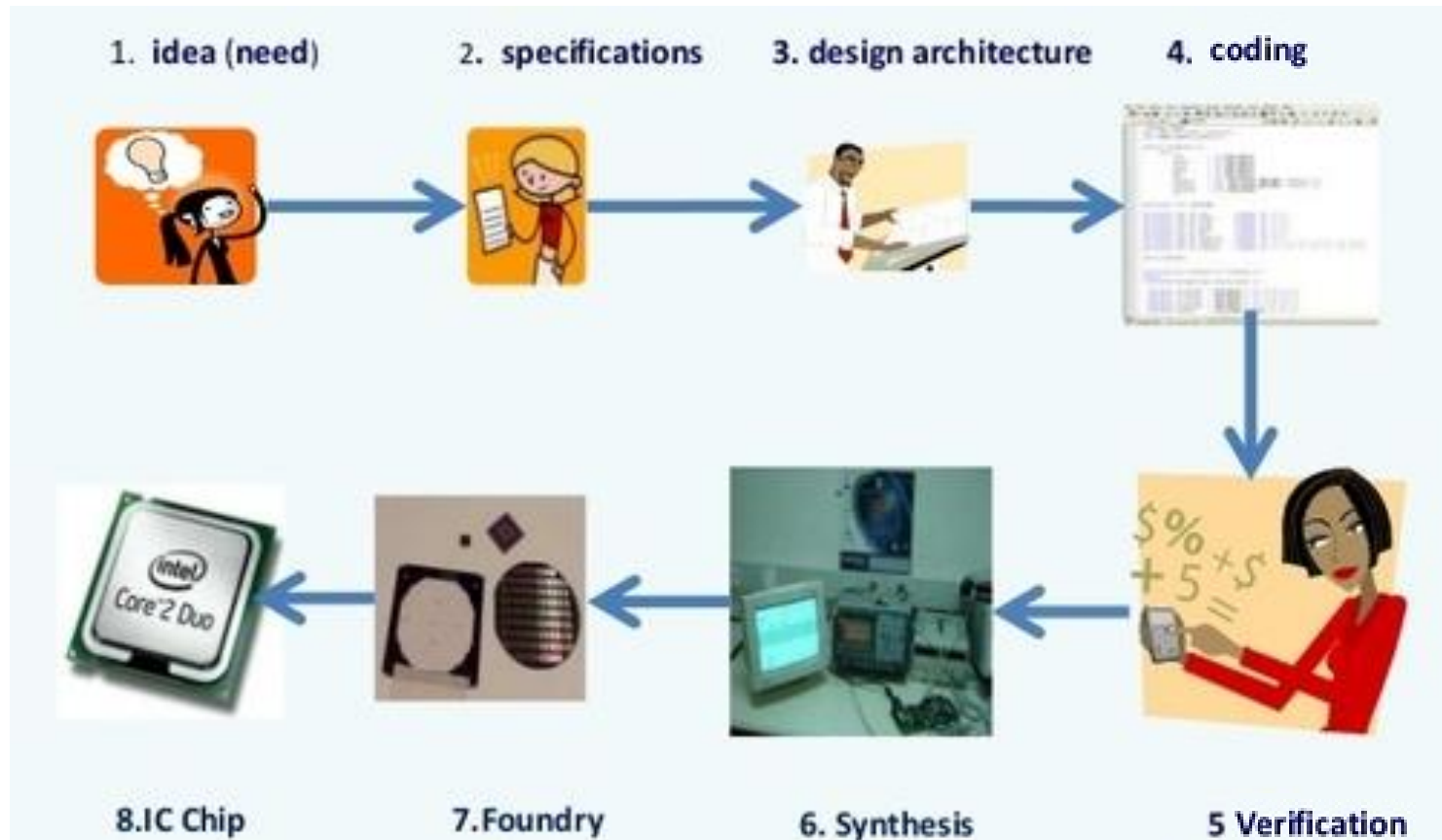


Design Flow in Detail

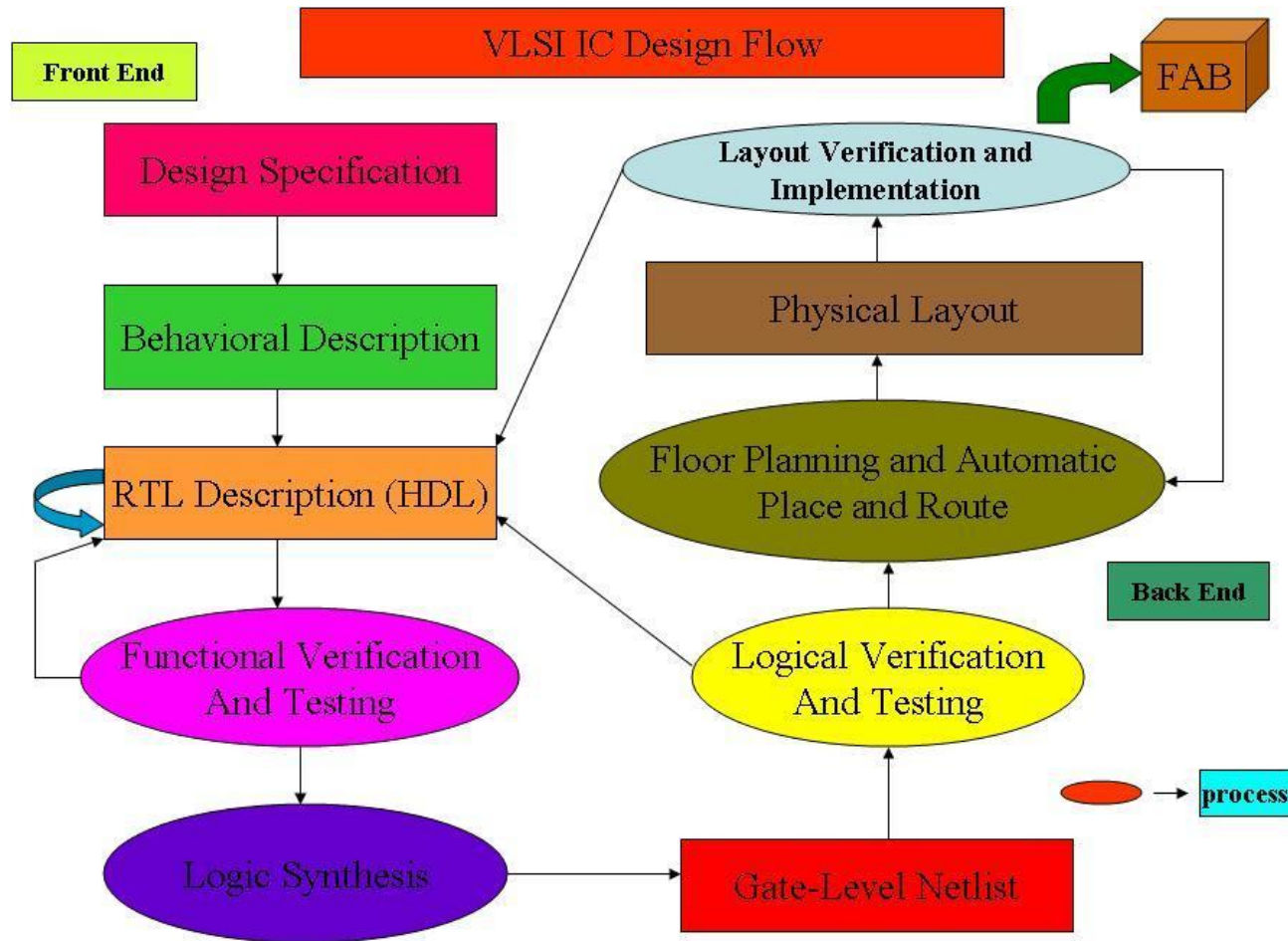


Simulation


- Design verification

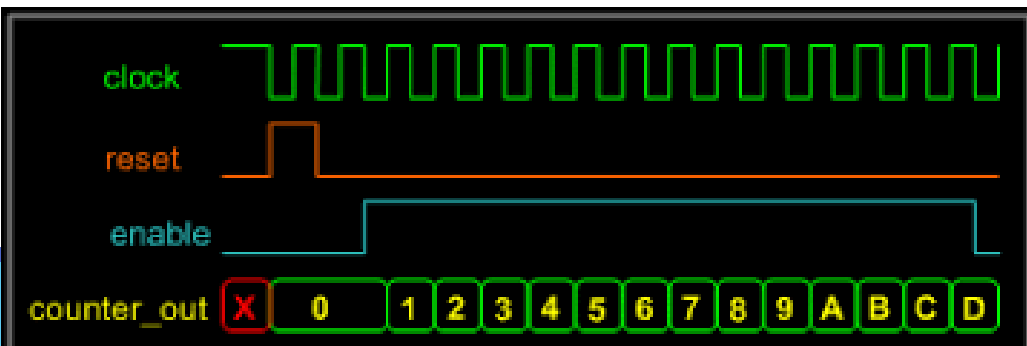 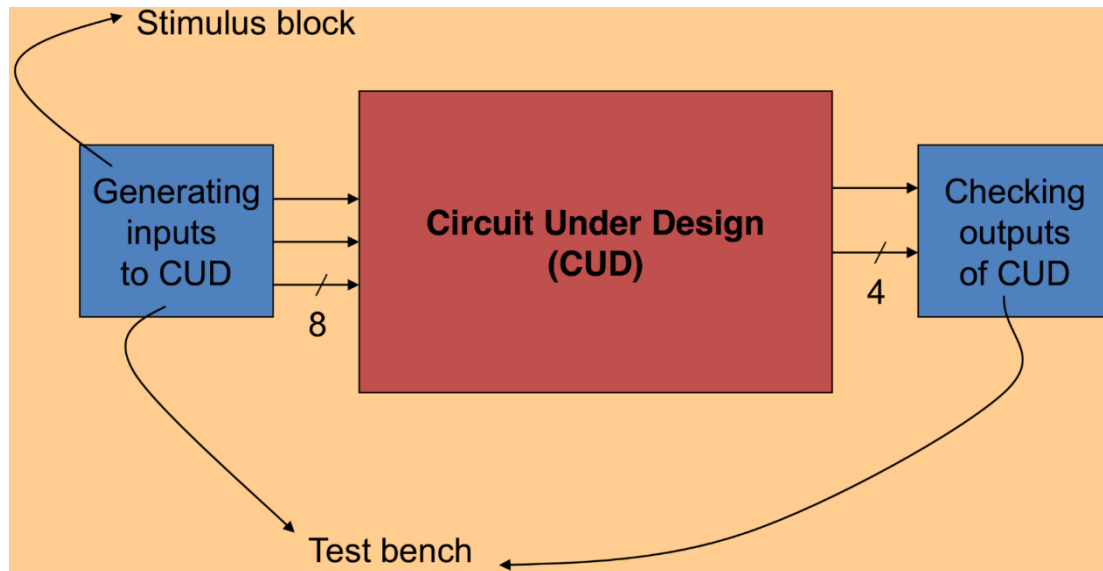


Synthesis

- Design implementation on real hardware

 

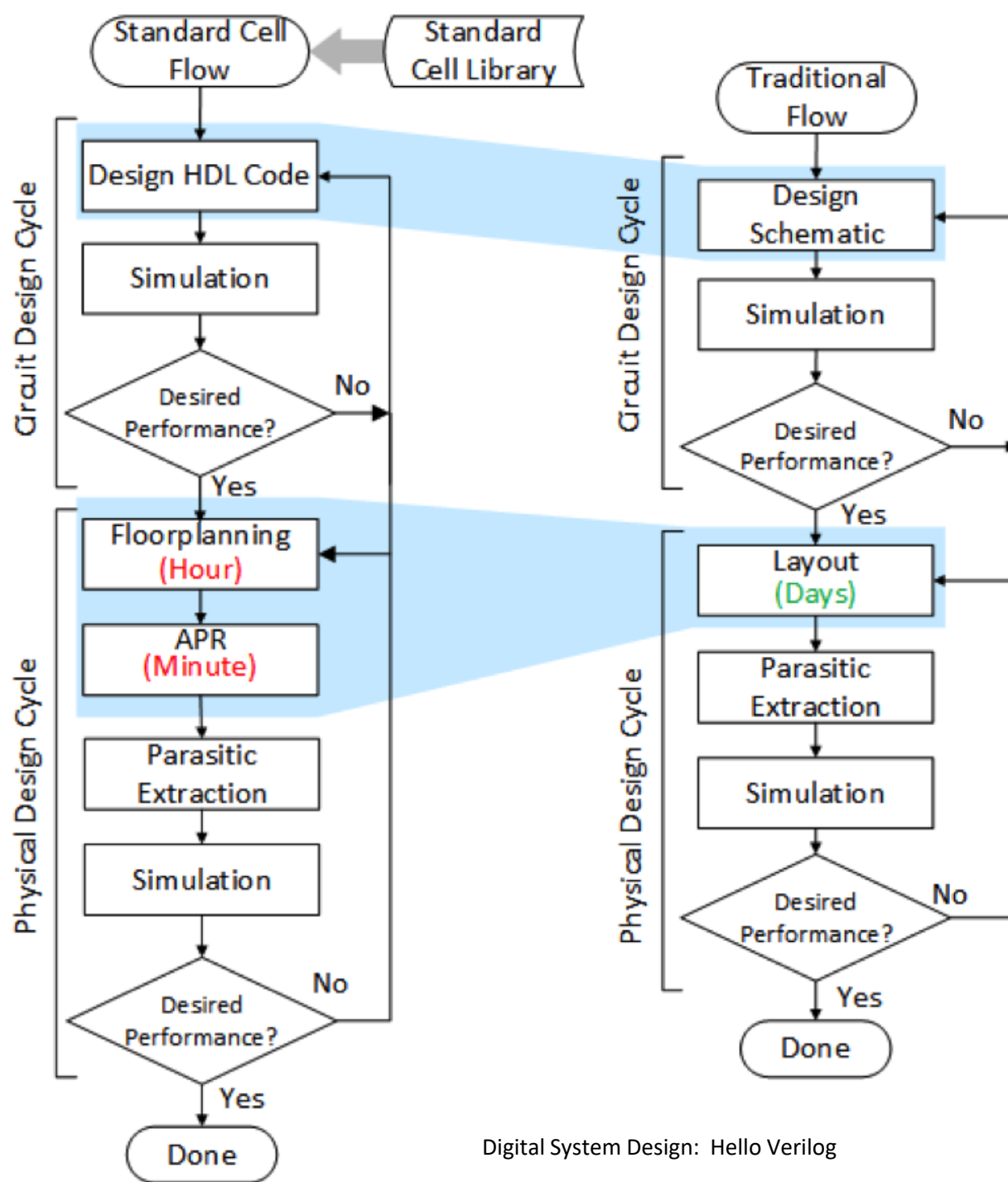

Basic Blocks

 

Module

- A **module** is the **main building block** in Verilog
- Collection of **lower-level design block**
- Provides necessary **functionality** to **higher-level block**
- Hides **internal implementation**

Defining a Module in Verilog



- We first need to define:
 - **Name** of the module
 - **Directions** of its **ports** (e.g., **input**, **output**)
 - **Names** of its **ports**

Then:

- Describe the **functionality** of the module



Implementing a Module in Verilog

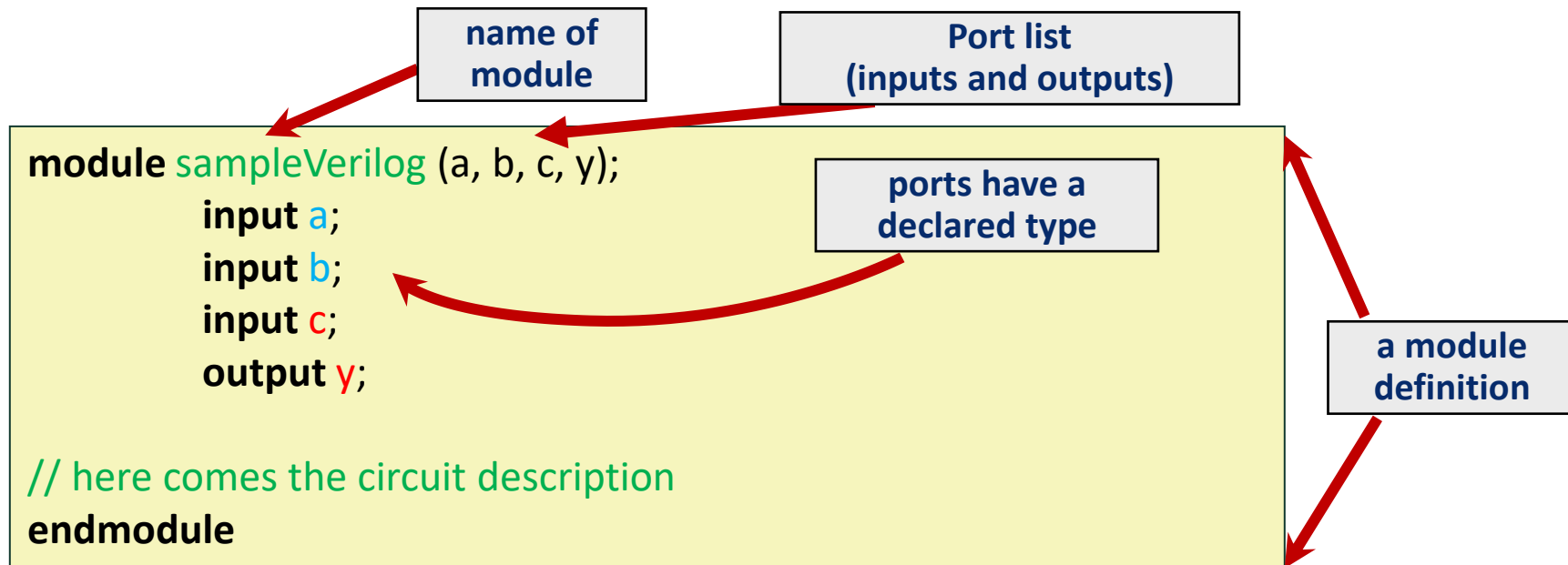 

A Question of Style

The following two codes are functionally identical

```
module test ( a, b, y );  
    input a;  
    input b;  
    output y;  
  
endmodule
```

```
module test ( input a,  
              input b,  
              output y );  
  
endmodule
```

port name and direction declaration
can be combined

What If We Have Multi-bit Input/Output?

- You can also define multi-bit Input/Output (Bus)
 - [range_end : range_start]
 - **Number of bits:** range_end – range_start + 1
- Example:
 - A represents a 32-bit value, so we prefer to define it as: [31:0] a
 - It is preferred over [0:31] a which resembles *array* definition
 - It is a good practice to be consistent with the representation of multi-bit signals, i.e., always [31:0] or always [0:31]

```
input  [31:0] a;    // a[31], a[30] .. a[0]
output [15:8] b1;   // b1[15], b1[14] .. b1[8]
output [7:0]  b2;   // b2[7], b2[6] .. b2[0]
input                c; // single signal
```

Manipulating Bits

- Bit Slicing

```
// You can assign partial buses  
wire [15:0] longbus;  
wire [7:0] shortbus;  
assign shortbus = longbus[12:5];
```

Manipulating Bits

- Bit Slicing

```
// You can assign partial buses  
wire [15:0] longbus;  
wire [7:0] shortbus;  
assign shortbus = longbus[12:5];
```

- Concatenation

```
// Concatenating is by {}  
assign y = {a[2],a[1],a[0],a[0]};
```

Manipulating Bits

- Bit Slicing

```
// You can assign partial buses
wire [15:0] longbus;
wire [7:0] shortbus;
assign shortbus = longbus[12:5];
```

- Concatenation

```
// Concatenating is by {}
assign y = {a[2],a[1],a[0],a[0]};
```

- Duplication

```
// Possible to define multiple copies
assign x = {a[0], a[0], a[0], a[0]}
assign y = { 4{a[0]} }
```

Basic Syntax

- Similar to C
- **Case sensitive**
 - `SomeName` and `somename` are not the same!
- **Keywords are in lowercase**
- Names **cannot start** with **numbers**:
 - `2good` is not a valid name
- Whitespaces are **ignored**
- **Comments**

```
// Single line comments start with a //  
  
/* Multiline comments  
   are defined like this */
```

Operators

- Unary

```
a = b;
```

- Binary


```
a = b && c;
```

- Ternary

- The only ternary operator

```
a = b ? c:d;
```

Design

 


```
always @(posedge clk) begin
```

```
assign pcinc = pc + 4;
```


```
for (i=0; i < 31; i = i+1) begin
```

Digital System Design: Hello Verilog

Three Common Abstraction Level

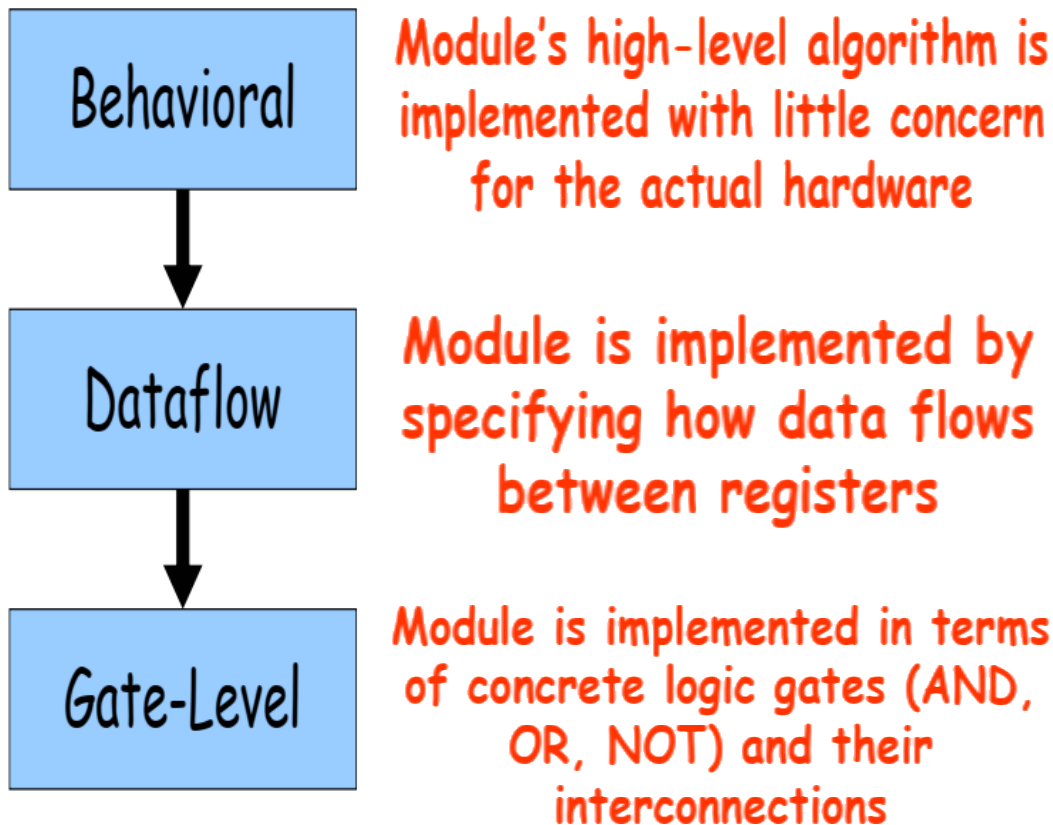

Three Common Abstraction Level

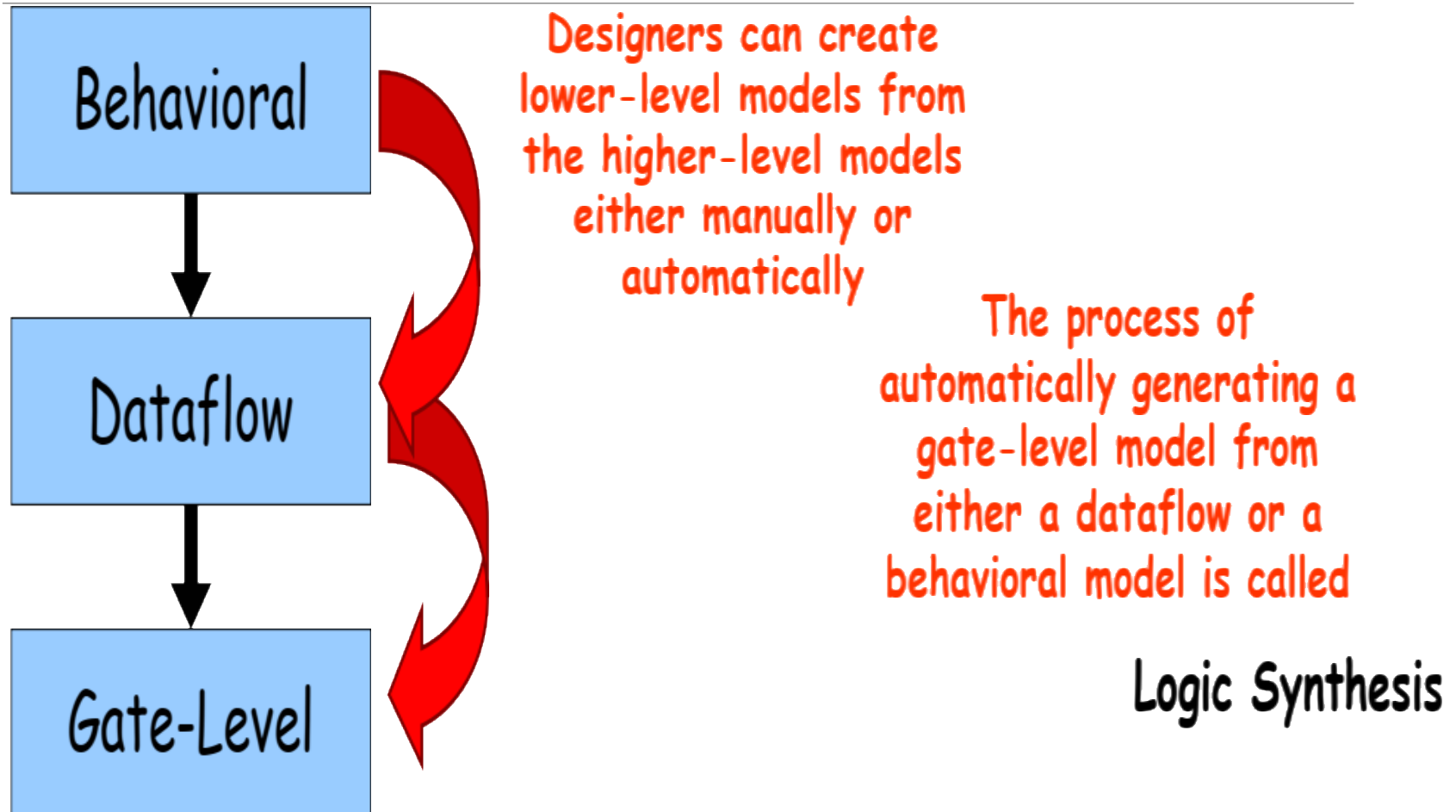


Structural Style

- **Structural (Gate-Level)**

- The module body contains **gate-level description** of the circuit
- Describe how modules are interconnected
- Each module contains other modules (instances)
- ... and interconnections between these modules
- Describes a hierarchy

Structural HDL: Instantiating a Module

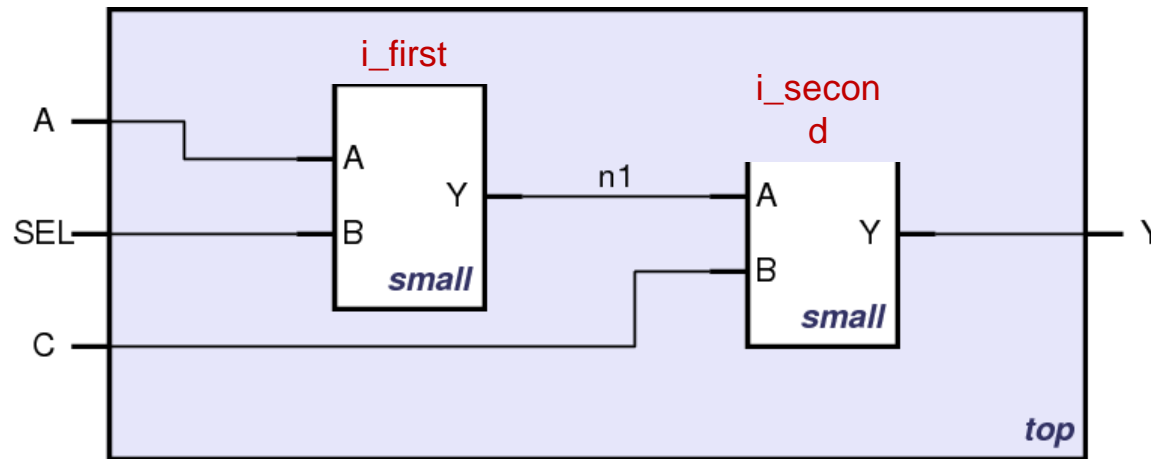


Schematic of module "top" that is built from two instances of module "small"

Structural HDL Example

Module Definitions in Verilog
 
```
module top(A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
endmodule
```




```
module small(A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

Structural HDL Example

Defining wires (module interconnections)

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
endmodule
```

 

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```


Structural HDL Example

The first instantiation of the “small” module

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
  // instantiate small once  
  small i_first ( .A(A),  
                  .B(SEL),  
                  .Y(n1) );
```

```
endmodule
```

 


```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
  // description of small  
endmodule
```

Structural HDL Example

The second instantiation of the “small” module
 
```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;  
  
  // instantiate small once  
  small i_first ( .A(A),  
                 .B(SEL),  
                 .Y(n1) );  
  
  // instantiate small second time  
  small i_second ( .A(n1),  
                  .B(C),  
                  .Y(Y) );  
  
endmodule
```



```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;  
  
  // description of small  
  
endmodule
```

Structural HDL Example

Short form of module instantiation

```
module top (A, SEL, C, Y);  
  input A, SEL, C;  
  output Y;  
  wire n1;
```

```
// alternative
```


```
small i_first ( A, SEL, n1 );
```

```
/* Shorter instantiation,  
   pin order very important */
```

```
// any pin order, safer choice
```

```
small i_second ( .B(C),  
                 .Y(Y),  
                 .A(n1) );
```

```
endmodule
```

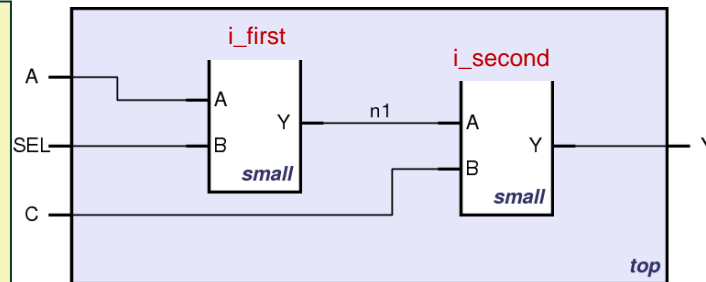

```
module small (A, B, Y);  
  input A;  
  input B;  
  output Y;
```

```
// description of small
```

```
endmodule
```


Structural HDL Example 2

- Verilog supports basic logic gates as predefined *primitives*
 - These primitives are *instantiated* like modules except that they are predefined in Verilog and *do not need a module definition*

```
module mux2(input  [3:0] d0, d1,
             input          s,
             output [3:0] y);

    wire ns;
    and  g1 (y1, d0, ns);
    and  g2 (y2, d1, s);
    or   g3 (y, y1, y2);
    not  g4 (ns, s);
endmodule
```

Data Flow Modeling

- Continuous assignment

$v = a + b;$

$w = b * 2;$


$x = v - w$

$y = v + w$

$z = x * y$

Sequential
 
```
module sampleDataFlow (a, b, z);  
    input a, b;  
    output z;  
    wire v, w, x, y;  
  
    assign v = a + b;  
    assign w = b * 2;  
    assign x = v - w;  
    assign y = v + w;  
    assign z = x * y;  
  
endmodule
```



Dataflow

Behavioral

- The module body contains functional description of the circuit
- Contains logical and mathematical operators
- **Level of abstraction is higher than gate-level**
 - Many possible gate-level realizations of a behavioral description

Thank You

