



Digital System Design

Hajar Falahati

hfalahati@ipm.ir
hfalahati@ce.sharif.edu

Design Session 3

Carry Look Ahead (CLA) Adder

- Steps:
 - Sketch block diagram and implement 1-bit full adder
 - Sketch block diagram and implement 4-bit CLA adder
- Model level
 - Behavioral
 - Dataflow
- How to deliver
 - Submit at CW



Thank You

